eGaN® ICs for Low Voltage DC-DC Applications

eGaN[®] ICs for Low Voltage DC-DC Applications



Michael de Rooij, Ph.D., Vice President of Applications Engineering, Yuanzhe Zhang, Ph.D., Director of Applications Engineering

eGaN[®] FETs from EPC have repeatedly demonstrated higher performance over MOSFET counterparts in many applications [1]. The lateral structure and material properties of eGaN FETs make it possible to monolithically integrate a number of FETs as demonstrated by products such as the EPC2107 [2]. The next phase in the eGaN FET and IC evolution includes gate driver integration. Integrating the gate driver with the FET offers a number of additional advantages over discrete gate driver and FET solutions such as extremely low common source inductance, matched gate driver to FET, and ease of design. All the traditional eGaN FET benefits such as significantly lower capacitance and inductance with zero reverse recovery charge (Q_{RR}) in a smaller footprint for a given on-resistance ($R_{DS(on)}$) than comparable MOSFETs are retained. However, the combined effect of the new characteristics and benefits ensures an ever great performance over comparable MOSFETs.

In this application note, we introduce EPC's new eGaN IC - EPC2112 that includes an integrated gate driver [3] used in a 27 W, 14 V - 48 V input to 19 V output single-ended primary-inductor converter (SEPIC) built on the EPC9131 demonstration board. The SEPIC converter is ideal for applications with a wide input voltage range and where the output voltage can be either below or above the input voltage. One application example is the post voltage regulator for resonant wireless power receiver unit. In this application the rectified voltage depends on factors such as the distance from the power surface, location and presence of other foreign objects and load power requirements.

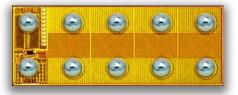


Figure 1. Bump side of EPC2112 eGaN IC. Dimensions: 2.9 x 1.1 mm.

Introducing the EPC2112 eGaN IC

The lateral structure of eGaN FETs allows for monolithic integration of a gate driver and a power FET with the goal being to enhance performance, reduce cost and simplify design. The single FET EPC2112 eGaN IC was designed with that in mind. Figure 1 shows a photo of the bump side of the EPC2112. It has a low bump count and only needs an input signal and 5V supply voltage to operate. The bump assignment is layout friendly, making designs easier to complete thereby ensuring high performance. Monolithic integration of the gate driver to the FET offers the lowest possible common source inductance (CSI) as it is moved to within the IC structure. Furthermore the gate driver has been optimized for the FET being driven to offer maximum performance under any operating condition. These benefits are on top of the well-established low capacitance and inductance, and zero reverse recovery charge (Q_{RR}) that enable efficient operation at high switching frequencies even under hard switching conditions. The key characteristics of the EPC2112 are given in table 1.

SEPIC Overview

The single-switch SEPIC topology is a noninverting output buck and boost converter. It can be configured with either a coupled inductor or two independent inductors. The two independent inductors version will be evaluated in this application note. The power circuit schematic of the SEPIC using EPC2112 is shown in figure 1.

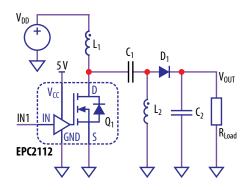


Figure 2. Schematic of SEPIC using EPC2112 with integrated gate driver.

Part Number	V _{DS}	$R_{DS(on)} V_{IN} = 5 V, V_{CC} = 5 V, T_{J} = 25^{\circ}C$	Q _{0SS} V _{IN} = 0 V, V _{CC} = 5 V	I _D Continuous T _A = 25°C
EPC2112	200 V	40 mΩ	24 nC V _{DS} = 100 V	$\begin{array}{c} 10 \text{ A} \\ \text{R}_{\text{\thetaJA}} = 18^{\circ}\text{C/W} \end{array}$

Table 1. EPC2112 key characteristics.

Design procedure for the two independent inductor SEPIC is well documented [4, 5, 6] and was followed to design the converter in this application note. The choice of an eGaN IC for the switch of the SEPIC allows high efficiency operation at high frequency despite operating under hard-switching conditions. The higher switching frequency allows lower value inductors to be used thereby reducing the size of the converter without compromising the performance.

Design examples

A SEPIC design example with specifications given in table 2 is presented.

The LM3481 [7] current-mode controller was chosen for the SEPIC as it included an on chip regulator that could be used to provide supply voltage power the eGaN IC. The LM3481 also comes with various control and protection features that can be configured to yield a stable converter capable of operation over a wide input voltage and load power ranges.

The designed power circuit components for the SEPIC are also shown in Table 2. Given that many modern converter applications have a thickness (component height) restriction, the components selected for this design example were 4 mm or less in height. Low profile ferrite inductors from Vishay (IHLP2525CZER220M11) and low profile electrolytic capacitors from Nichicon (UZR1H100MCL1GB) were used in the design as the highest profile components on the board. A 100 V schottky diode capable of 5 A from Diodes Inc. (PDS5100-13) was used for the output rectifier. A photo of the configured printed circuit board is shown in figure 3.

To ensure stable operation across the entire operating range conditions, an average model similar to [8] was created for the two inductor SEPIC and used to determine the phase and gain margins for the feedback controller. The feedback controller design method given in [9] was followed to yield maximum control bandwidth. Current-mode control with slope compensation was implemented to further ensure stable operation and limit the input current under low supply voltage conditions.

The pin assignment on the EPC2112 makes it easy to design a layout with high performance requirements. The bump assignment in figure 4 shows the grouping of the power and control bumps. Low loop inductance is essential for high performance operation and that have been achieved using the long narrow layout of the power bumps. The control signals are fed into one side of the device to achieve proper decoupling of the power and control loops.

An example layout is shown in figure 5, where control circuitry is on the left side and power on the right side and can be design decoupled from each other. Since the gate drive is integrated, the PWM loop inductance is significantly less critical than in the case of a FET only design. Therefore, the controller may be placed further away from the eGaN IC. Wide traces for drain and source connections ensure low power loop inductance. The design can be achieved using only two layers with most of the connection on a single layer, thus leaving the bottom layer for ground assignment only thereby ensuring low EMI radiation from the circuit.

Input Voltage	Output Voltage	Frequency	Max Power	С ₁	D ₁	L ₁ , L ₂
14-48 V	19 V	300 kHz	27 W	20 µF	100 V, 5 A	22 μH

Table 2. Summary of the SEPIC design parameters.

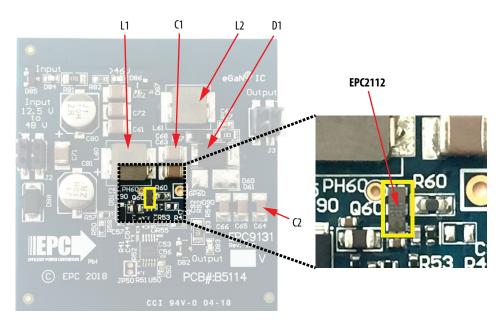


Figure 3. Photo of EPC9131 SEPIC regulator with EPC2112.

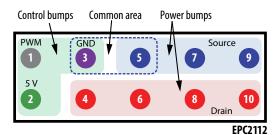


Figure 4. Bump assignment for easy layout.

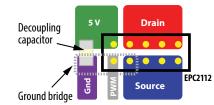


Figure 5. Example layout with low power loop inductance.

eGaN® ICs for Low Voltage DC-DC Applications

Design evaluation

The SEPIC converter was designed on the EPC9131 evaluation board and tested under various input voltage and load power settings. The efficiency of the converter was measured with a range of output power from 1 W through 27 W, at discrete input voltage steps from 20 V through 48 V. The measured power loss includes logic/control circuity and the results are shown in figure 6. The peak efficiency

is around 90% at 20 V input. The increase of input voltage results in higher power losses. At 48 V input and 27 W output, the efficiency is 85%.

The measured switch-node waveform of the SEPIC with EPC2112 is shown in figure 7 that reveals good clean transitions despite hard switching.

To verify the performance of the integrated gate driver, a second identical SEPIC was designed built with the only difference being a commercially available discrete GaN compatible gate driver from Texas Instruments (UCC27611) [10] and paired with the EPC2019 eGaN FET [11] that replaced the EPC2112 eGaN IC. The efficiency of this converter was measured at 48 V input delivering the same range of output power as the eGaN IC version with the results shown in figure 8.

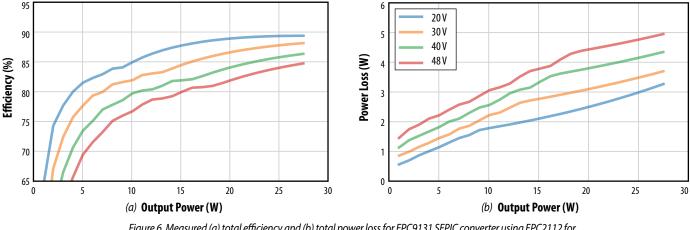


Figure 6. Measured (a) total efficiency and (b) total power loss for EPC9131 SEPIC converter using EPC2112 for various input voltages delivering 19 V output over the load range from 1 W through 27 W.

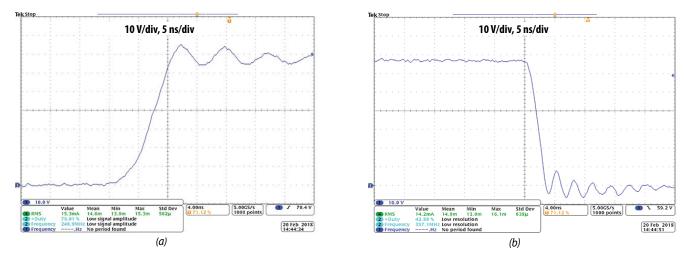


Figure 7. Switch-node voltage waveforms of the SEPIC at 48 V input, 19 V and 27 W output. (a) rising edge and (b) falling edge.

Summary

In this application note, the eGaN IC EPC2112 was introduced and evaluated in a 300 kHz hardswitching SEPIC suitable for a low voltage DC-DC application, such as a post regulator for wireless power receivers. The integrated gate driver yields similar performance compared to discrete gate driver and in some cases superior performance. The EPC2112 eGaN IC simplifies the design and board thus reducing cost and design time without compromising on performance compared to a discrete solution.

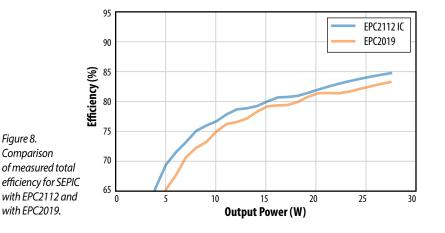


Figure 8.

References:

- A. Lidow, J. Strydom, M. de Rooij, D. Reusch, *GaN Transistors for Efficient Power Conversion*. Second Edition, Wiley, ISBN 978-1-118-84476-2.
- [2] Efficient Power Conversion Corporation, "Enhancement Mode Power Transistor," EPC2107 datasheet, Jul. 2015 [Online] Available: http://epc-co com/epc/documents/datasheets/EPC2107_datasheet.pdf
- [3] Efficient Power Conversion Corporation, "200 V, 10 A Integrated Driver GaN FET," EPC2112 datasheet, March 2018, [Online] Available: http://epc-co.com/ epc/documents/datasheets/EPC2112_datasheet.pdf
- [4] J. Falin, "Designing DC/DC converters based on SEPIC topology," Analog Applications Journal Texas Instruments, 2008, pp 18 – 23.
- [5] R. Ridley, "Analyzing the Sepic Converter," Power Systems Design Europe, November 2006, pp 14 – 18.
- [6] W. Gu, "Designing A SEPIC Converter," National Semiconductor Application Note 1484, June 2007.
- [7] LM3481 datasheet, Texas Instruments, [Online] Available: http://www.ti.com lit/ds/symlink/lm3481.pdf

eGaN® IC is a registered trademark of Efficient Power Conversion Corporation.

- [8] D. Adar, G. Rahav and S. Ben-Yaakov, "A Unified Behavioral Average Model of SEPIC Converters with Coupled Inductors," Record of the 28th Annual IEEE Power Electronics Specialists Conference (PESC), June 1997, Vol. 1, pp 441-446.
- J. Falin, "TPS61175 SEPIC Design," Texas Instruments Application Report, SLVA337, January 2010, [Online] Available: http://www.ti.com/lit/an/slva337 slva337.pdf
- [10] UCC27611 datasheet, Texas Instruments, [Online] Available: http://www.ti.com/lit/ds/symlink/ucc27611.pdf
- [11] Efficient Power Conversion, "EPC2019 Enhancement Mode Power Transistor," EPC2019 datasheet, June 2014 [Revised September 2015], [Online] Available: http://epc-co.com/epc/Products/eGaNFETs/EPC2019.aspx

EPC – EFFICIENT POWER CONVERSION CORPORATION | WWW.EPC-CO.COM | COPYRIGHT 2018