




The eGaN[®] FET
Journey Continues


GaN: Raising the Bar for Power Conversion Performance

David Reusch and Johan Strydom

Efficient Power Conversion Corporation

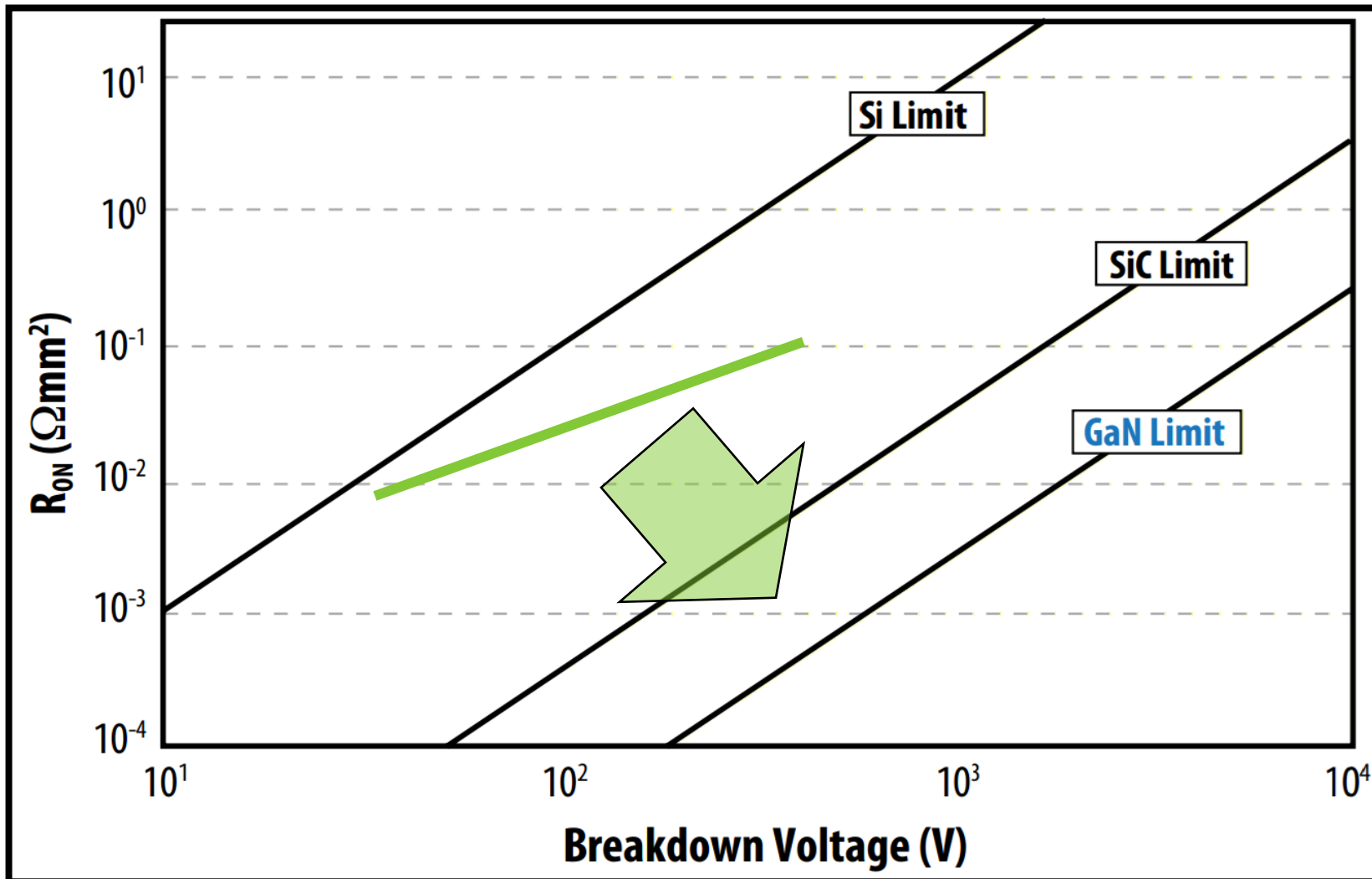
- **Why GaN?**
- **What have we learned?**
- **Higher current applications**
- **Higher frequency applications**
- **Summary**



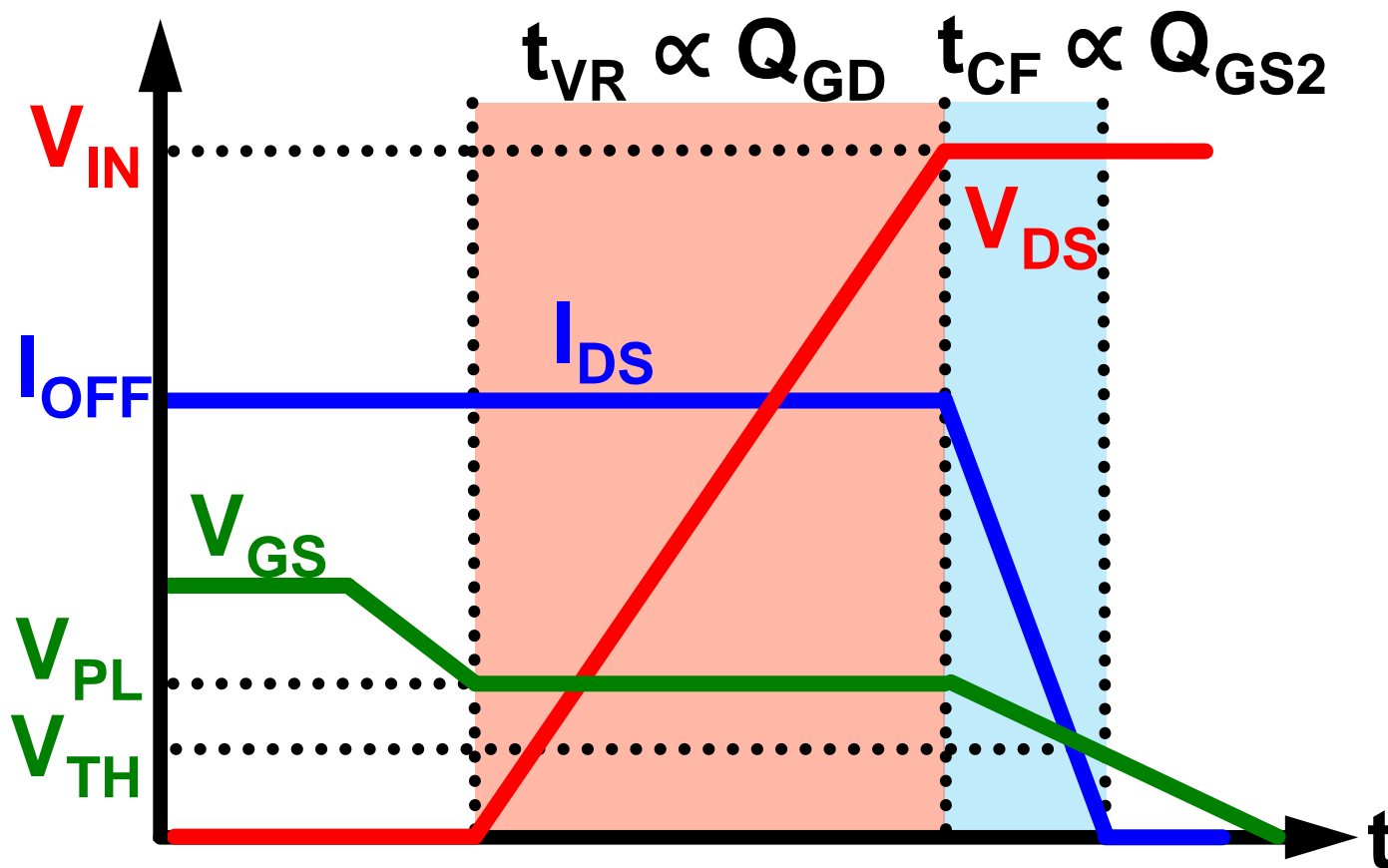


$$P_{t_{VR}} \approx \frac{V_{IN} * I_{OFF} * Q_{GD}}{2 * I_G}$$



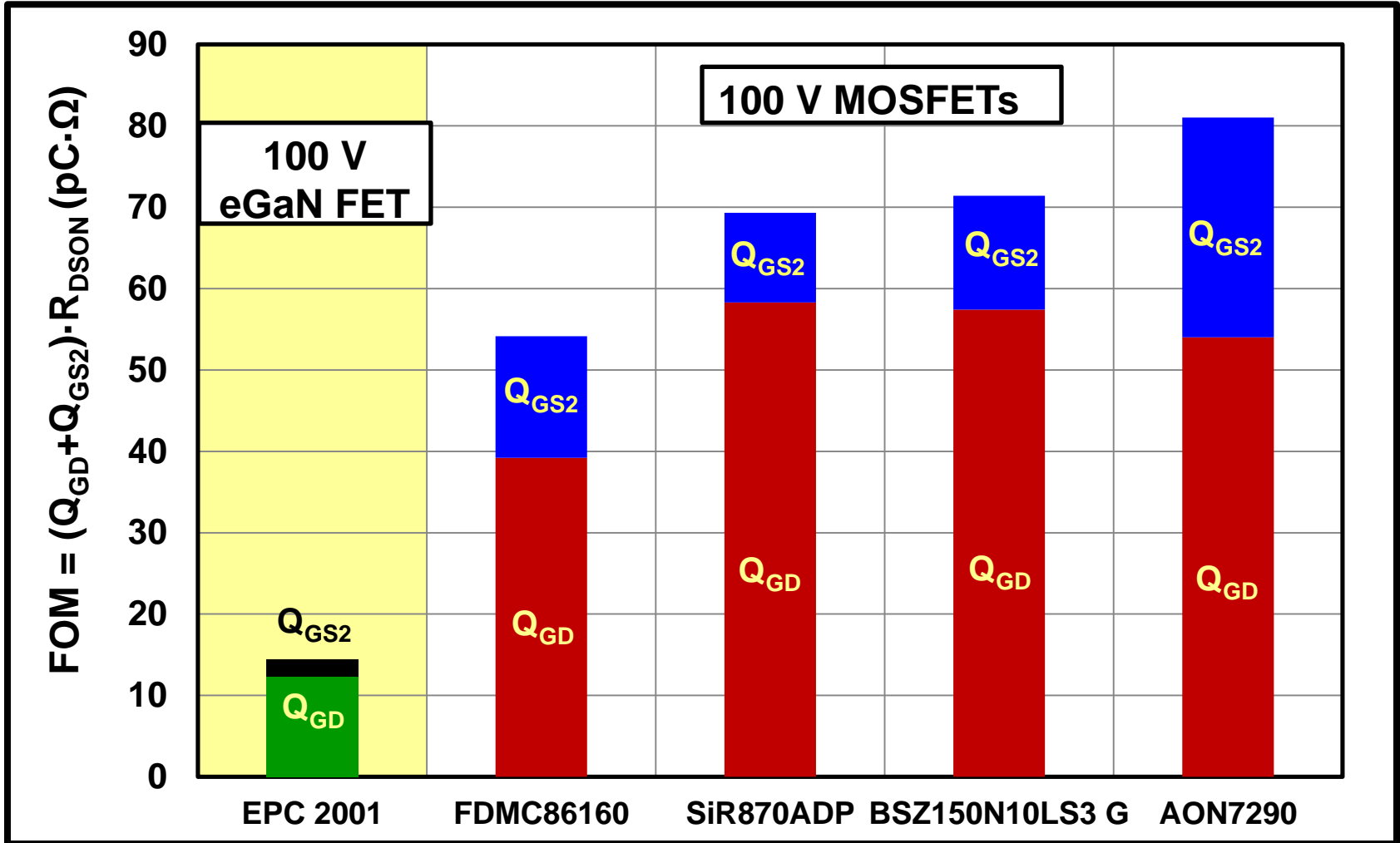
$$P_{t_{CF}} \approx \frac{V_{IN} * I_{OFF} * Q_{GS2}}{2 * I_G}$$




$$V_{DS}=0.5*V_{DS}, I_{DS}= 10 A$$

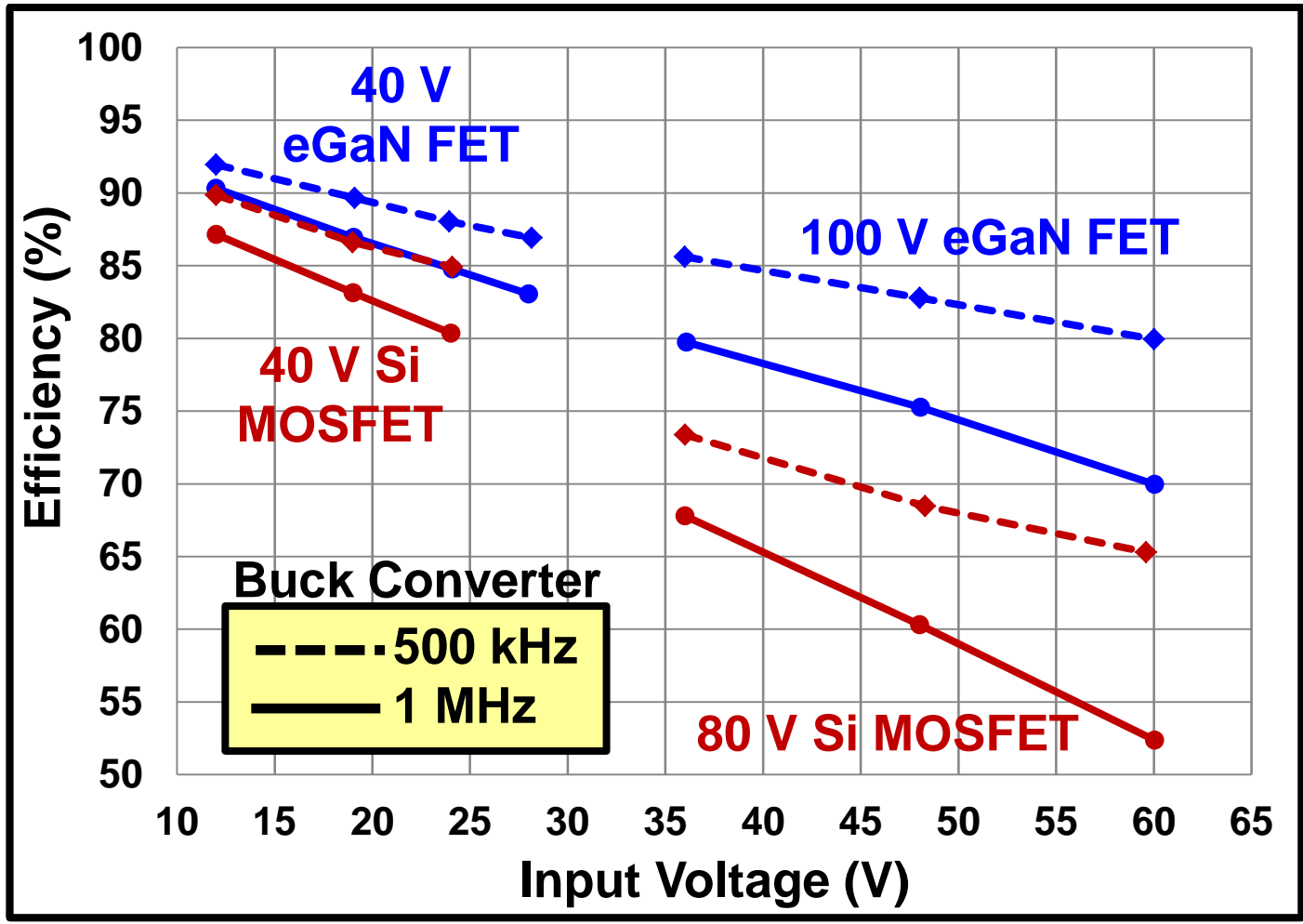

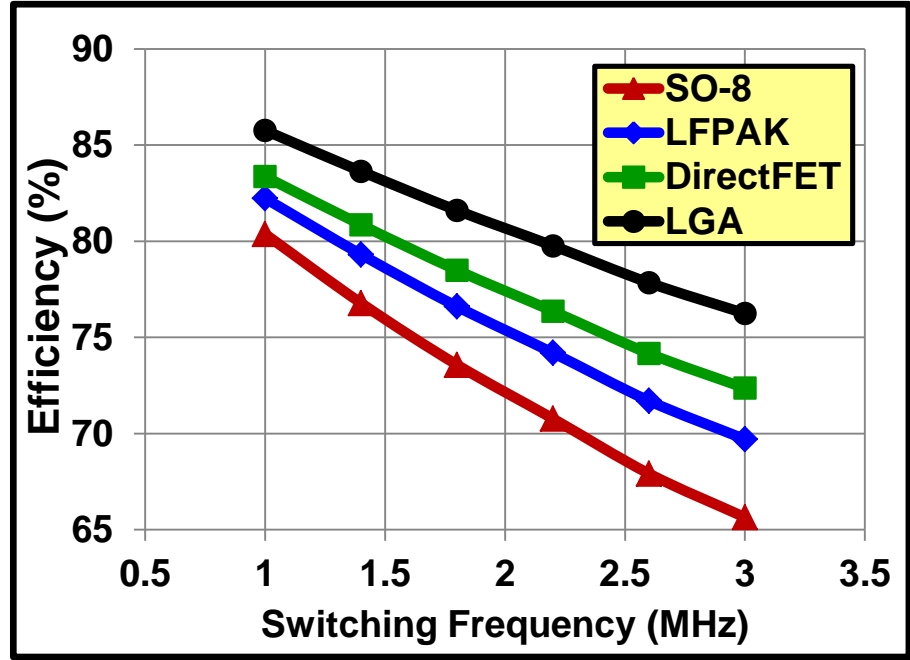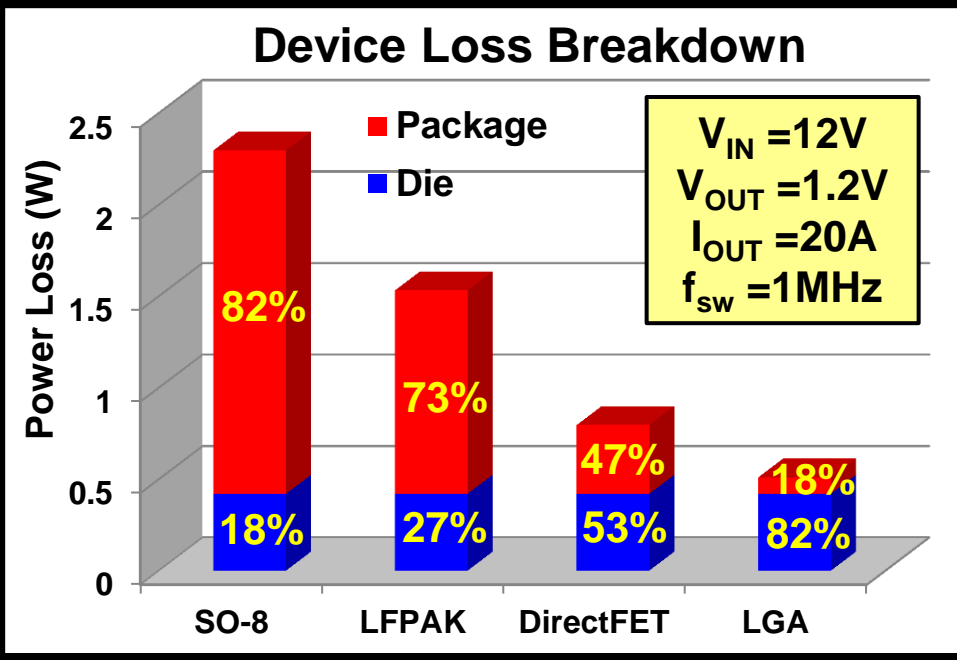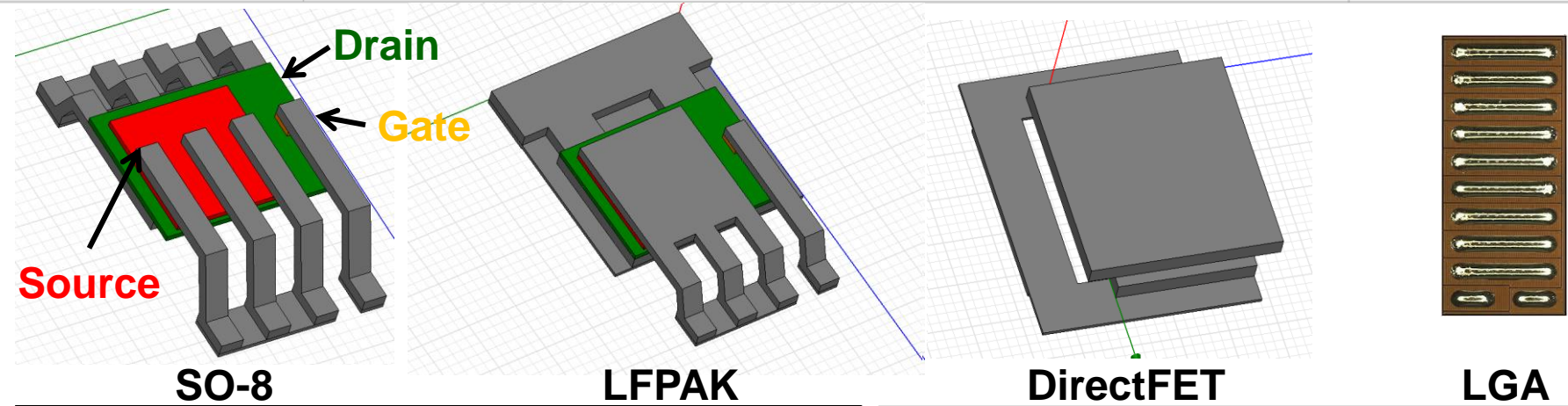Measured Efficiency $V_{OUT}=1.2\text{ V}$ $I_{OUT}=10\text{ A}$




Measured Efficiency

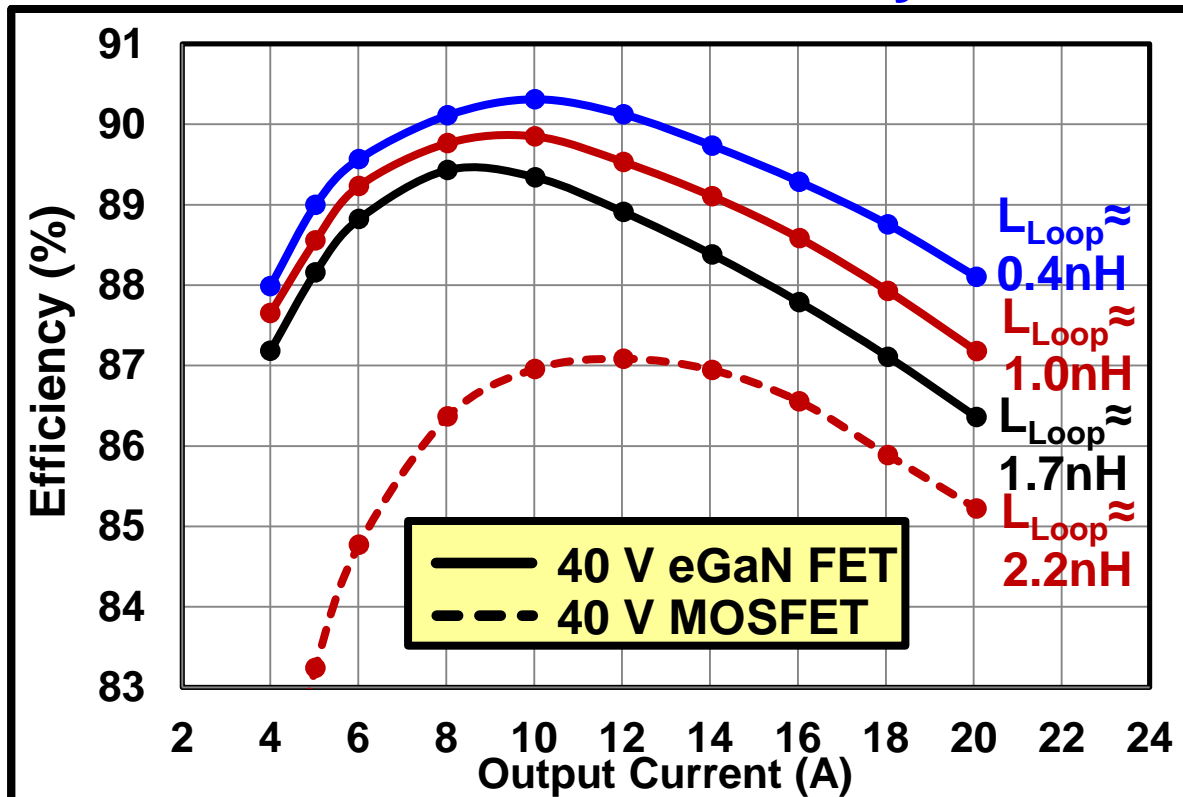


$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$, $f_{sw}=1\text{ MHz}$, $L=300\text{ nH}$


EPC Optimal Layout

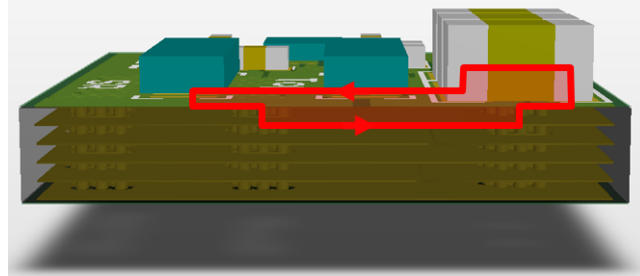

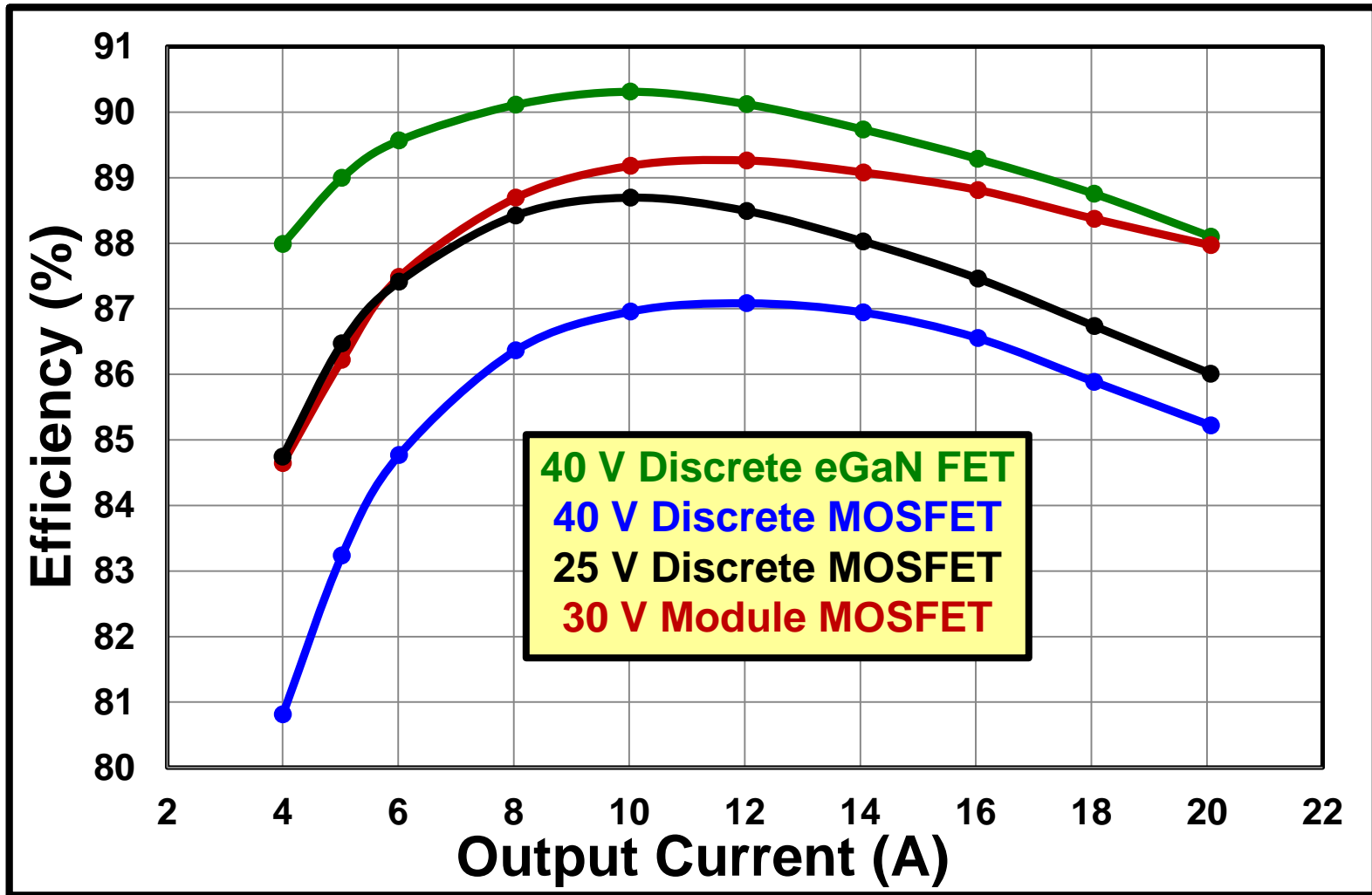
Ref: D. Reusch, J. Strydom,
 "Understanding the Effect of PCB Layout
 on Circuit Performance in a High
 Frequency Gallium Nitride Based Point of
 Load Converter," APEC 2013



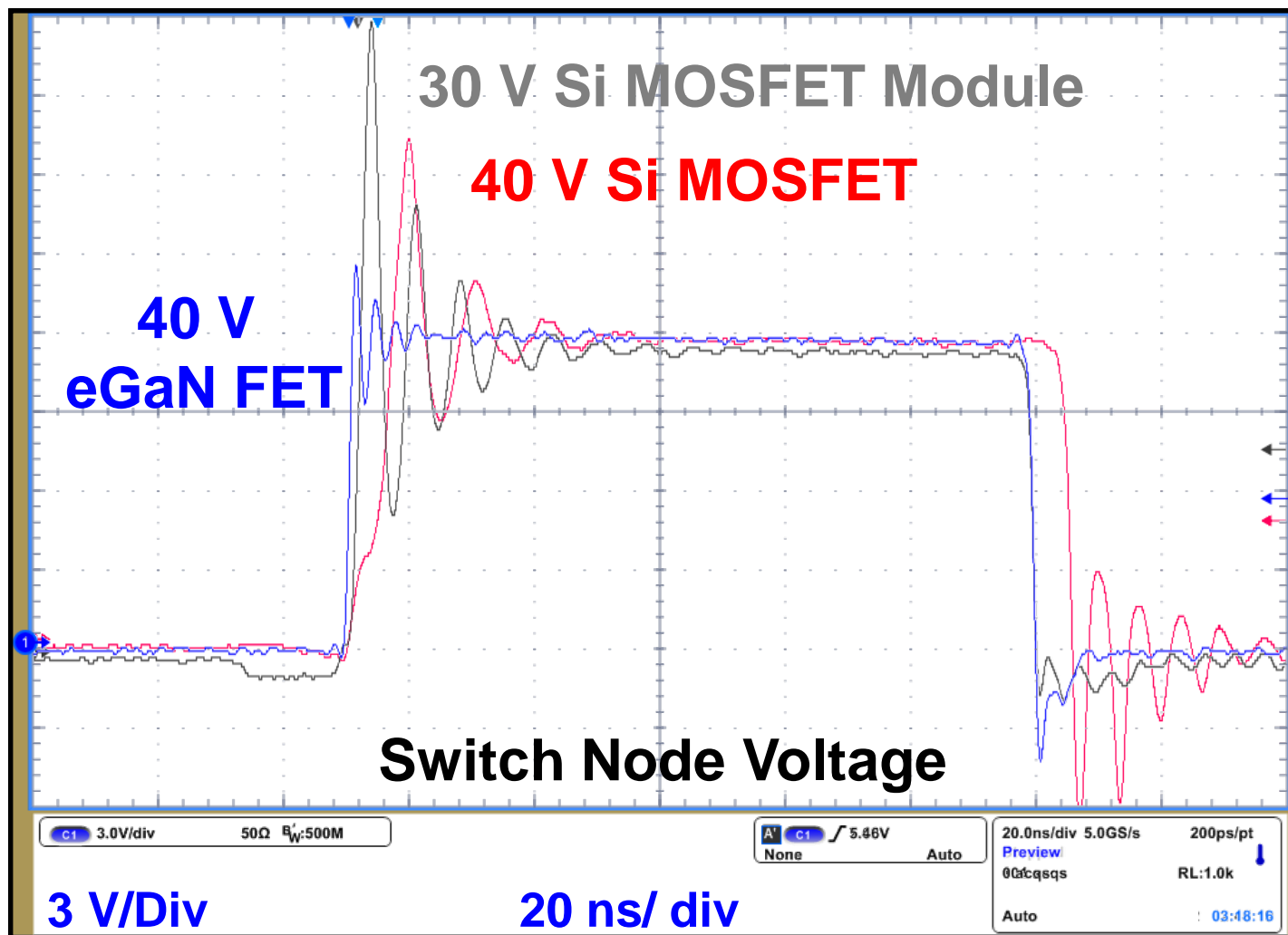$V_{IN}=12\text{ V}$ $V_{OUT}=1.2\text{ V}$ $f_{sw}=1\text{ MHz}$ $L=300\text{ nH}$



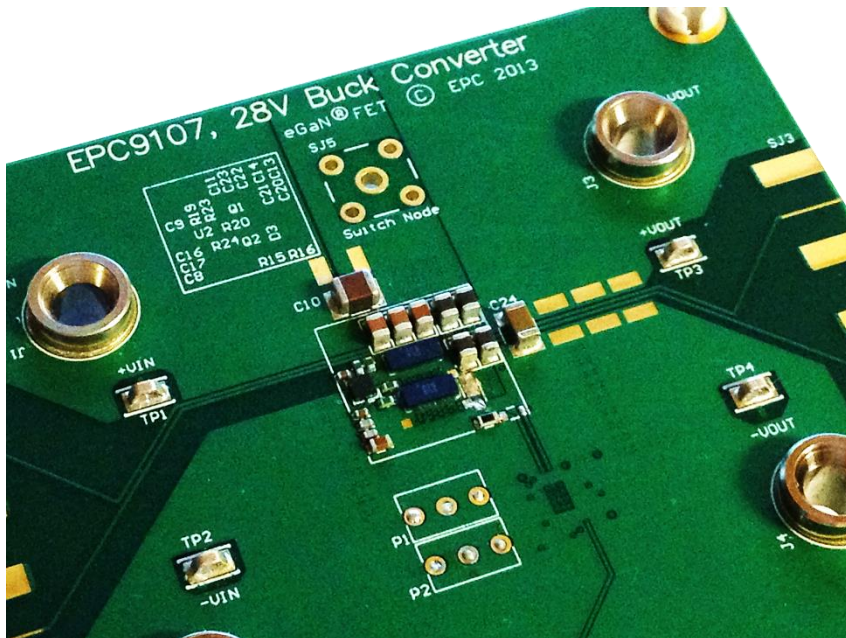
$V_{IN}=12\text{ V}$ $V_{OUT}=1.2\text{ V}$ $I_{OUT}=20\text{ A}$ $f_{sw}=1\text{ MHz}$ $L=300\text{ nH}$





$V_{IN}=12-28\text{ V}$ $V_{OUT}=3.3\text{ V}$
 $I_{OUT}=15\text{ A}$ $f_{sw}=1\text{ MHz}$
2 x EPC2015

EPC9107 Switching Node Voltage


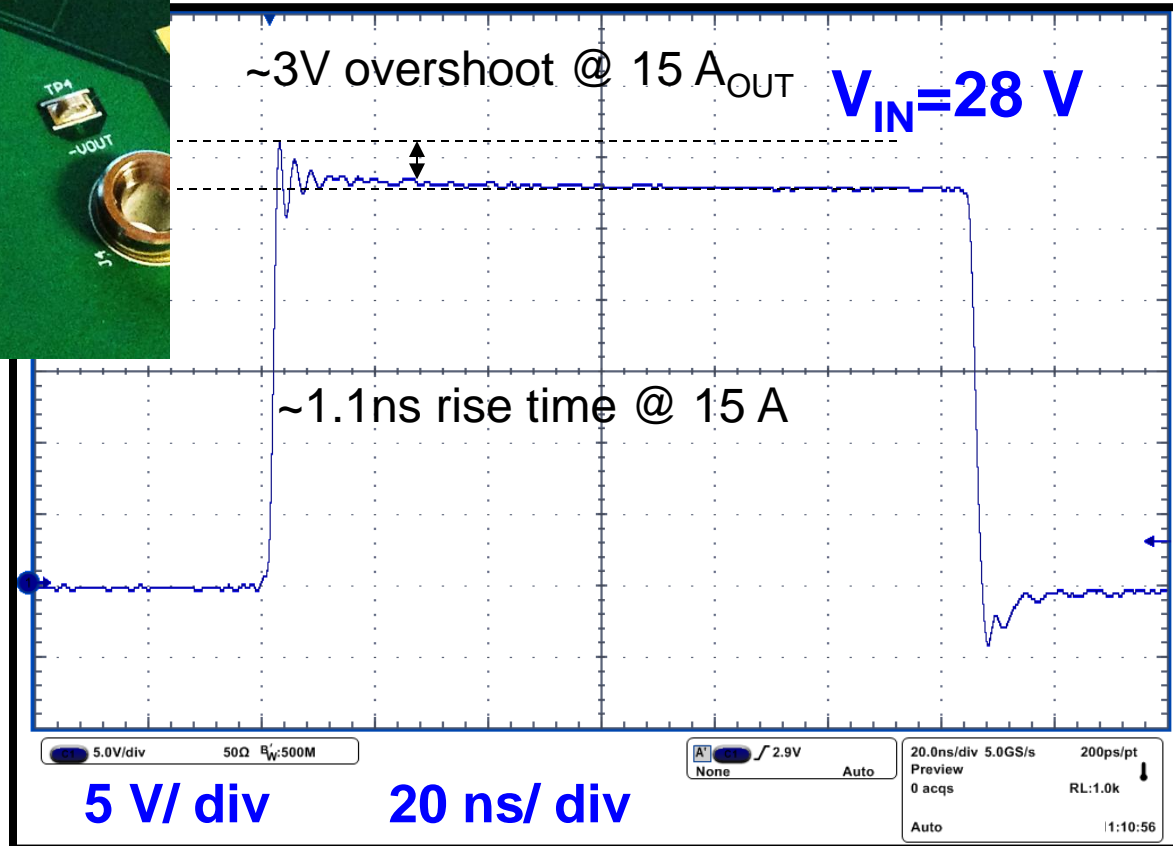
$V_{IN}=28\text{ V}$ $I_{OUT}=15\text{ A}$



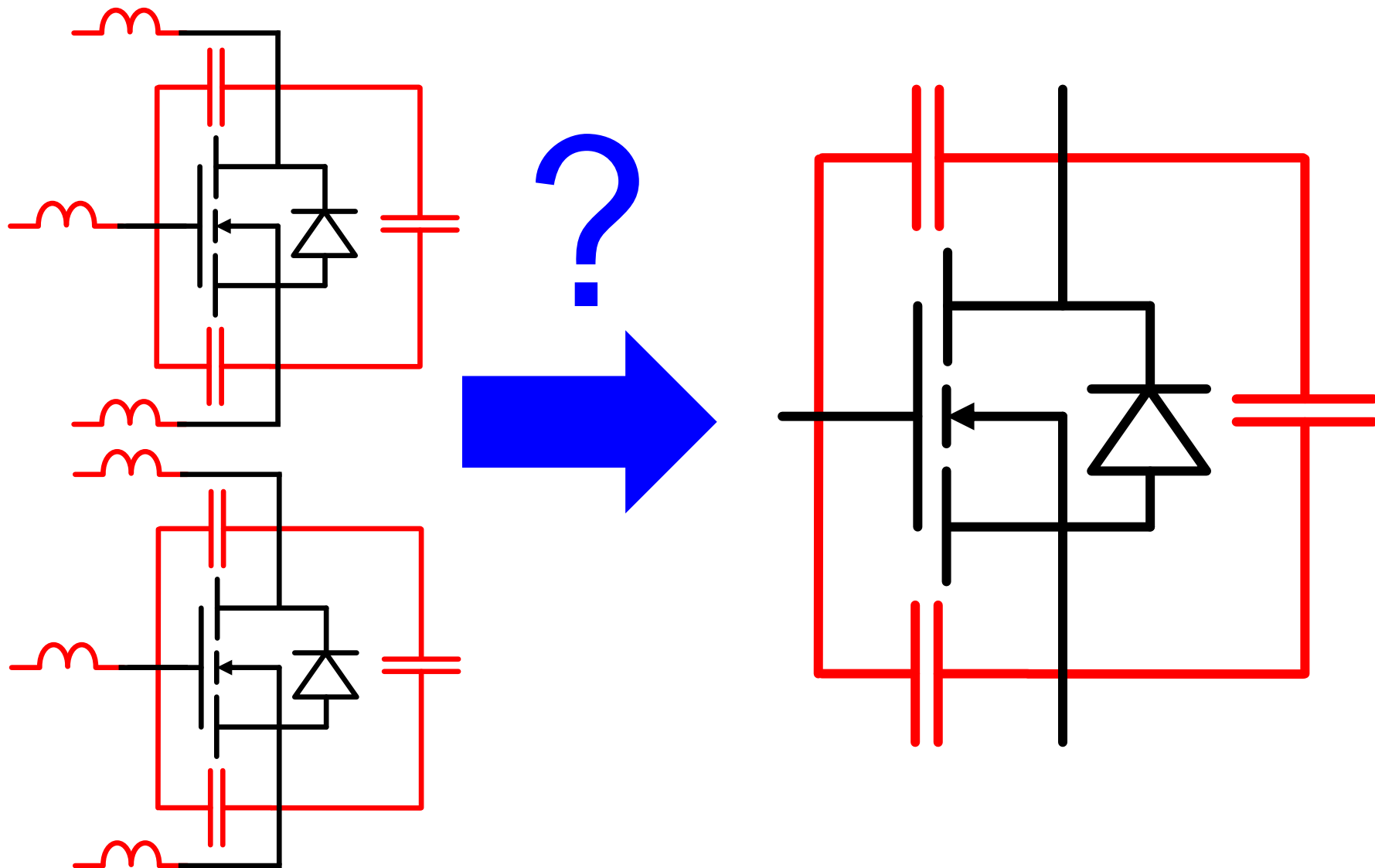


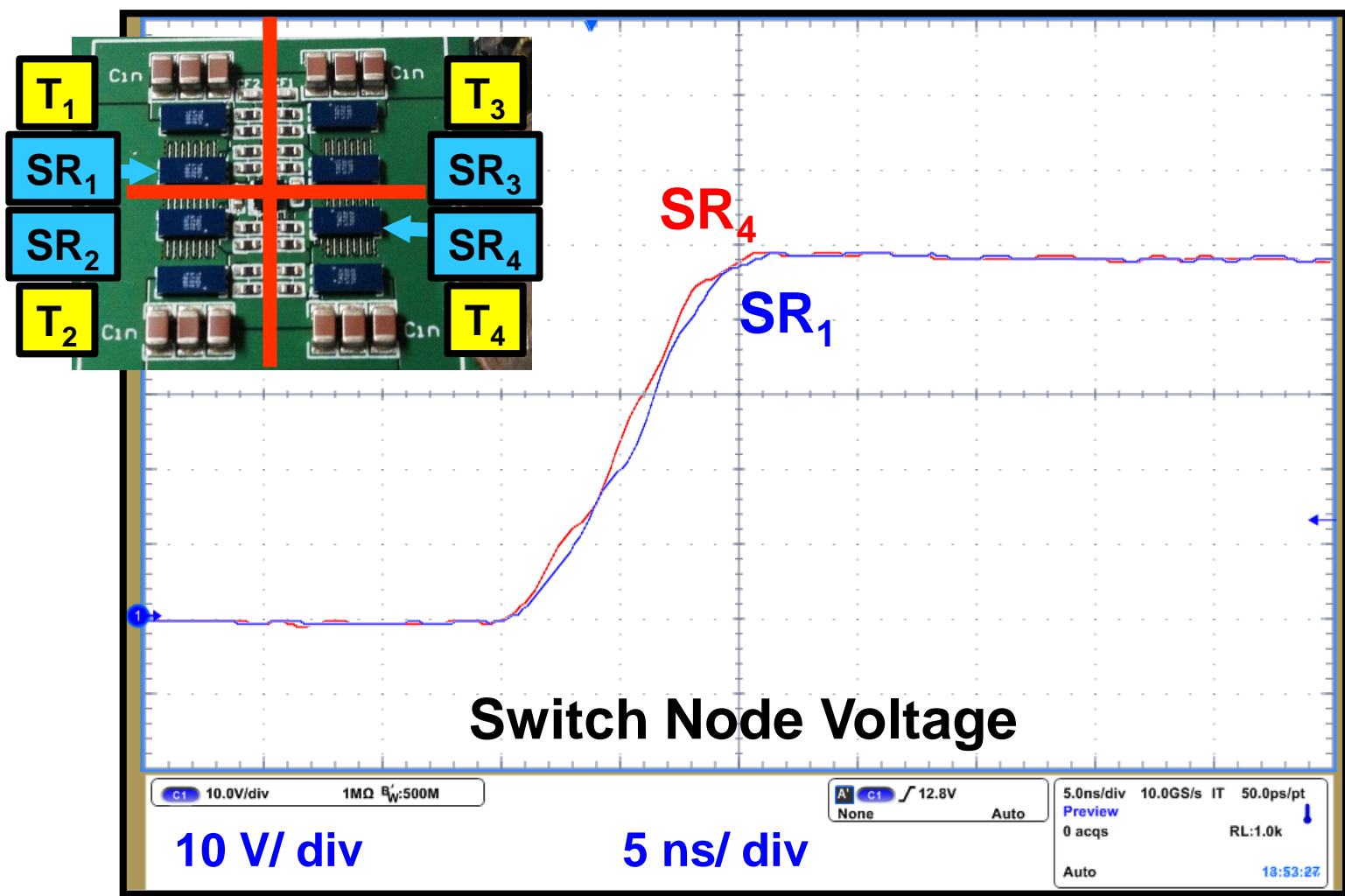

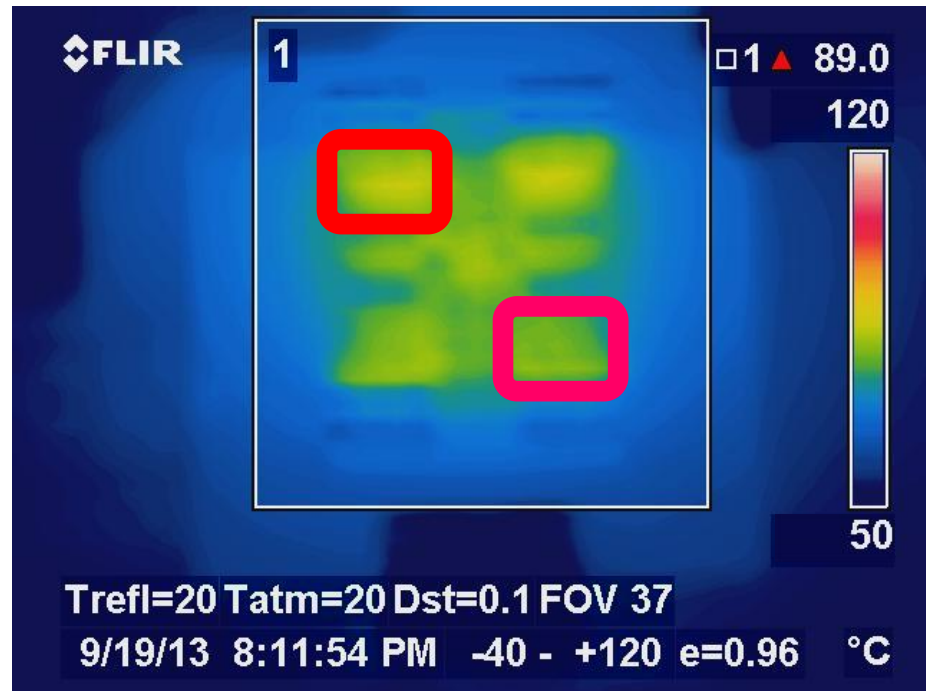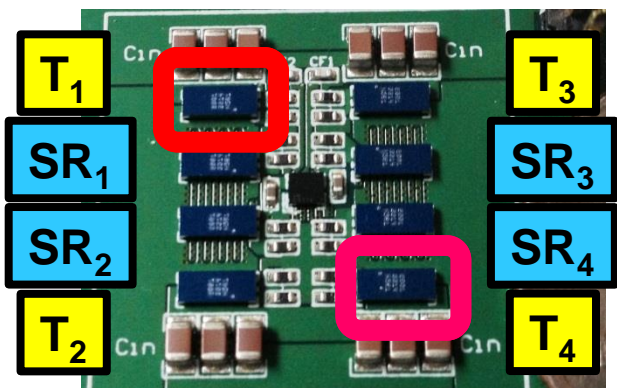
$V_{IN}=48\text{ V}$ $V_{OUT}=12\text{ V}$ $I_{OUT}=30\text{ A}$ $f_{sw}=300\text{ kHz}$ $L=3.3\text{ }\mu\text{H}$ GaN FET T/SR: 100 V EPC2001



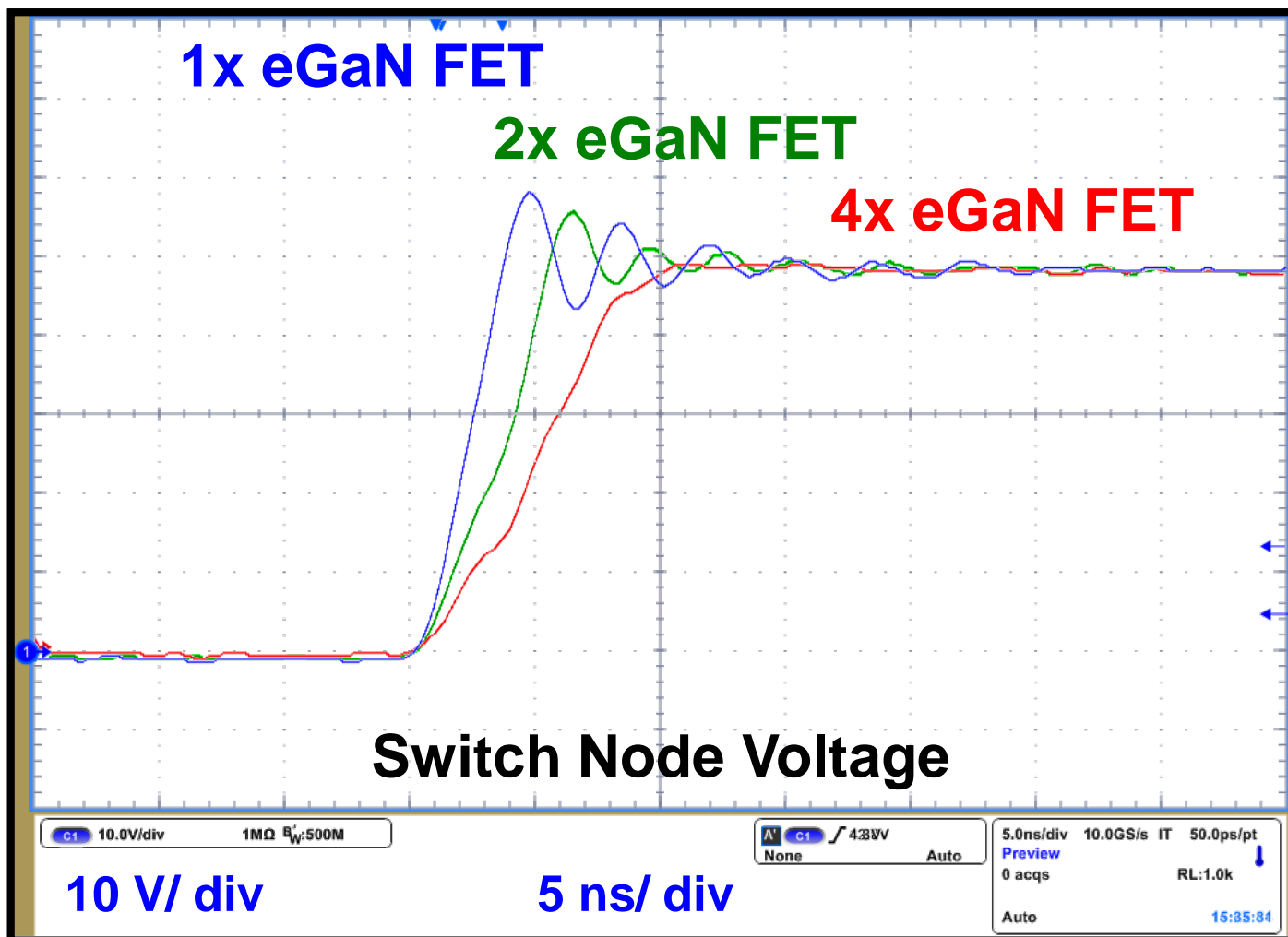
$V_{IN}=48\text{ V}$ $V_{OUT}=12\text{ V}$ $I_{OUT}=30\text{ A}$ $f_{sw}=300\text{ kHz}$ $L=3.3\text{ }\mu\text{H}$ Fan Speed=200 LFM
 GaN FET T/SR: 100 V EPC2001




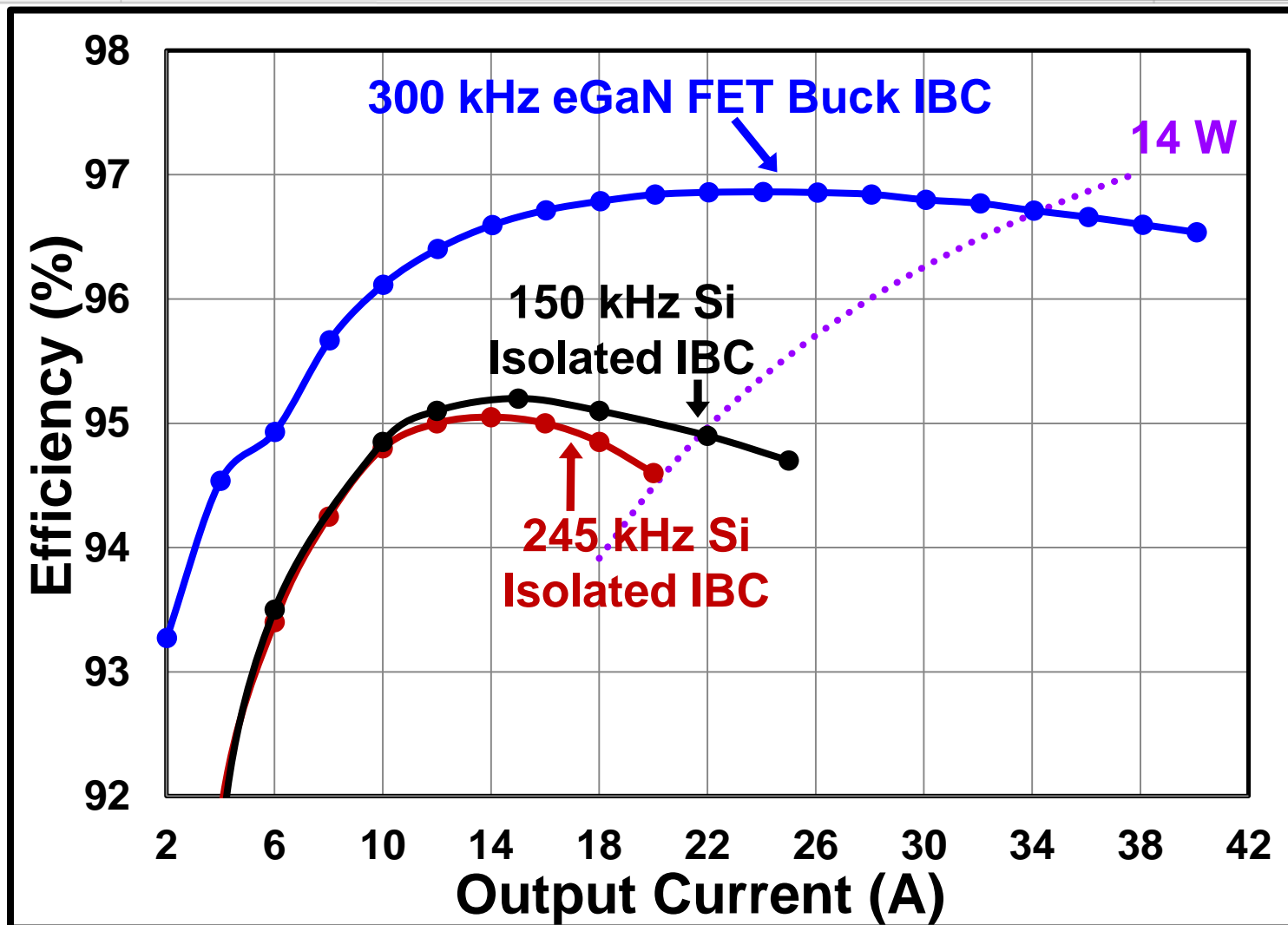$V_{IN}=48\text{ V}$ $V_{OUT}=12\text{ V}$ $I_{OUT}=30\text{ A}$ / number of devices $f_{sw}=300\text{ kHz}$ GaN FET T/SR: 100 V EPC2001



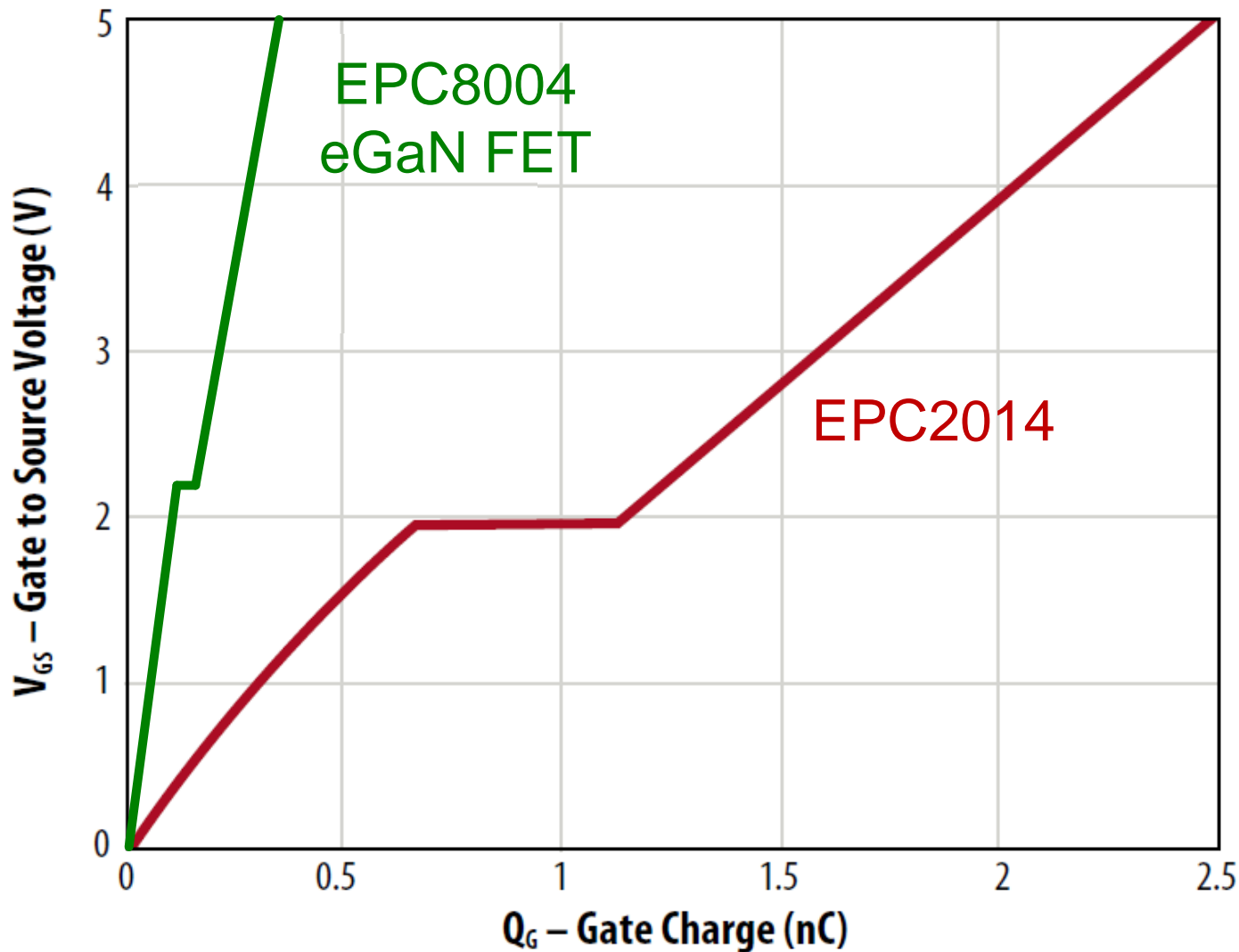$V_{IN}=48\text{ V}$ $V_{OUT}=12\text{ V}$ Fully Regulated IBC



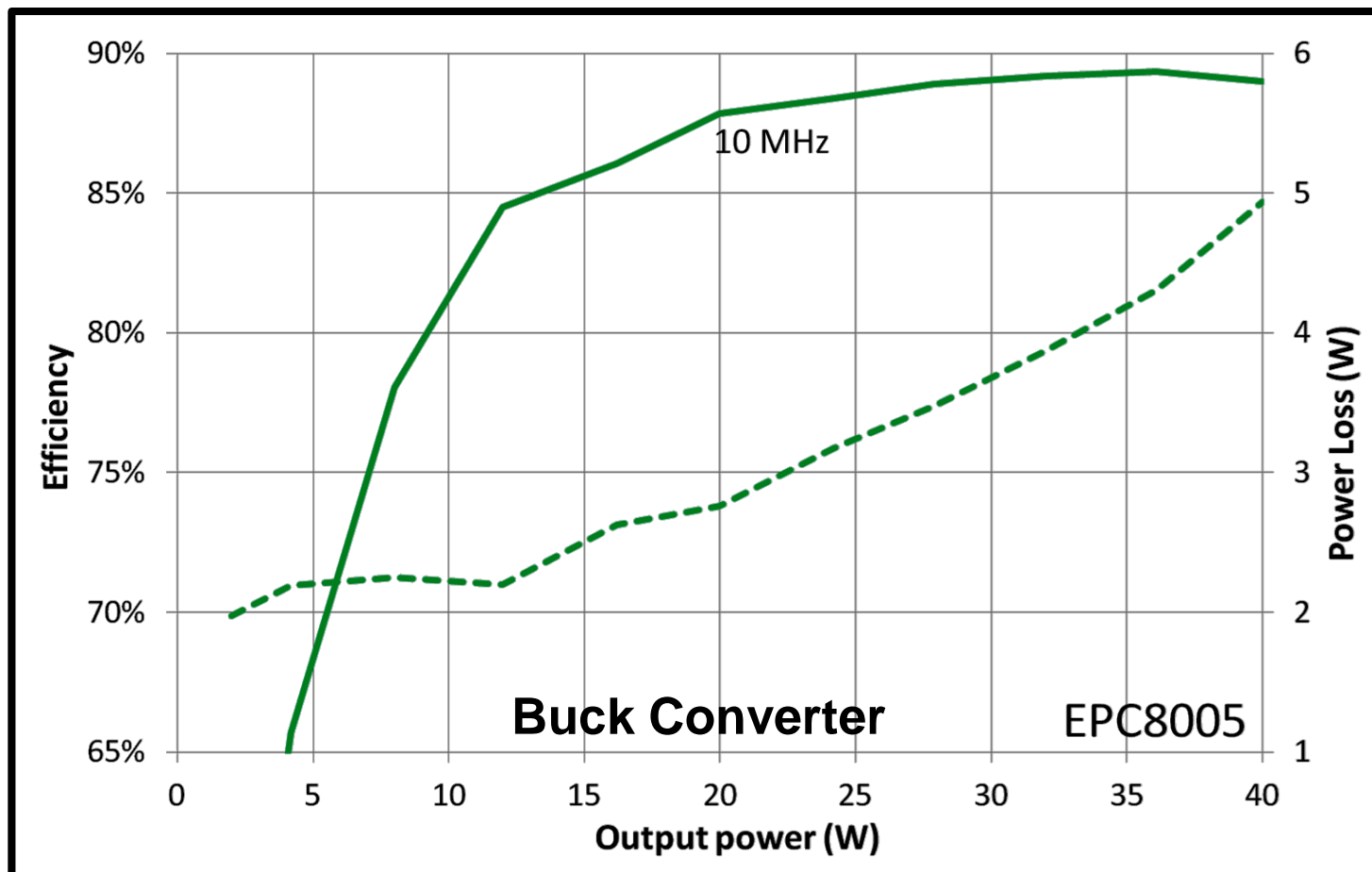


$V_{IN}=42\text{ V}$ $V_{OUT}=20\text{ V}$ $f_{sw}=10\text{ MHz}$ eGaN FET T/SR: EPC8005

See High Frequency Talk Today in Session T30!


Ultra High Frequency Family
1 - 3 GHz

Launched Sept 2013

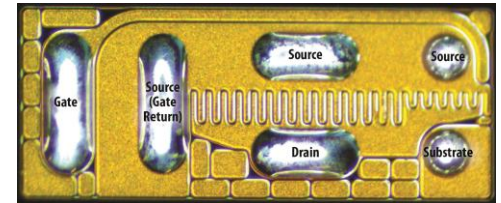


Mass Production
40 V - 200 V
~500 MHz

Higher Current
45 A

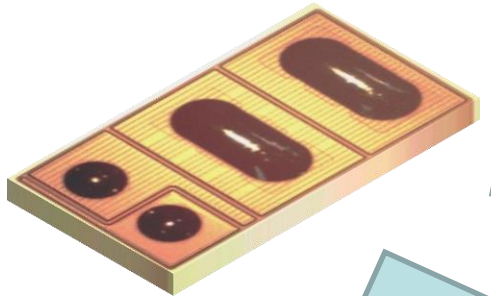

Higher Voltage
600 V

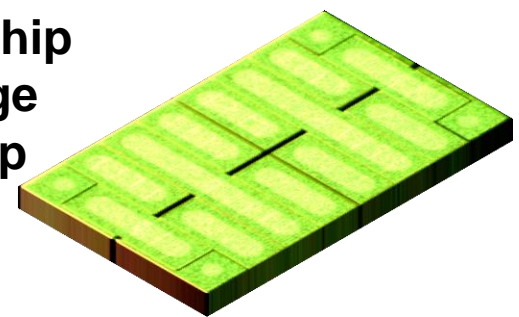More functions on a chip
Monolithic half bridge
Driver on power chip



Next Generation Devices
2 x FOM Improvement

eGaN FETs continue to raise the bar for power conversion performance

- **Better FOM's**
- **Better Packaging**
- **Improved PCB Layout Techniques**
 - **Better In-Circuit Performance**
 - **Good Parallel Performance**
- **Higher Frequency Devices**

Thank You For Your Time ! Questions?



*The end of the road
for silicon.....*

*is the beginning of
the eGaN FET
journey!*