



The eGaN® FET
Journey Continues

National Taiwan University

Emerging Applications for GaN Transistors

Alex Lidow

Efficient Power Conversion Corporation

November 2012



Agenda



- Why Gallium Nitride?
- Hard Switched Converters
 - Envelope Tracking
- High Frequency Resonant Converters
 - Wireless Power
- Summary




Why Gallium Nitride?



- Enhancement-Mode devices available (eGaN® FETs)
- $R_{DS(ON)}$ per unit area much smaller than silicon power MOSFET
- Much faster switching
- Very low capacitance (C_G , C_{ISS} , C_{OSS})
- No parasitic PN junction body ($Q_{RR}=0$)




eGaN® FET Structure

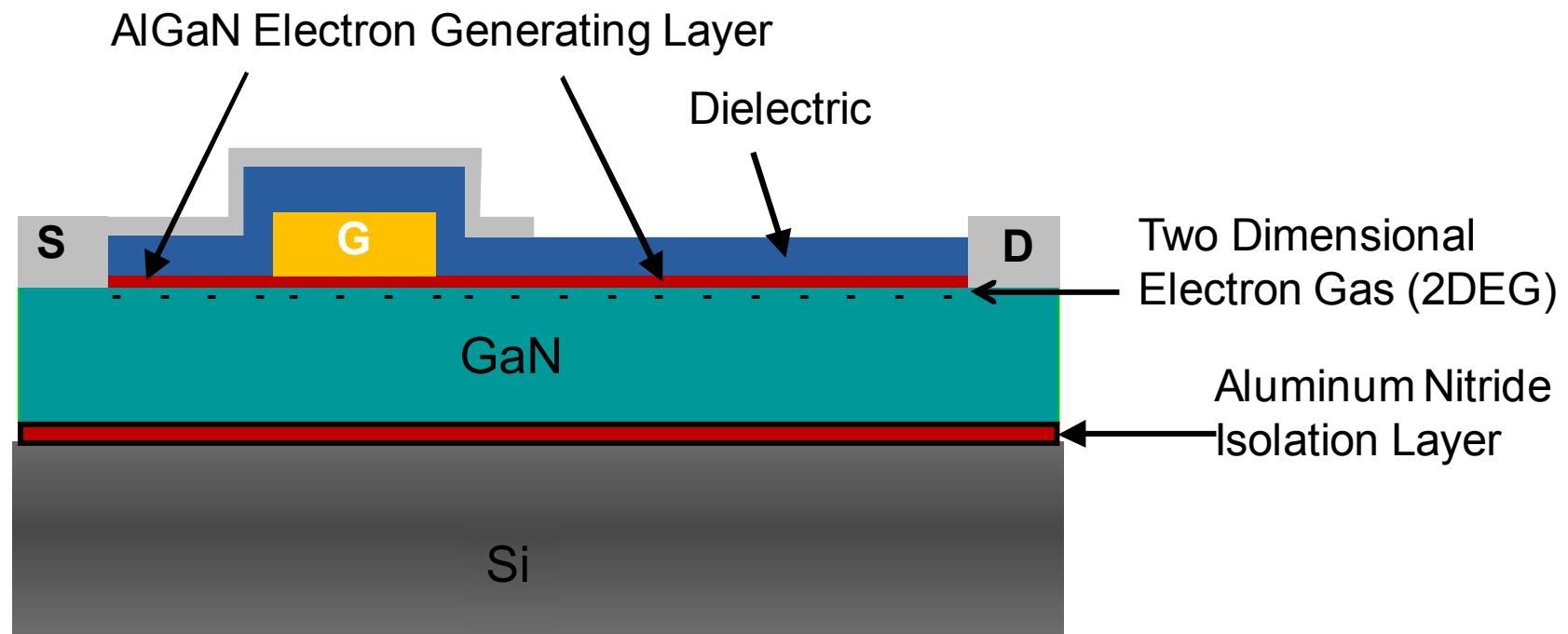

4.



Flip Chip Assembly



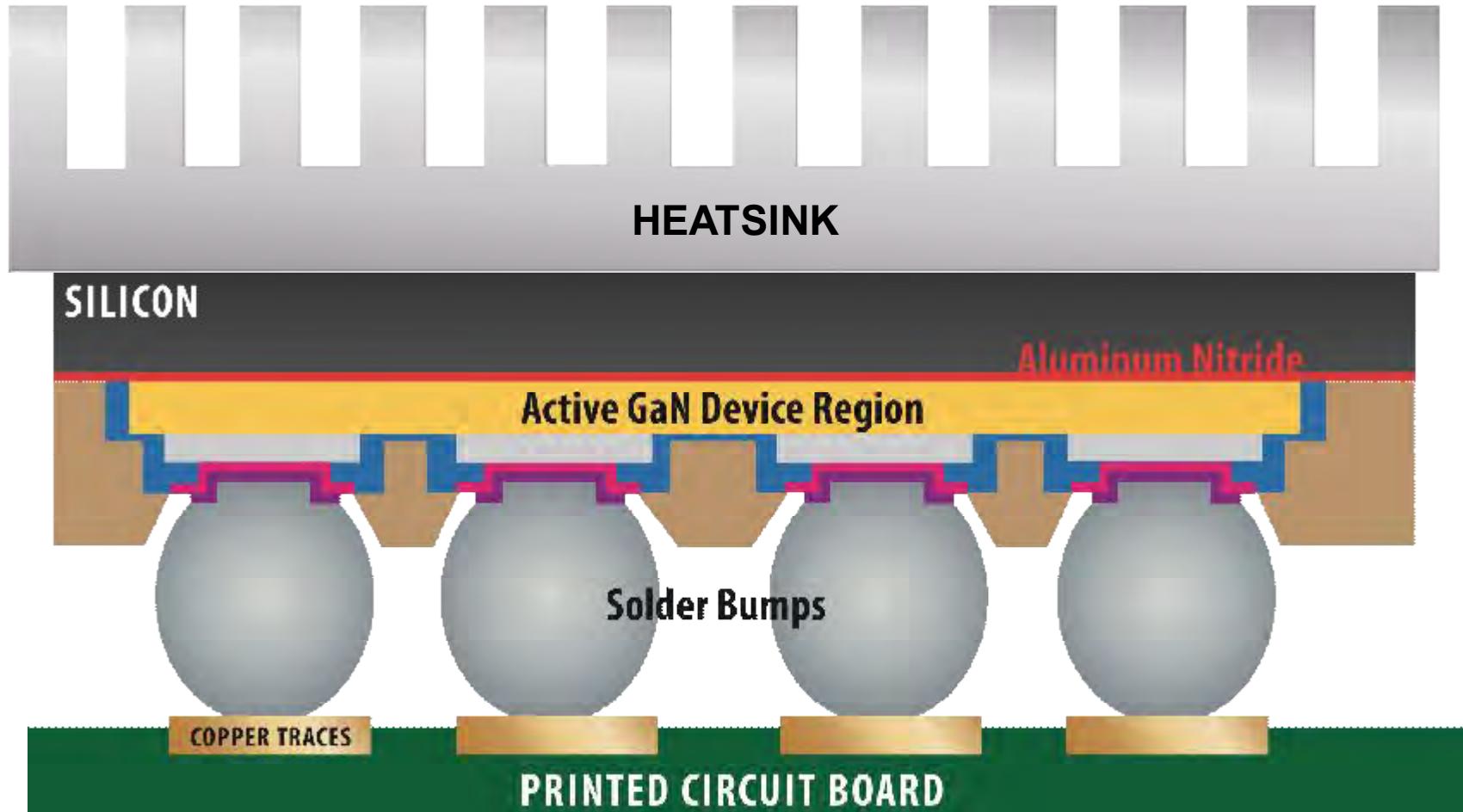




Hard Switched Converters




Example: Buck Converter

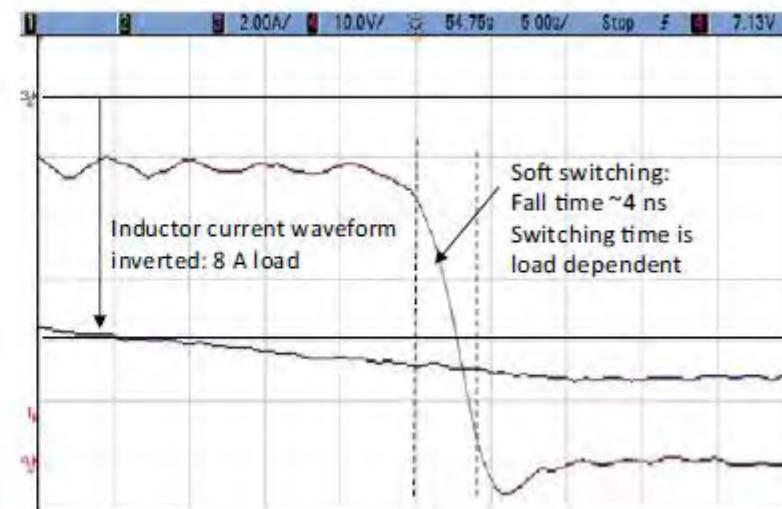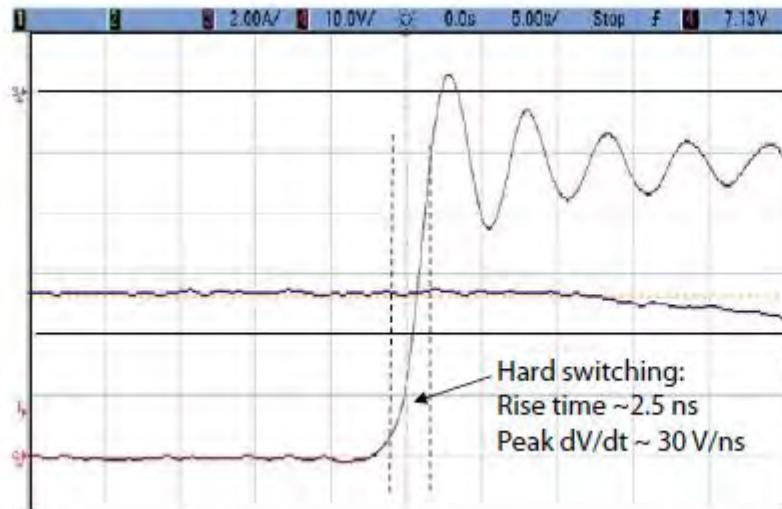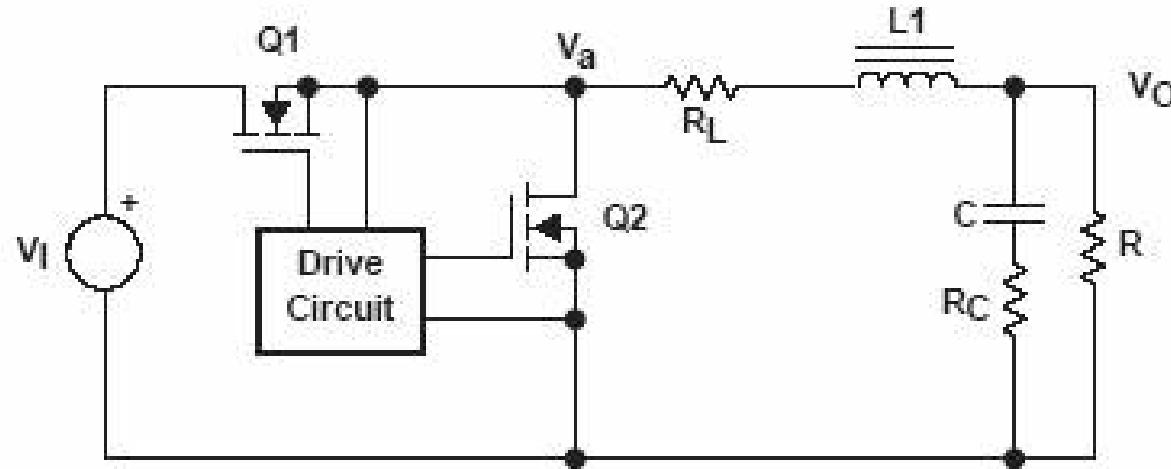




Buck Converter Parasitics

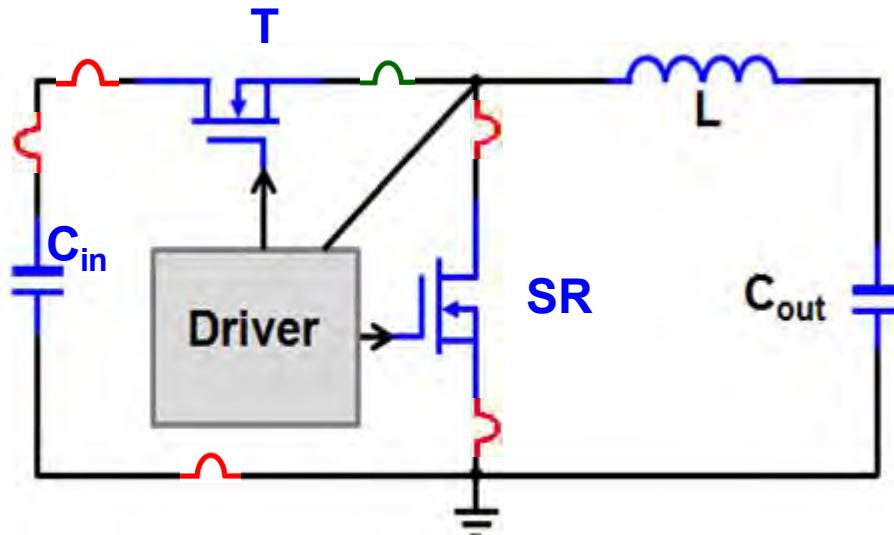

L_S : Common Source Inductance



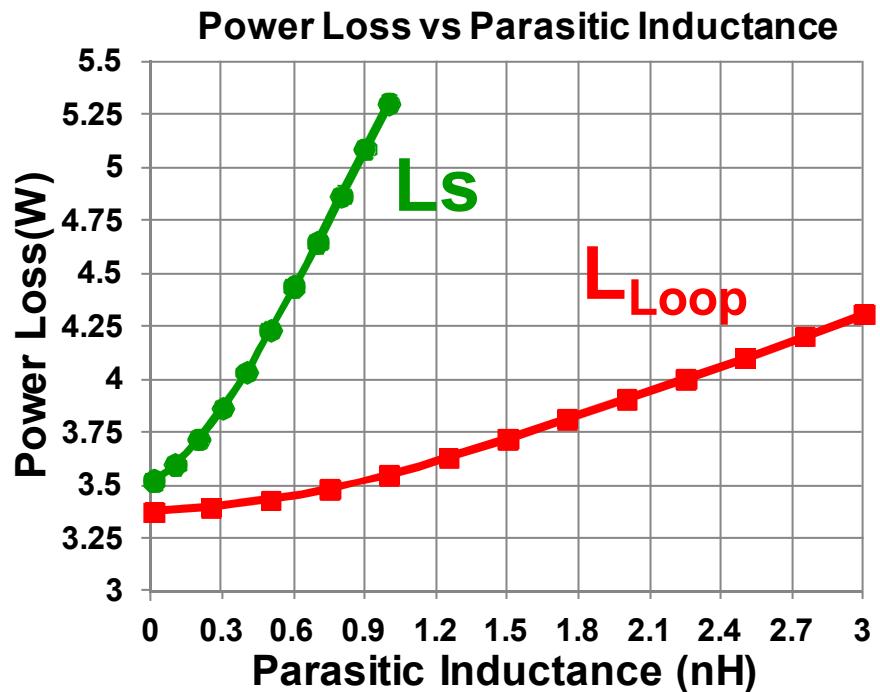
L_{Loop} : High Frequency Power Loop Inductance



$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$,
 $F_s=1\text{ MHz}$, $I_{OUT}=20\text{ A}$



Packaging Evolution

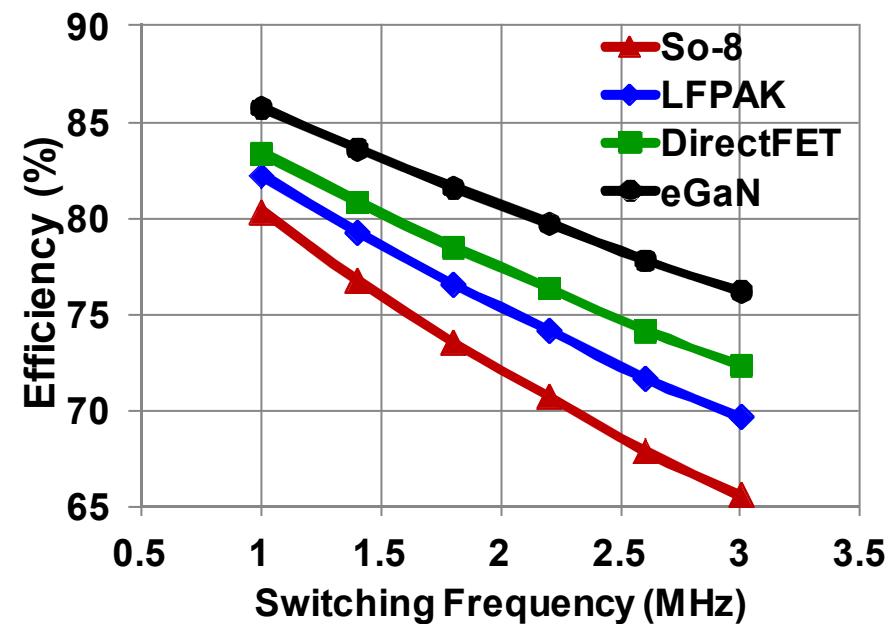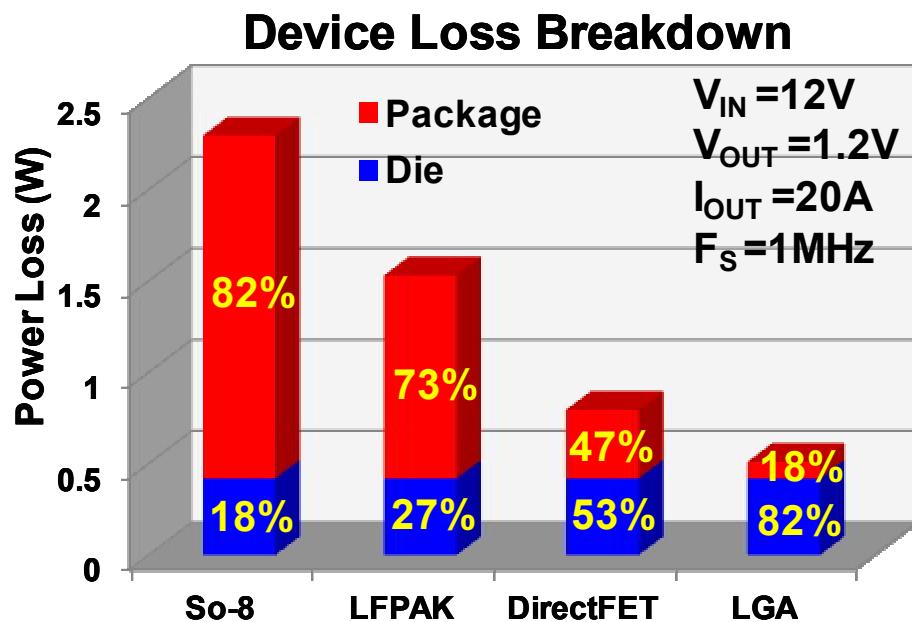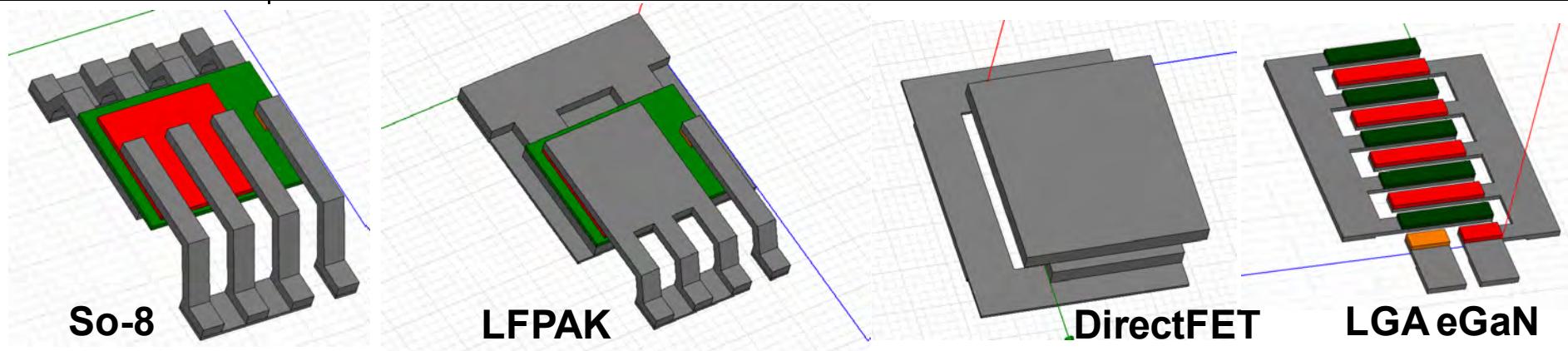




Layout Impact on Efficiency




Experimental Efficiency

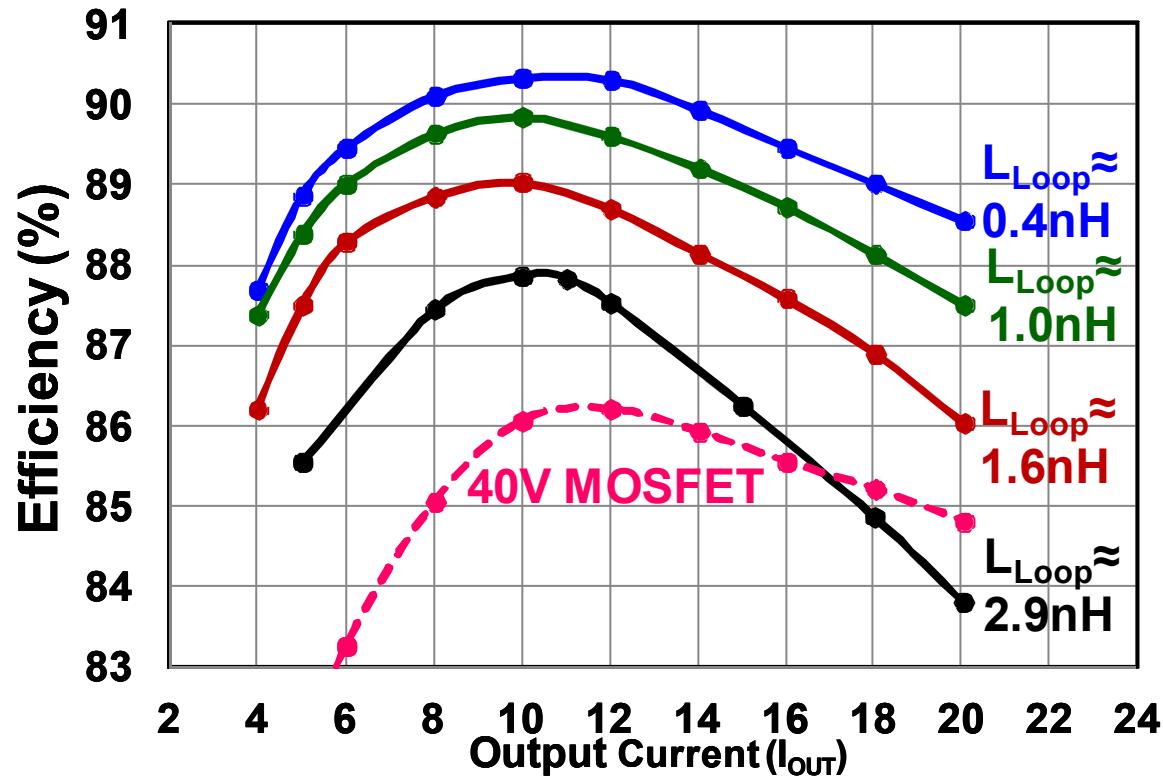

$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$,
 $F_S=1\text{ MHz}$, $L=150\text{ nH}$



Peak Voltage Comparison

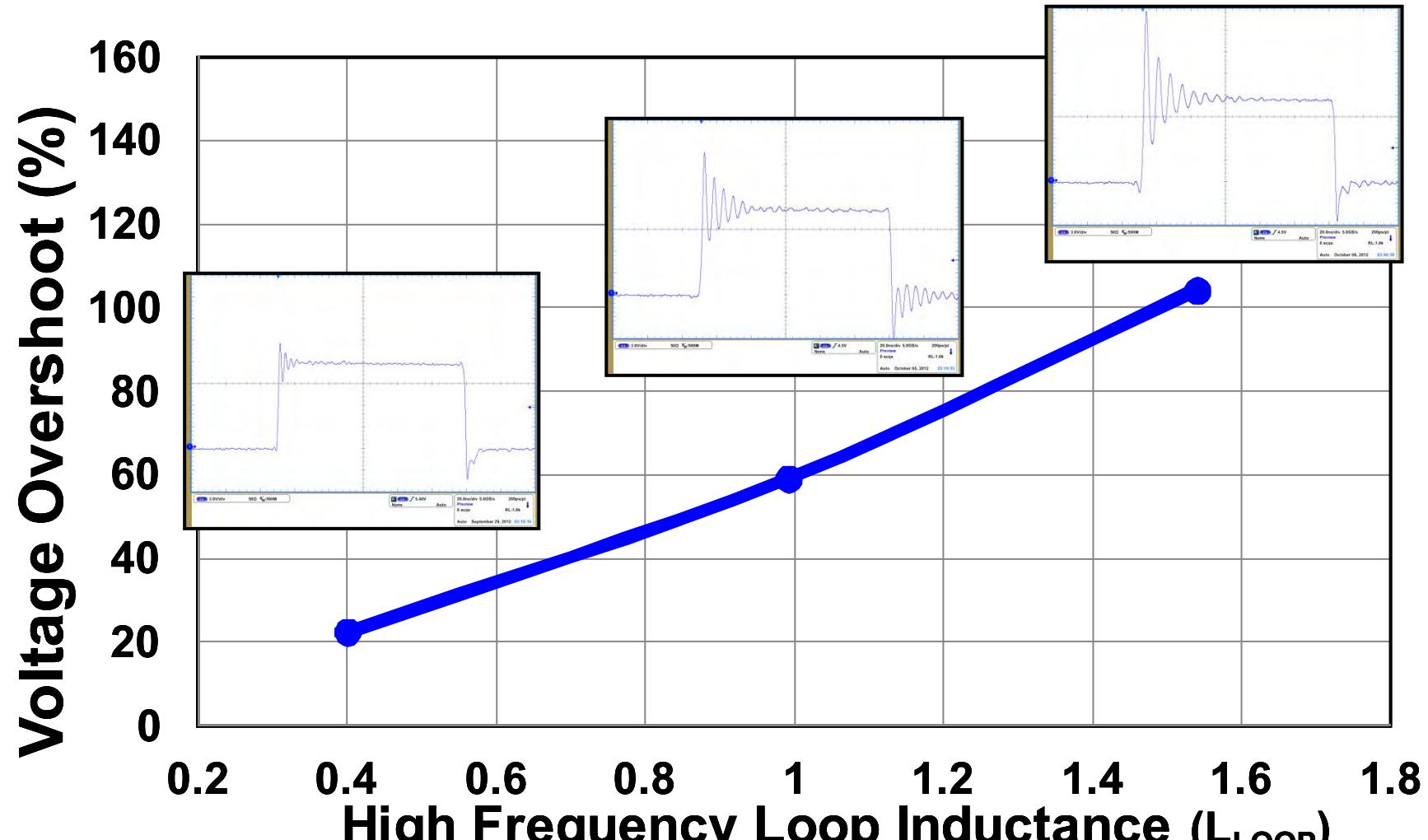



$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$, $F_s=1\text{ MHz}$, $L=150\text{ nH}$



Envelope Tracking




RF Transmission

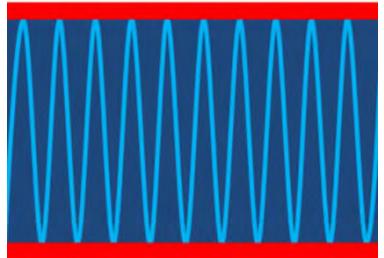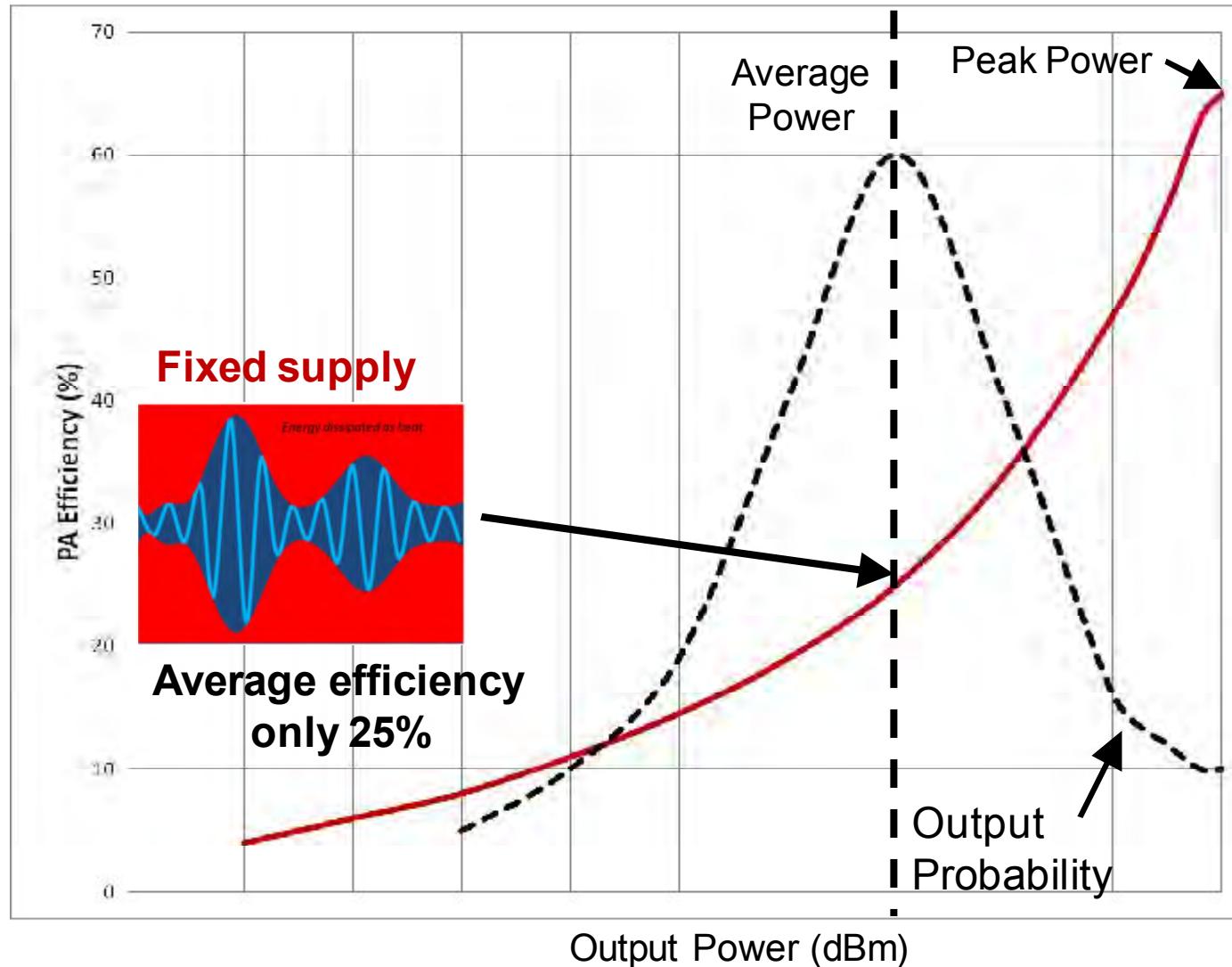

**Peak efficiency
up to 65%**




Effect of ET

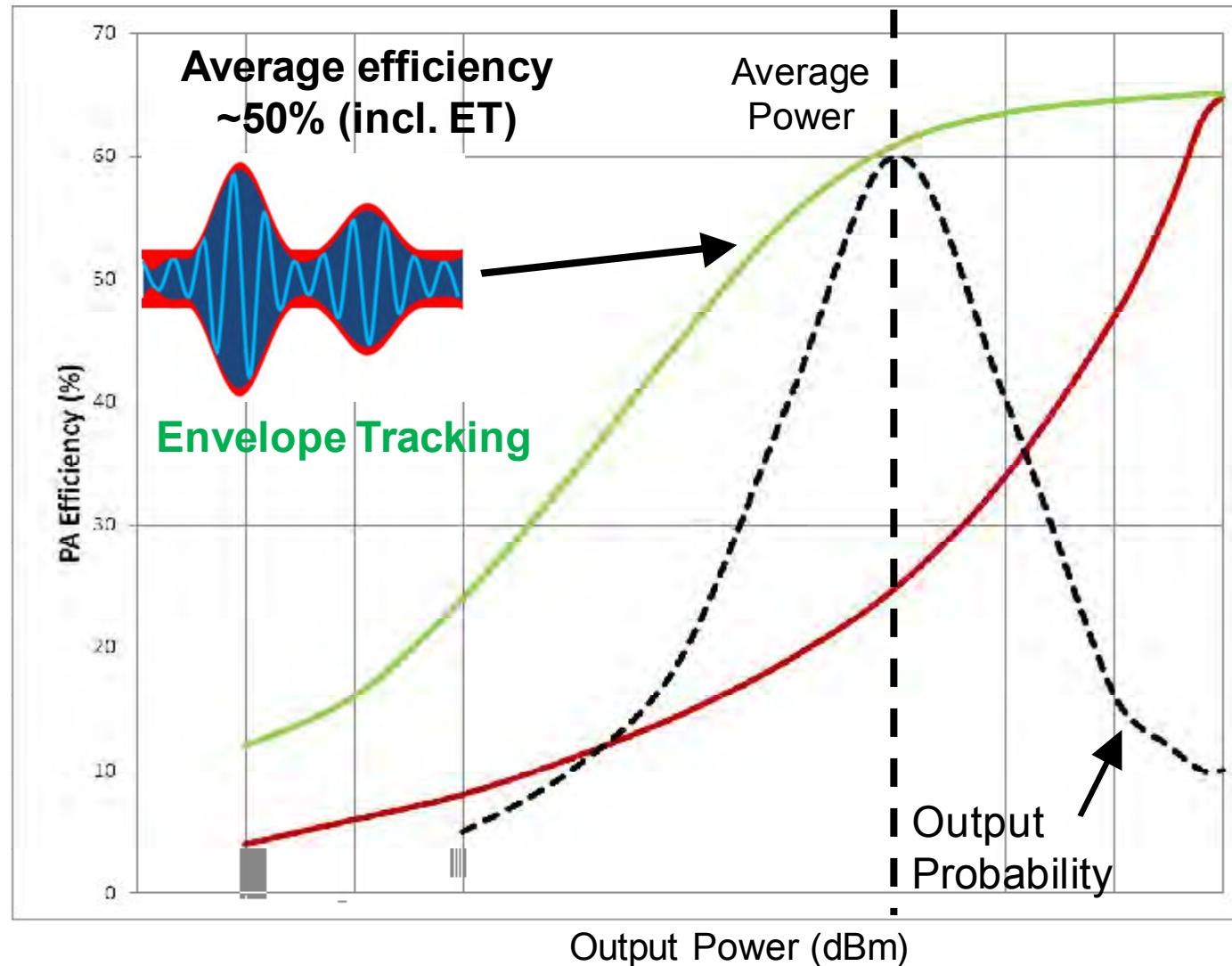




Linear-Assisted Buck ET

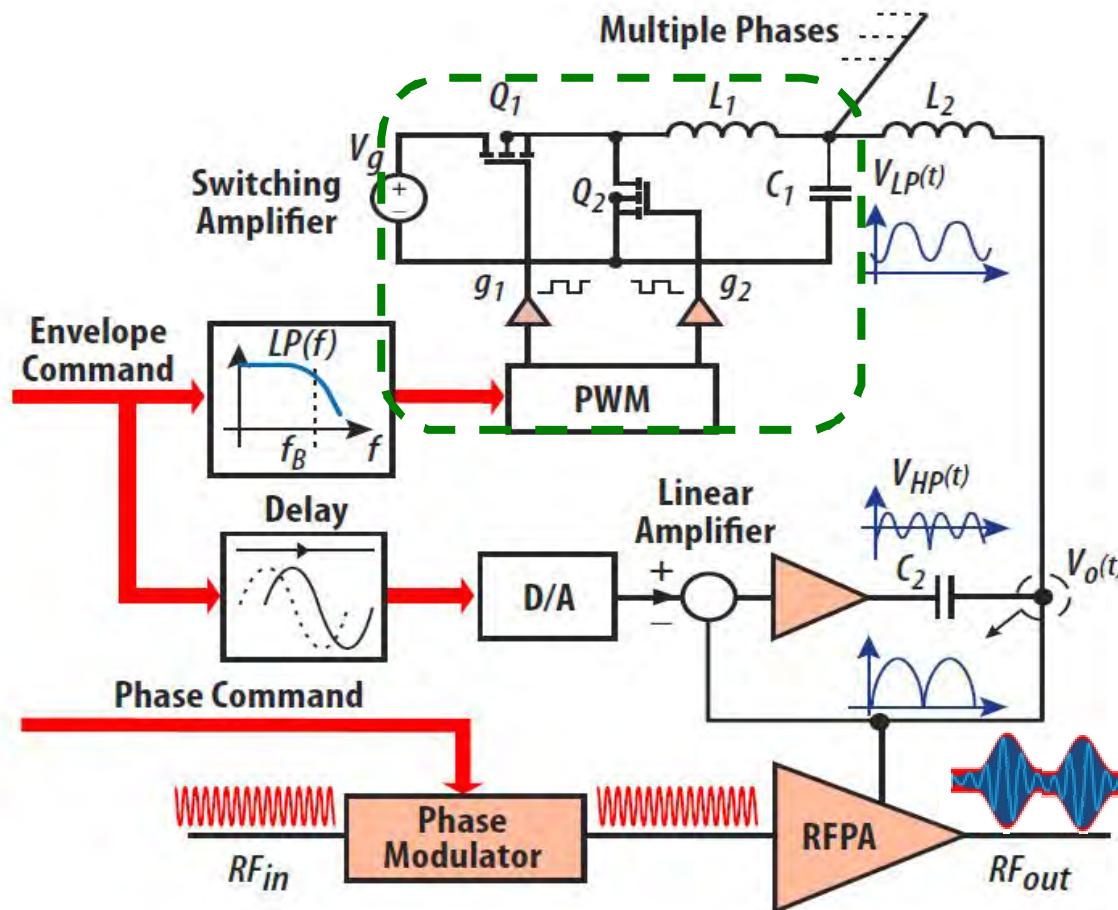




Efficiency

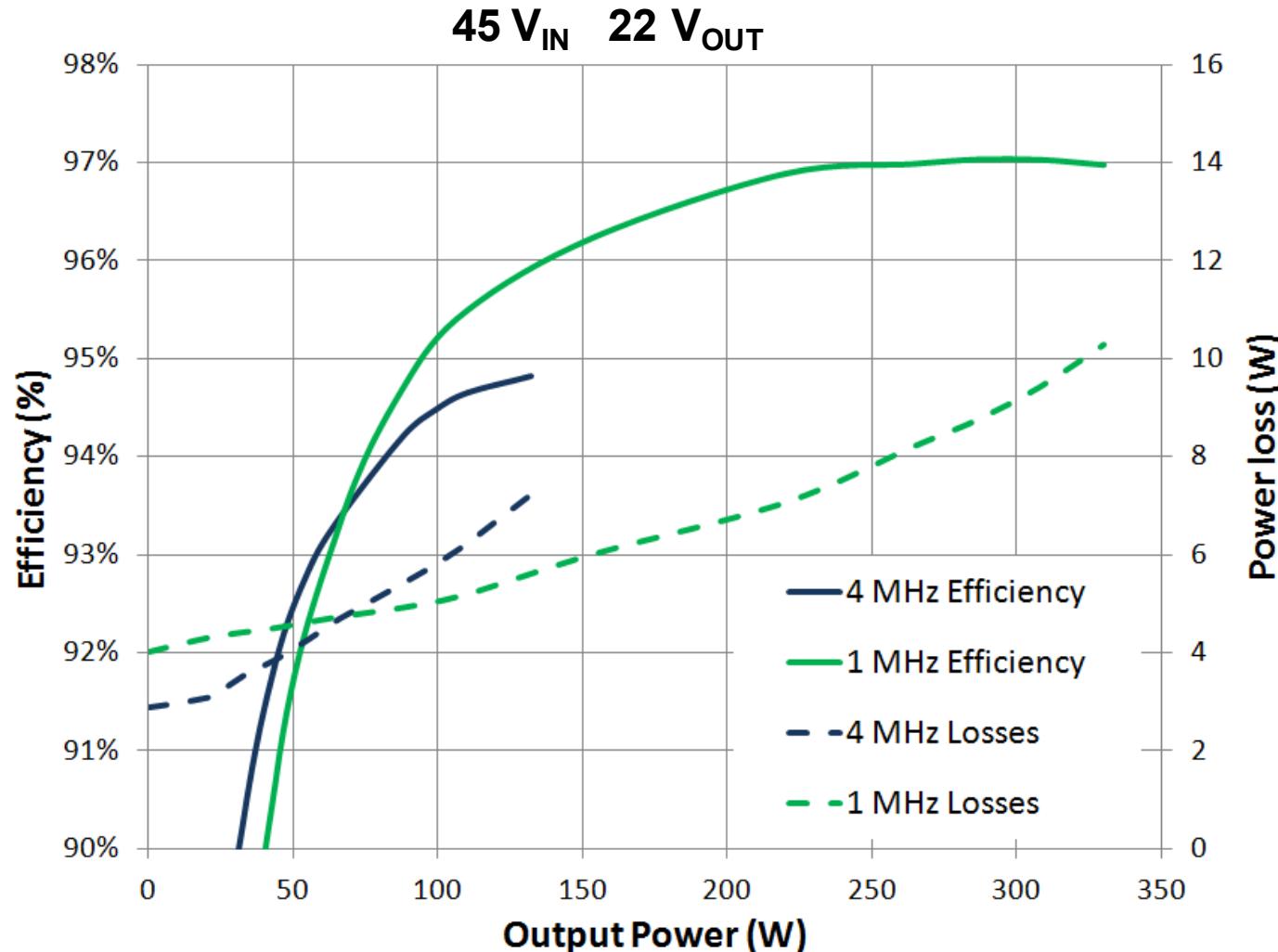



4MHz Loss Breakdown

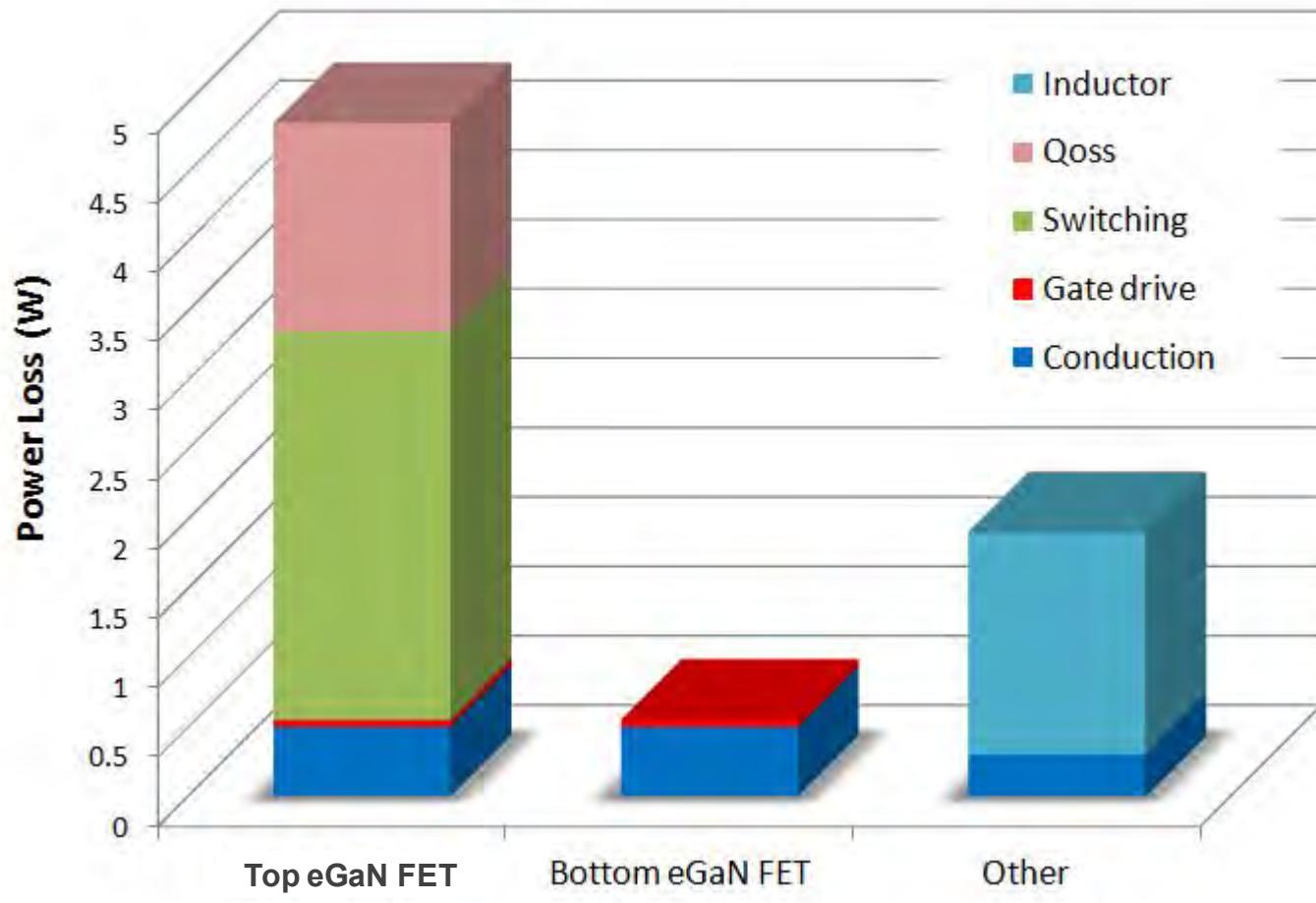




Resonant Converters




Resonant Converter

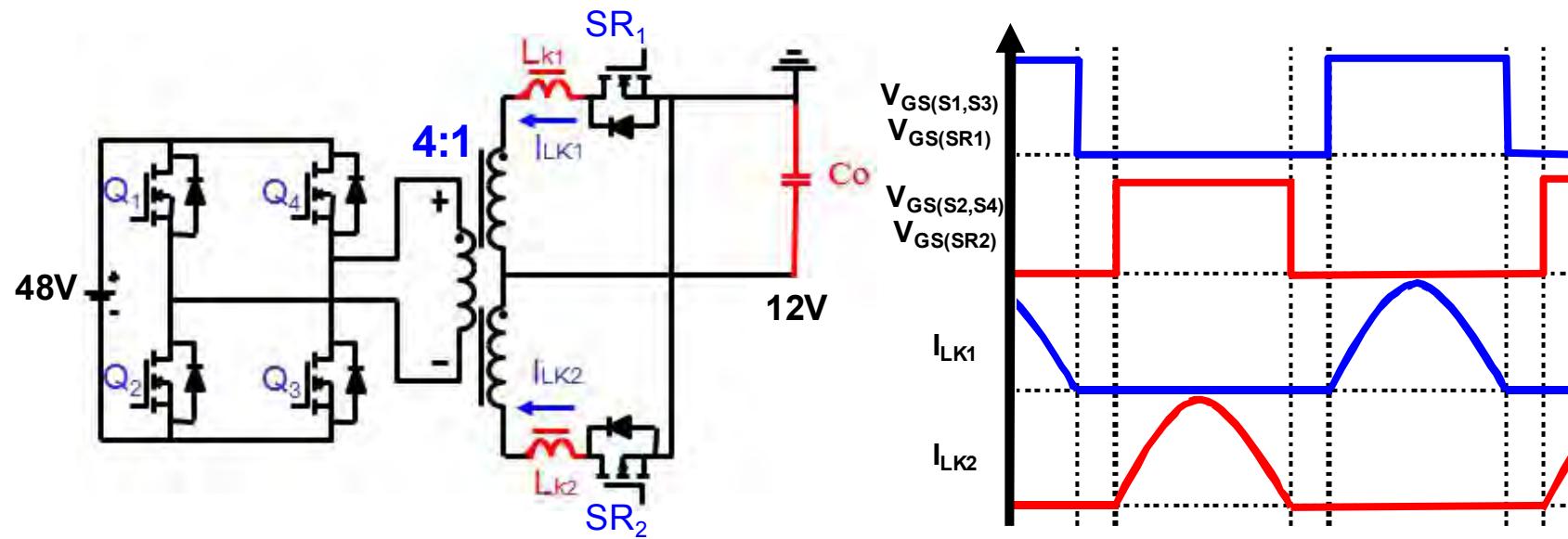

Ref: Y. Ren, M. Xu, J. Sun, and F. C. Lee, "A family of high power density unregulated bus converters," IEEE Trans. Power Electron., vol. 20, no. 5, pp. 1045–1054, Sep. 2005.




eGaN® FET vs MOSFET

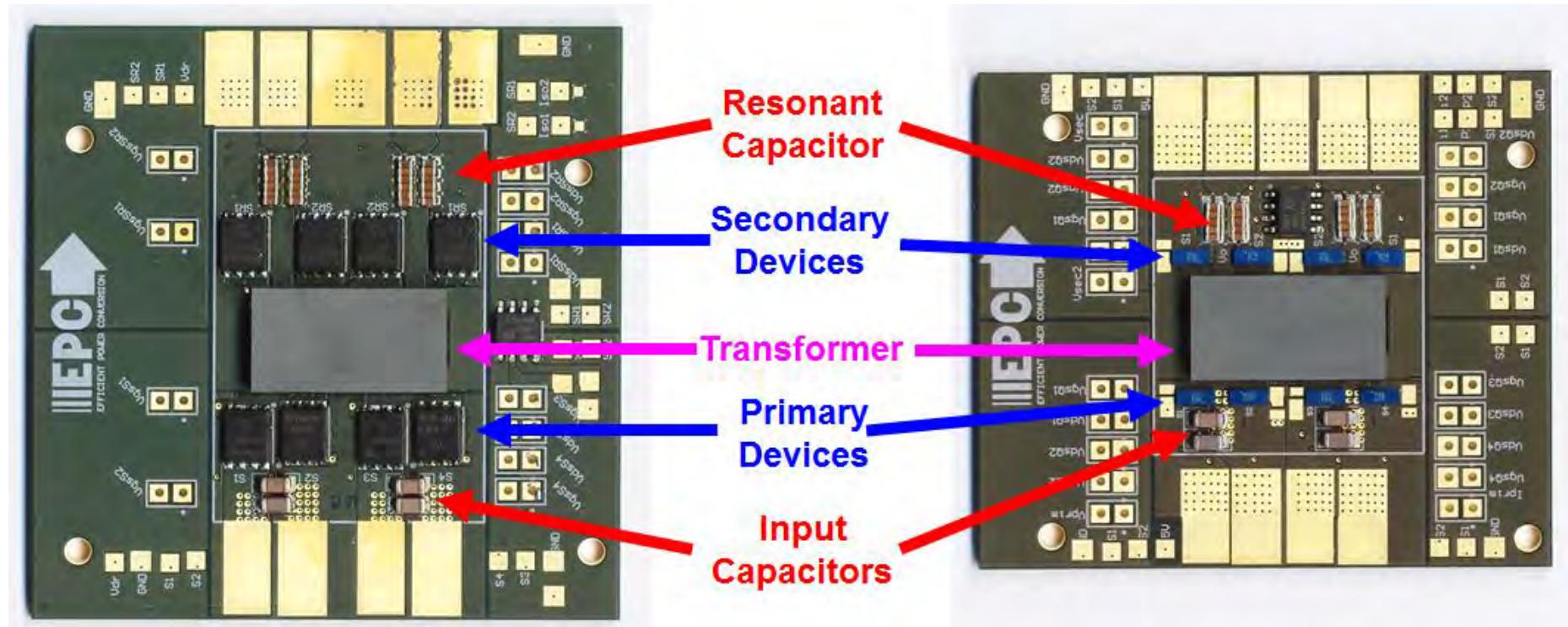




Duty Cycle Comparison

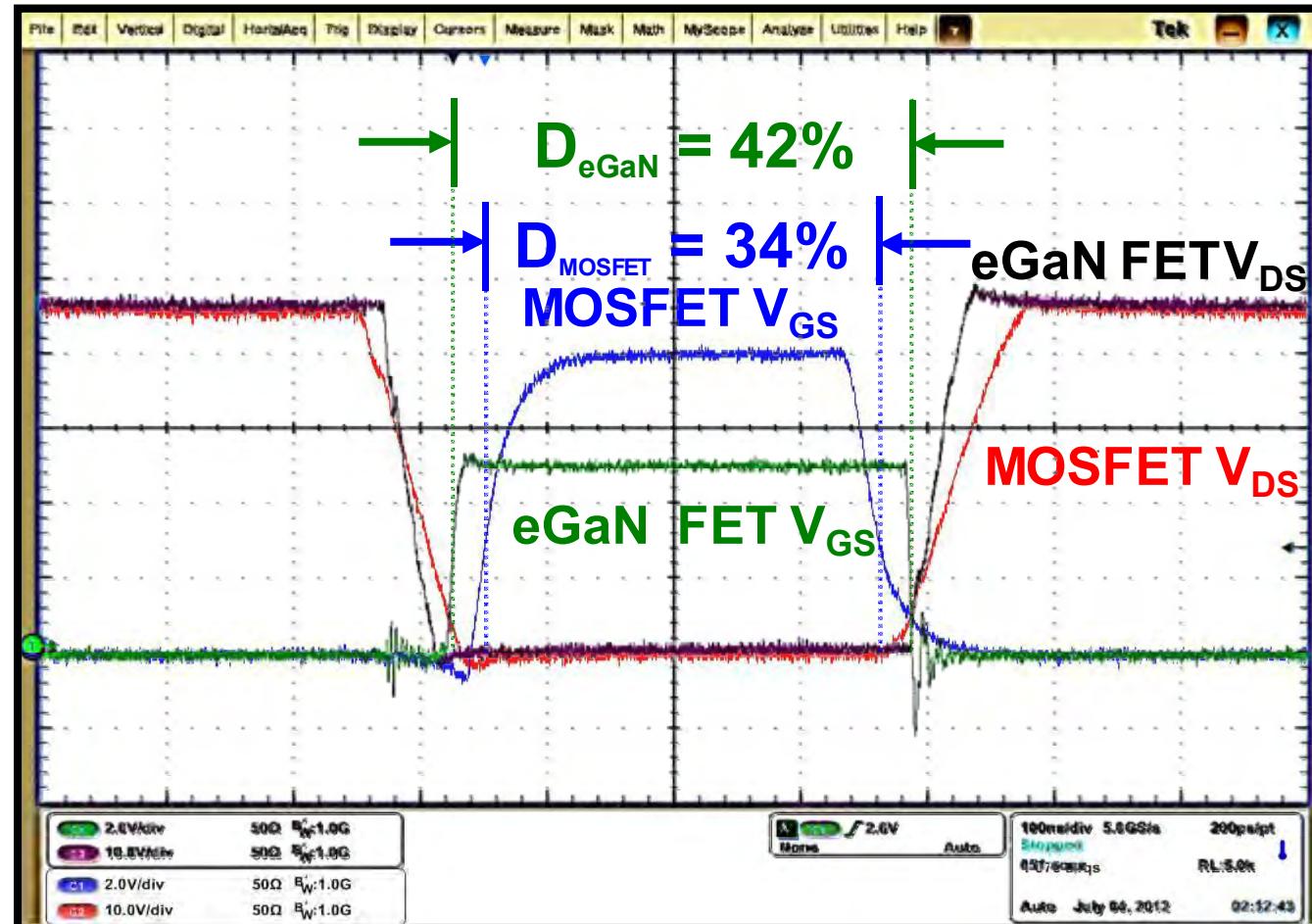

$F_s = 1.2 \text{ MHz}$, $V_{IN} = 48 \text{ V}$, and $V_{OUT} = 12 \text{ V}$




Efficiency Comparison

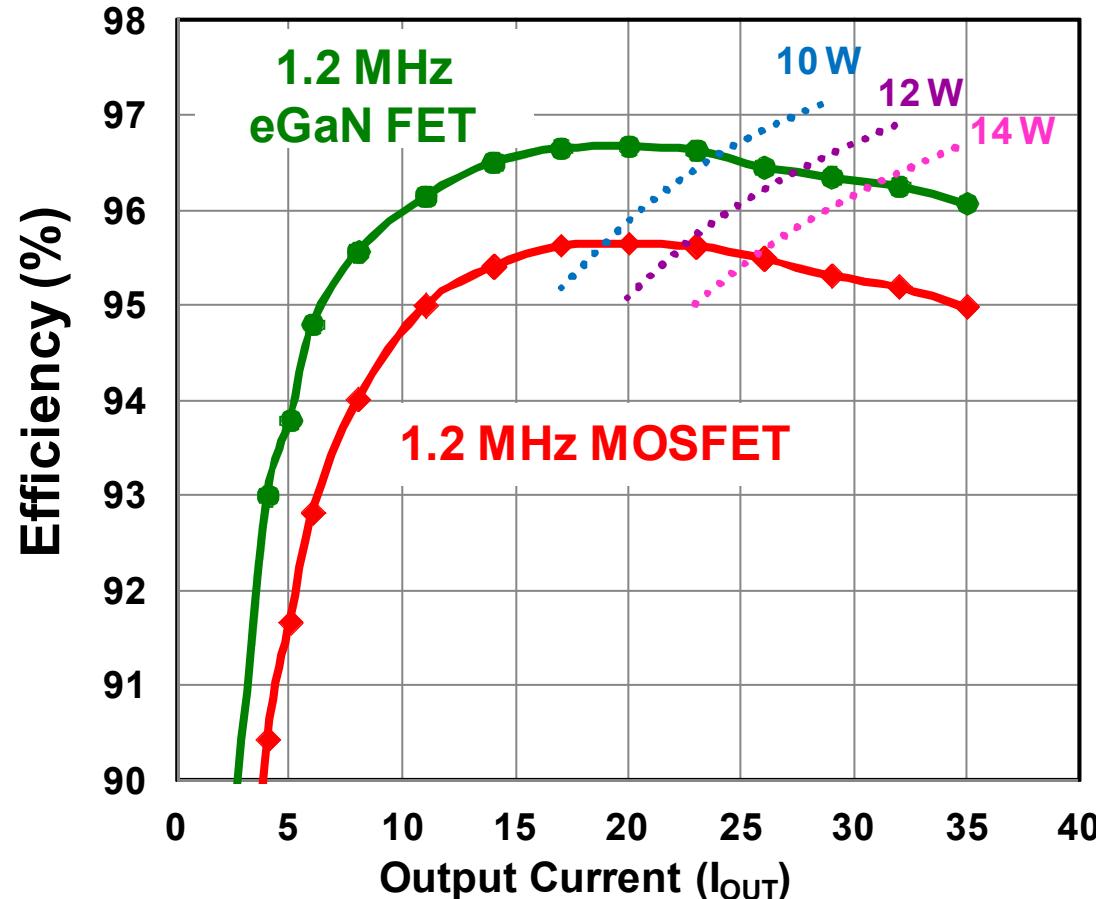

$F_s = 1.2 \text{ MHz}$, $V_{IN} = 48 \text{ V}$, and $V_{OUT} = 12 \text{ V}$



Loss Breakdown

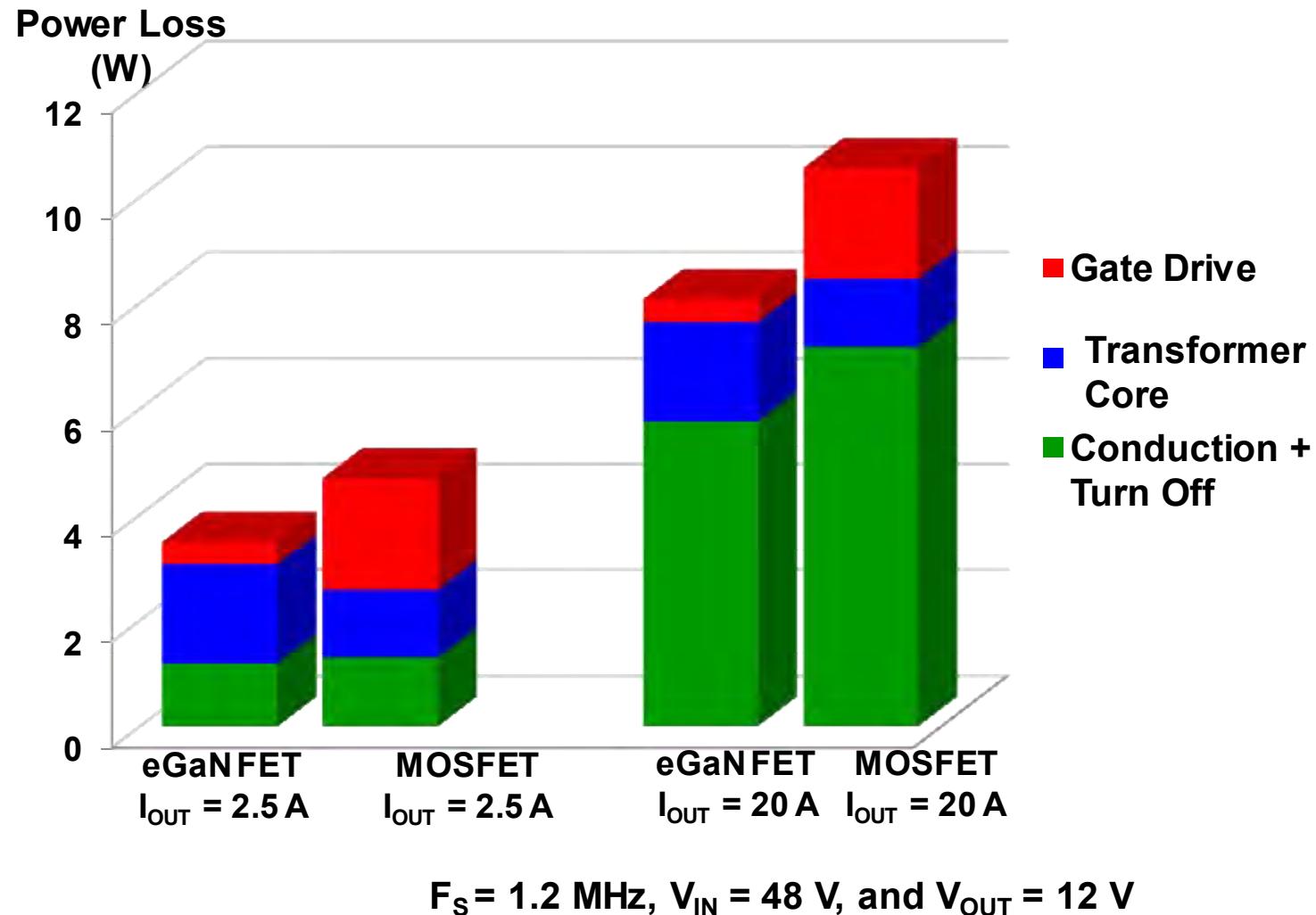




Wireless Power




Wireless Power

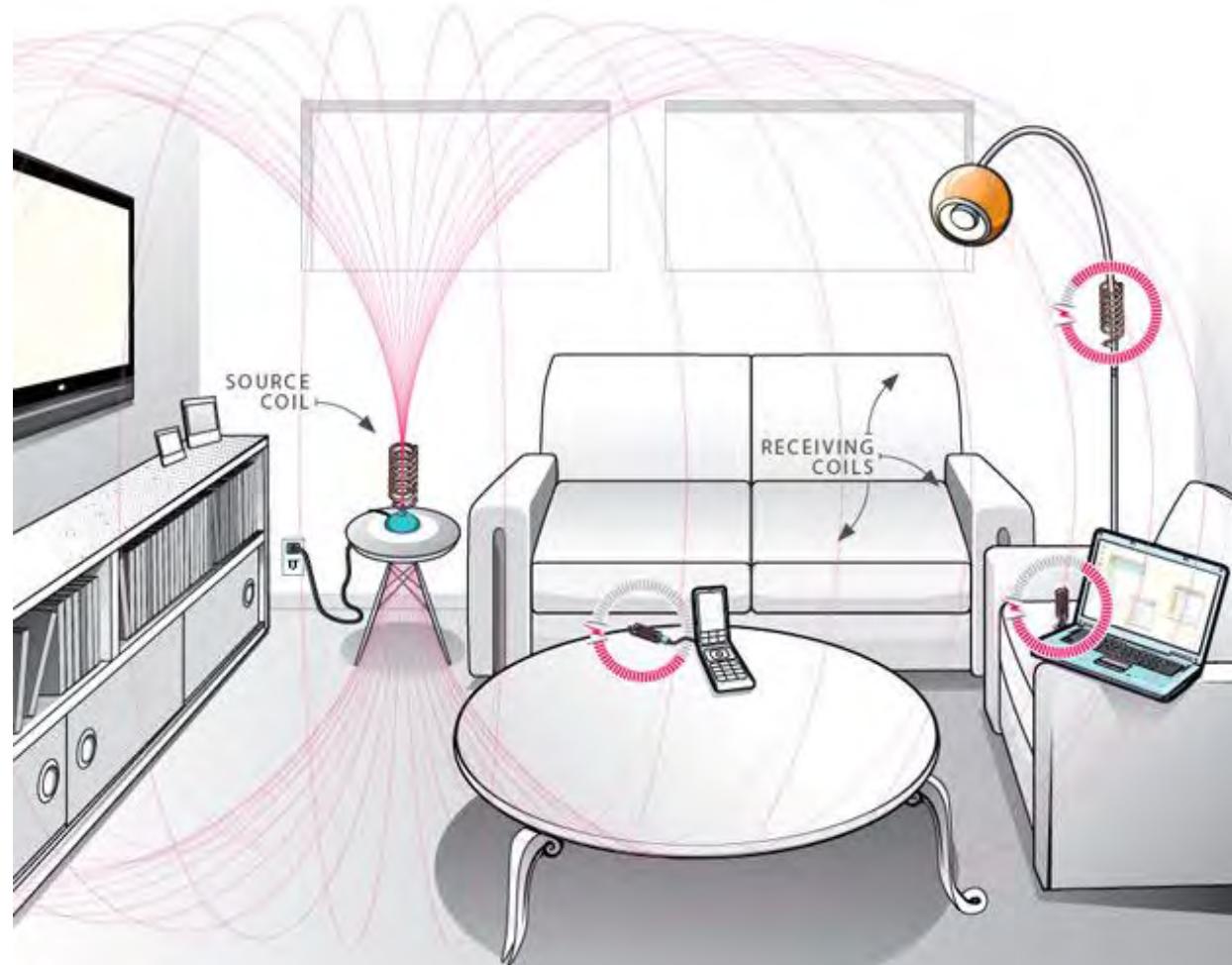




Wireless Power

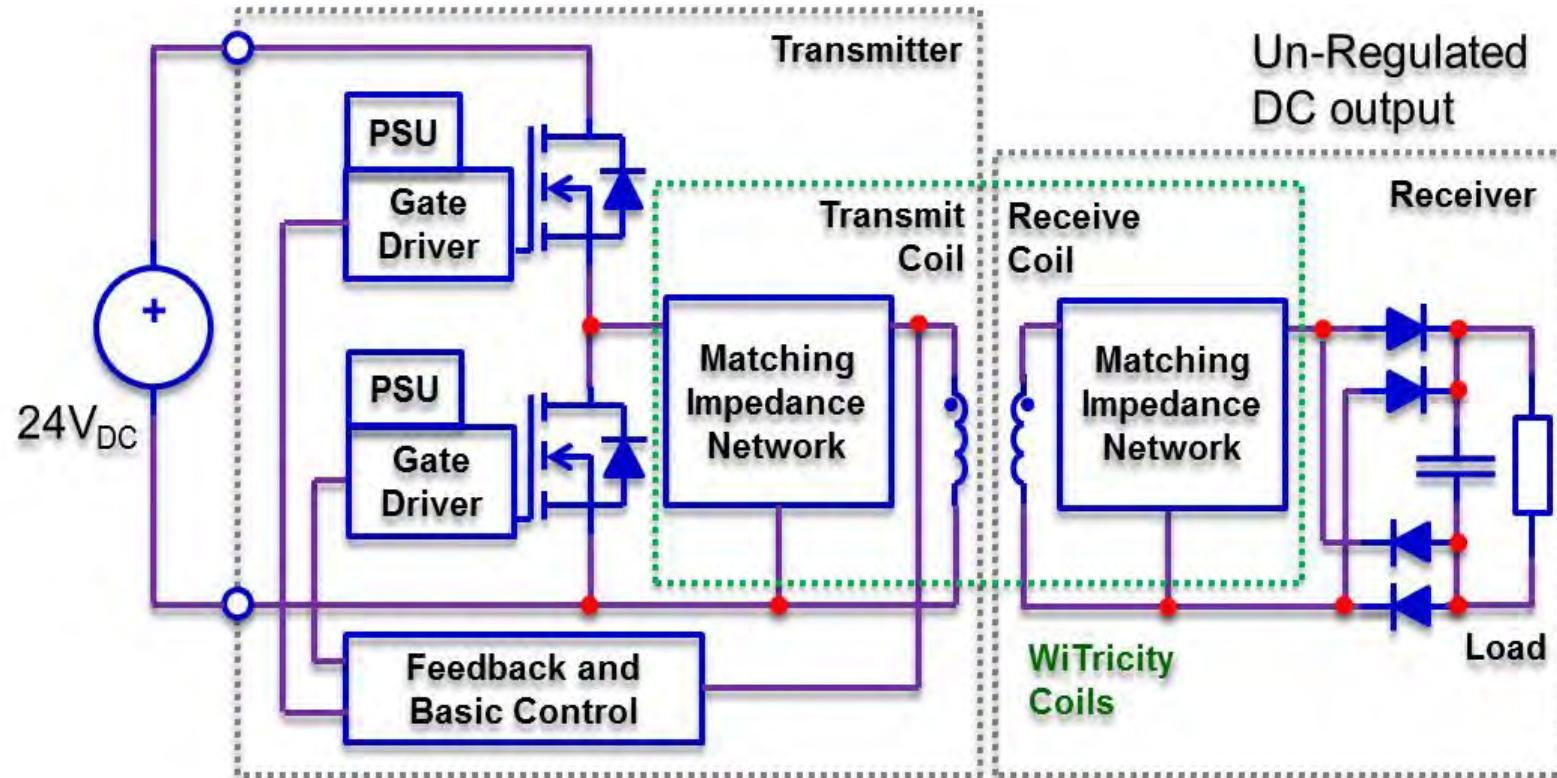



Wireless Power

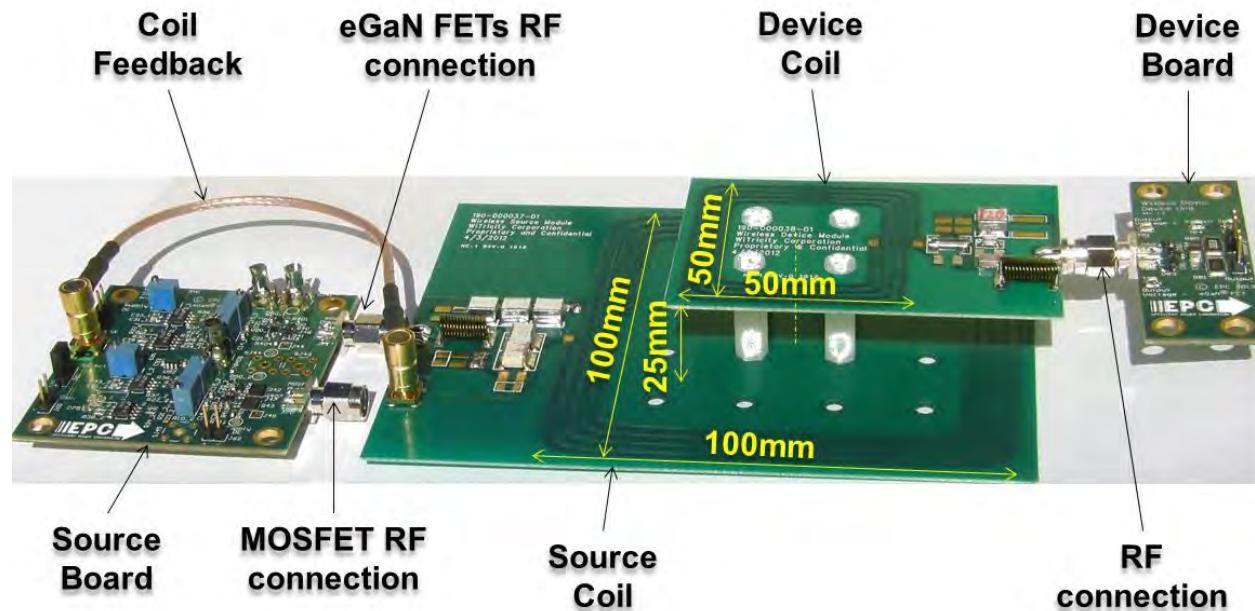




Efficiency Comparison




Efficiency [%]

6.639 MHz, 23.6 Ω load

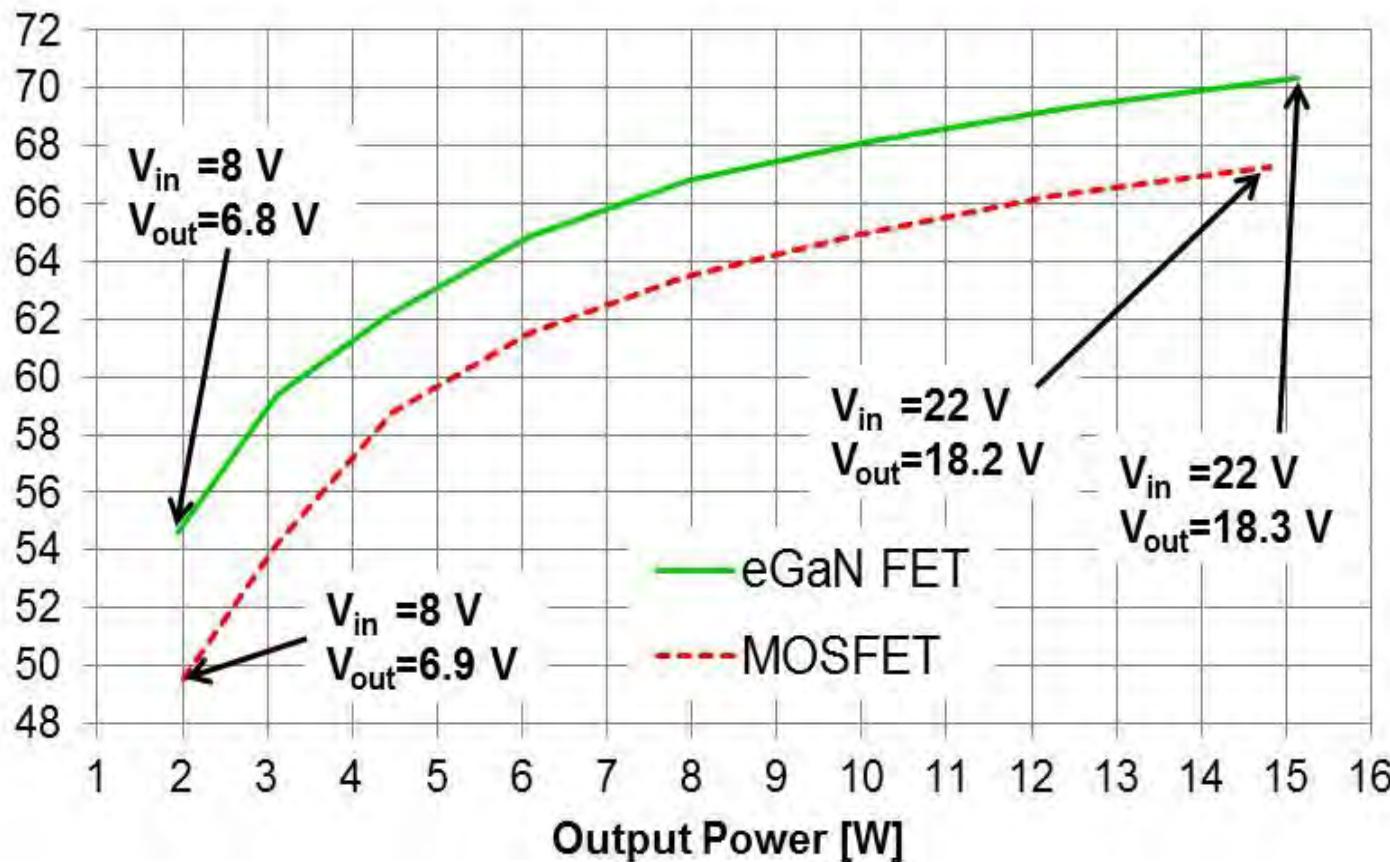



Loss Breakdown

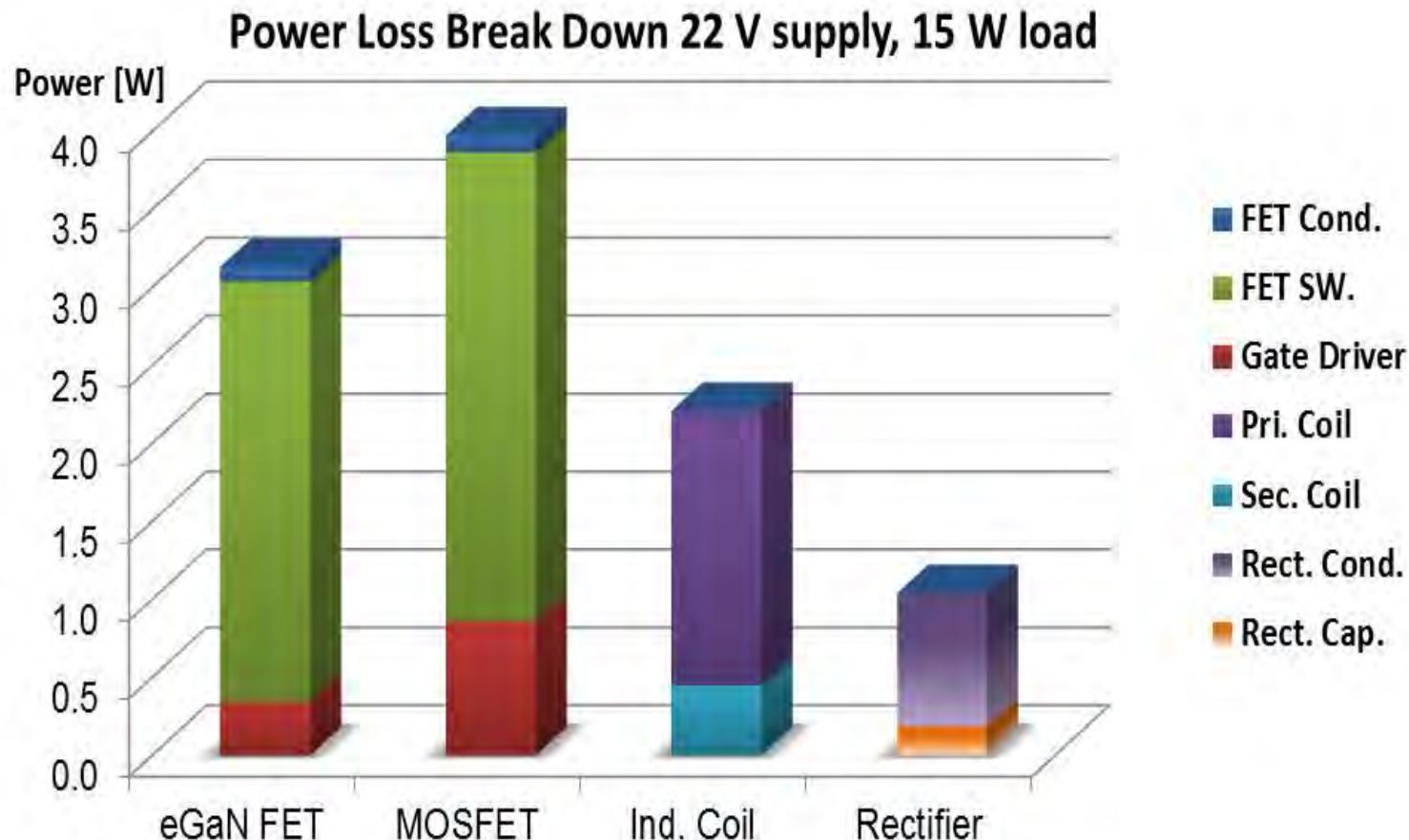



Summary



- eGaN FETs operate efficiently in multi-megahertz envelope tracking systems which can reduce transmit power by 50%.
- eGaN FETs reduce power losses by 25% or more in 1.2 MHz resonant DC-DC converters.
- eGaN FETs reduce power losses by 25% in 6.78 MHz wireless power transmission systems.
- You can always improve efficiency with eGaN FETs!



*The end of the road
for silicon.....*

*is the beginning of
the eGaN FET
journey!*