

The eGaN<sup>®</sup> FET  
Journey Continues

Performance Comparison for A4WP  
Class-3 Wireless Power Compliance  
between eGaN<sup>®</sup> FET and MOSFET in a  
ZVS Class D Amplifier



# Agenda



- Introduction to the A4WP Class-3 Specifications
- ZVS Class D Amplifier
- eGaN<sup>®</sup> FET versus MOSFET Comparison
- Synchronous Bootstrap FET Gate Driver
- Experimental Results
- Summary

eGaN<sup>®</sup> is a registered trademark of Efficient Power Conversion Corporation



# Introduction




- Wireless power transfer solutions must address convenience-of-use such as:  
device orientation and distance, multiple device capability, user simplicity, and power.
- Only the Alliance for Wireless Power (A4WP / Rezence) standard does:
  - Highly resonant (6.78 MHz ISM band)
  - Loosely coupled coils
  - Operation off-resonance
- ZVS Class D amplifier will be tested to the Class-3 requirements






# A4WP Class-3 Impedance Requirements

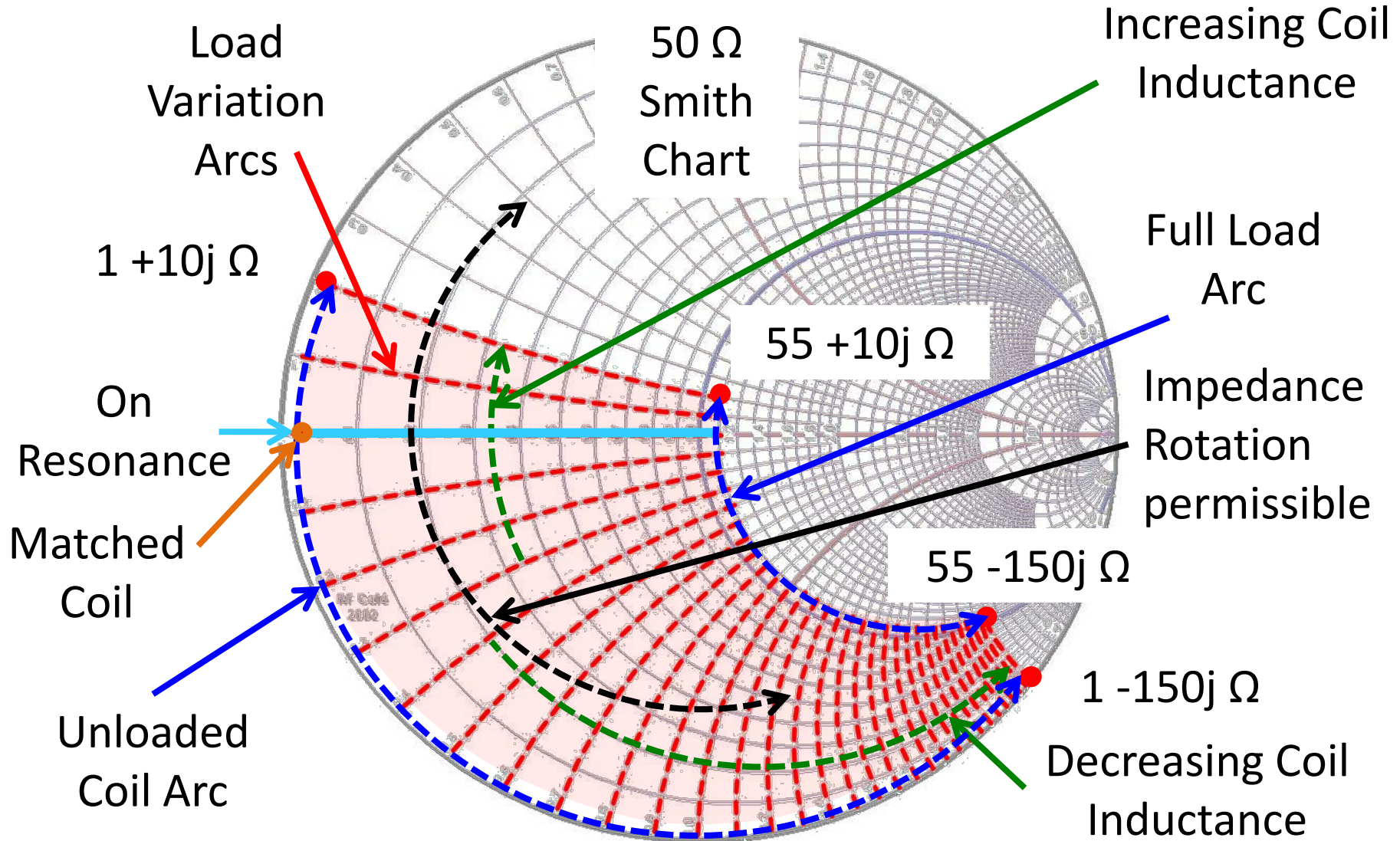

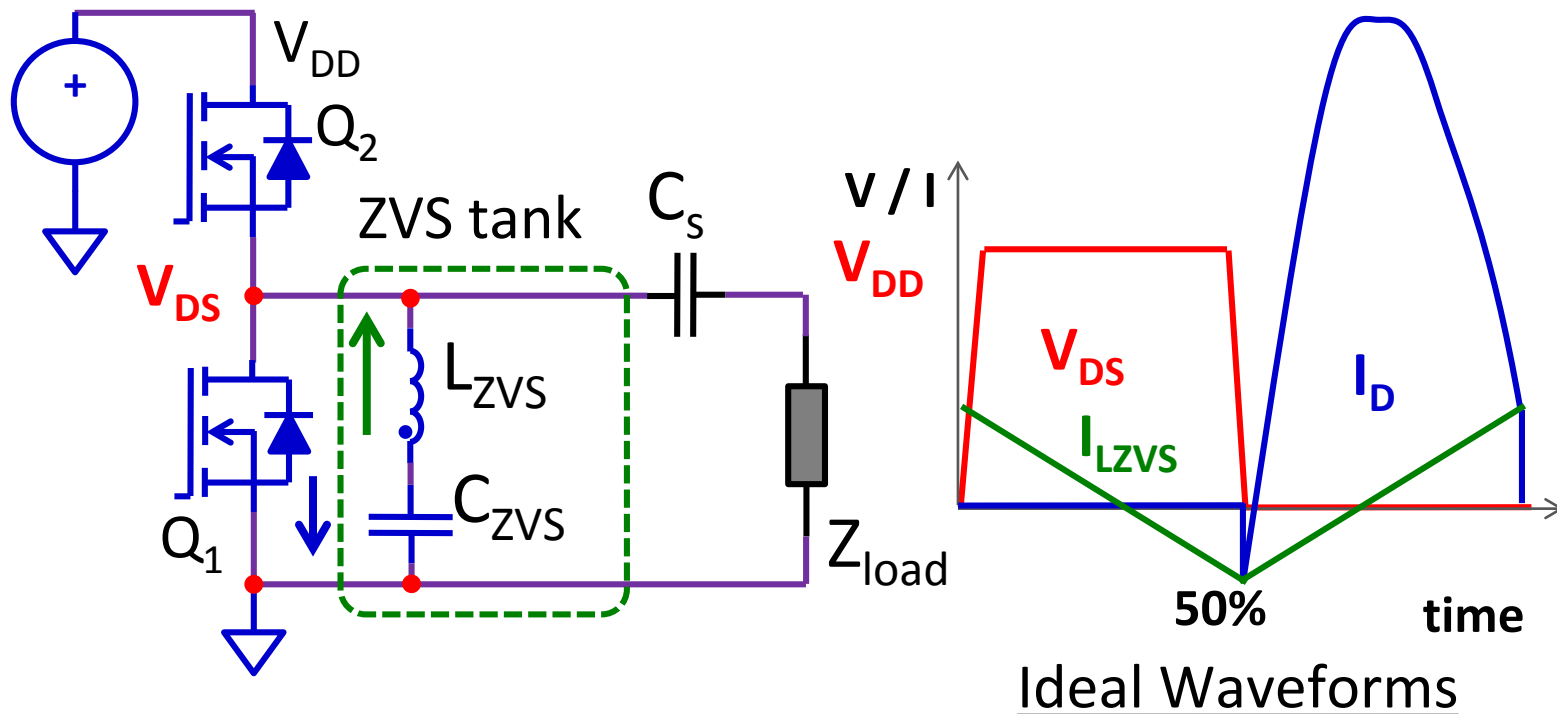- Switch voltage rating = Supply ( $V_{DD}$ ).
- $C_{OSS}$  Voltage is transitioned by the ZVS tank
- ZVS tank circuit does not carry load current
- Coil Voltage =  $\frac{\sqrt{2}}{\pi} \cdot V_{DD}$  [ $V_{RMS}$ ]







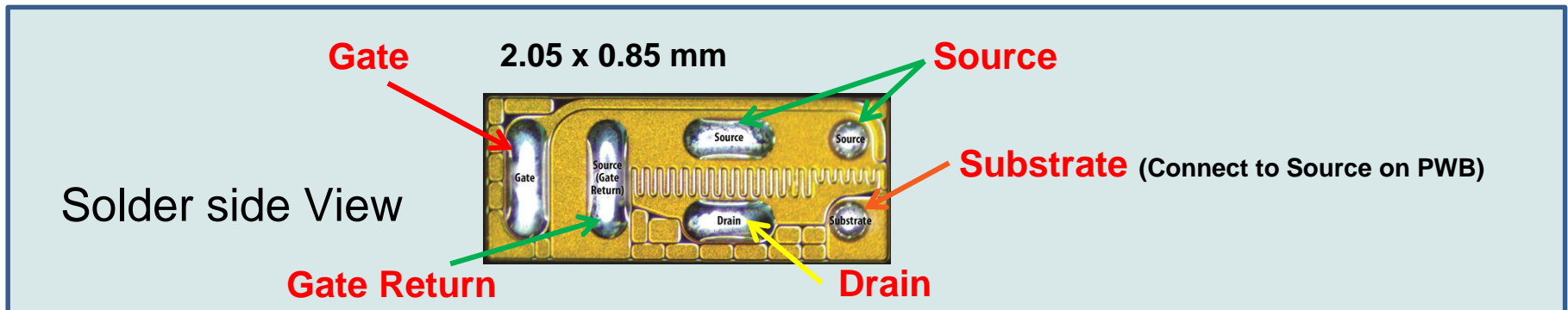
# Ultra High Frequency eGaN FETs



- Proven in various wireless power transfer amplifiers
- Low  $C_{ISS}$
- Low  $C_{OSS}$
- Zero  $Q_{RR}$
- Full  $dv/dt$  immunity



Part Number	Package (mm)	$V_{DS}$ (V)	$V_{GS}$ (V)	$R_{DS(on)}$ @5 V (m $\Omega$ )	$Q_G$ @5 V Typ. (pC)	$Q_{GS}$ Typ. (pC)	$Q_{GD}$ Typ. (pC)	$R_G$ Typ. ( $\Omega$ )	$V_{th}$ Typ. (V)	$Q_{RR}$ (nC)	$I_D$ (A)	$T_J$ Max. ( $^{\circ}C$ )
<a href="#">EPC8004</a>	LGA 2.05x0.85	40	6	125	358	110	31	0.34	1.4	0	2.7	150
<a href="#">EPC8009</a>	LGA 2.05x0.85	65	6	138	380	116	36	0.3	1.4	0	2.7	150
<a href="#">EPC8010</a>	LGA 2.05x0.85	100	6	160	354	109	32	0.3	1.4	0	2.7	150




# Wireless Power Transfer Figure of Merit



## Best-In-Class MOSFET comparison


- All topologies are ZVS:  $Q_G - Q_{GD}$
- $C_{OSS}$  is “absorbed” in matching but is important as it:
  - Drives off resonance losses
  - Determines design-ability
- $Q_{RR}$  ignored – poorly defined, amplifier is soft switching, BUT, transition time  $< t_{RR}$ :
  - eGaN FET  $Q_{RR} = 0$  nC
  - MOSFET 2  $Q_{RR} = 18.1$  nC !  
(FoM = 1900 nC·mΩ)

FoM<sub>WPT</sub> [nC·mΩ]

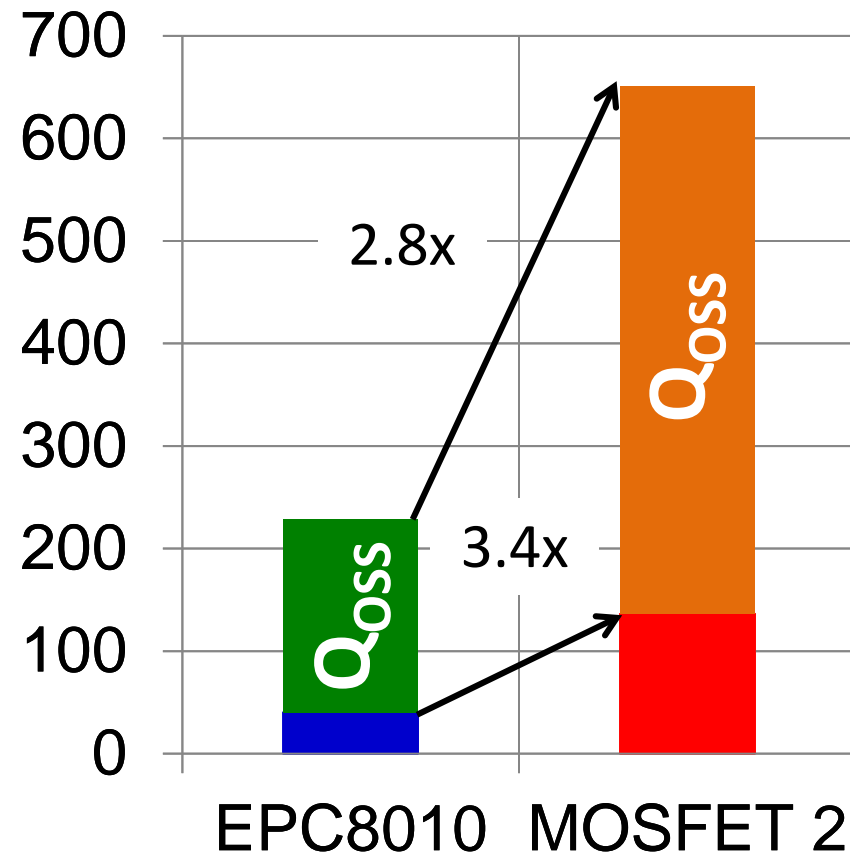


$$FOM_{WPT} = R_{DS(on)} \cdot (Q_G - Q_{GD} + Q_{OSS})$$

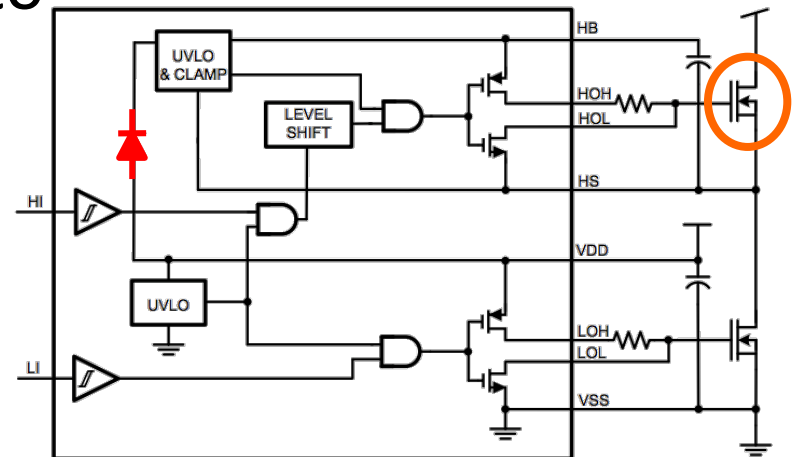- Gate drivers with internal bootstrap diodes always have  $Q_{RR}$  (schottky diode is very difficult to implement in IC form)
- Bootstrap diode  $Q_{RR}$  induces losses in the high side device
  - $Q_{RR}$  losses proportional to frequency
  - Present even with ZVS as  $t_{ZVS}$  (Switch-node voltage transition time) is shorter than  $t_{RR}$





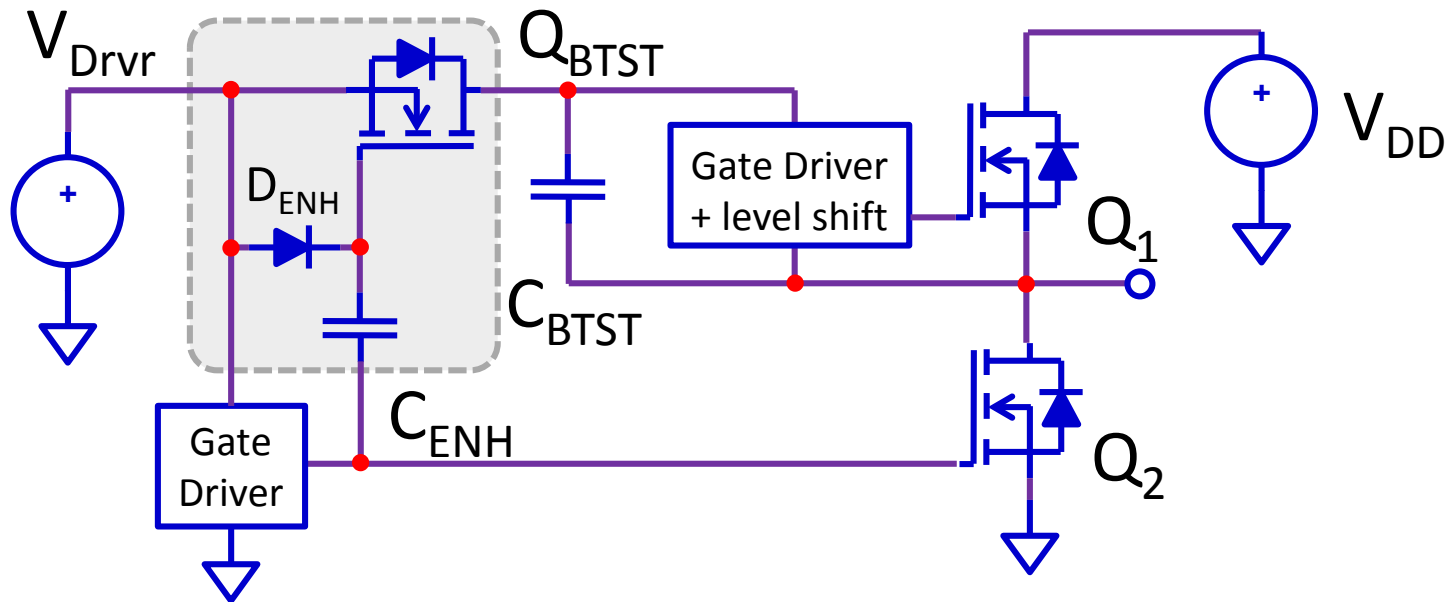- $Q_{BTST}$  – Bootstrap FET for main switch ( $Q_1$ ) zero  $Q_{RR}$
- $Q_{BTST}$  – Switches synchronously with  $Q_2$
- No additional active gate driver circuitry needed
- $C_{ENH}$  – Used for level shifting
- $D_{ENH}$  – Bootstrap diode for  $C_{ENH}$  (Low voltage < 20V zero  $Q_{RR}$ )






# Load Variation ( $j\Omega$ ) Results



## Total Amplifier Losses

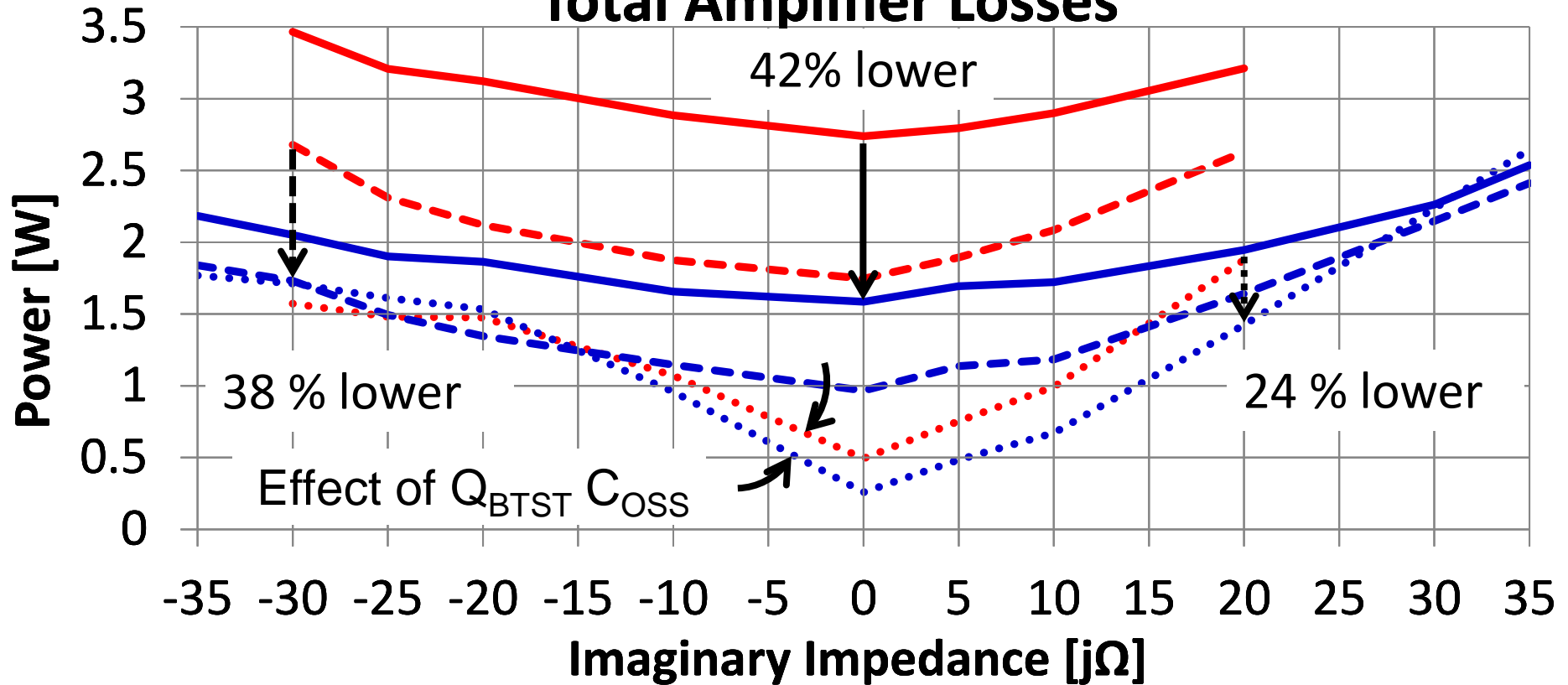

..... EPC8010 10  $\Omega$  7 W

..... MOSFET 10  $\Omega$  7 W

---- EPC8010 36  $\Omega$  16 W

---- MOSFET 36  $\Omega$  16 W

— EPC8010 55  $\Omega$  16 W


— MOSFET 55  $\Omega$  16 W



# Load Variation ( $\Omega$ ) Results



## Total Amplifier Losses

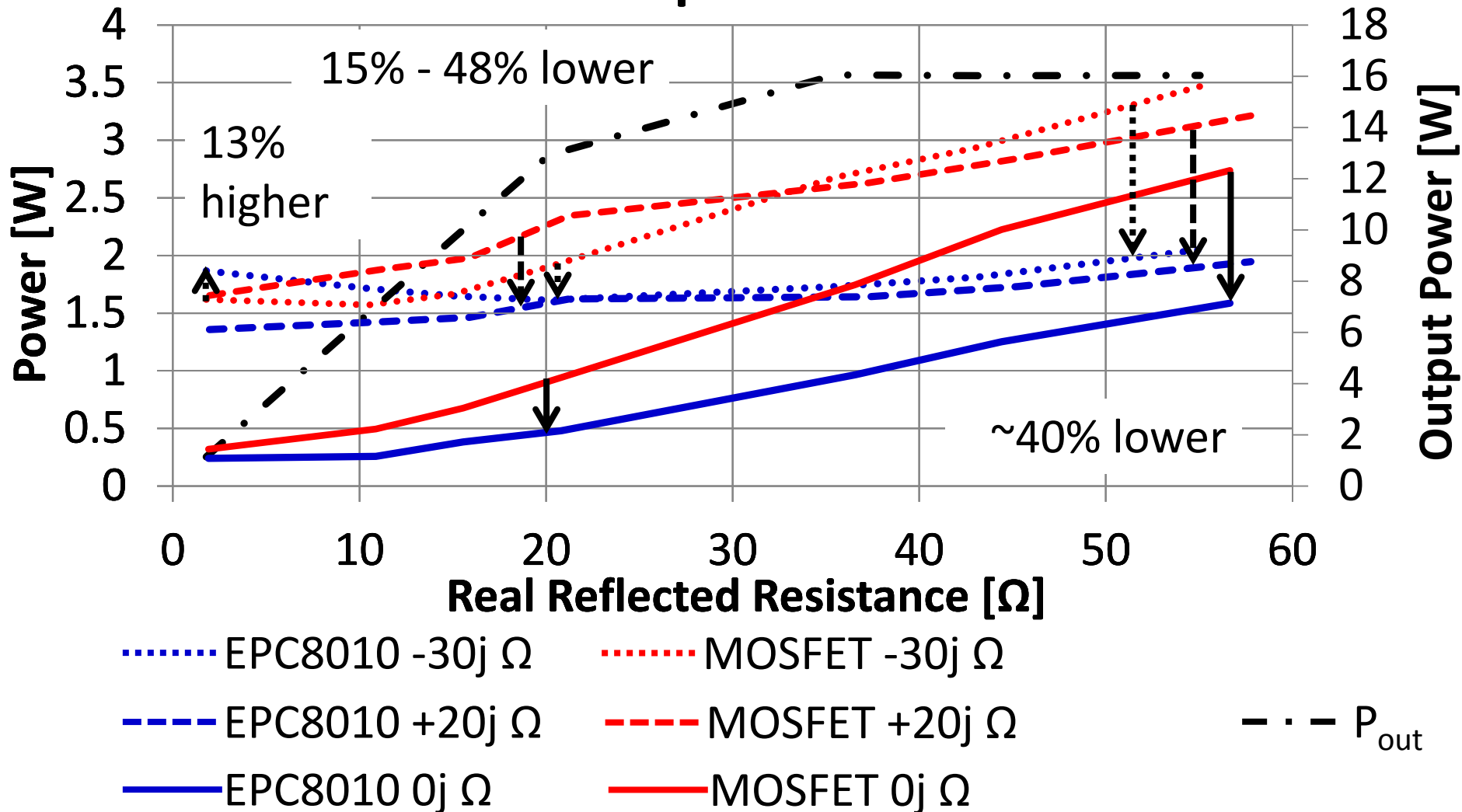





# Waveform Improvements



$V_{DD} = 45 \text{ V}$ , No load

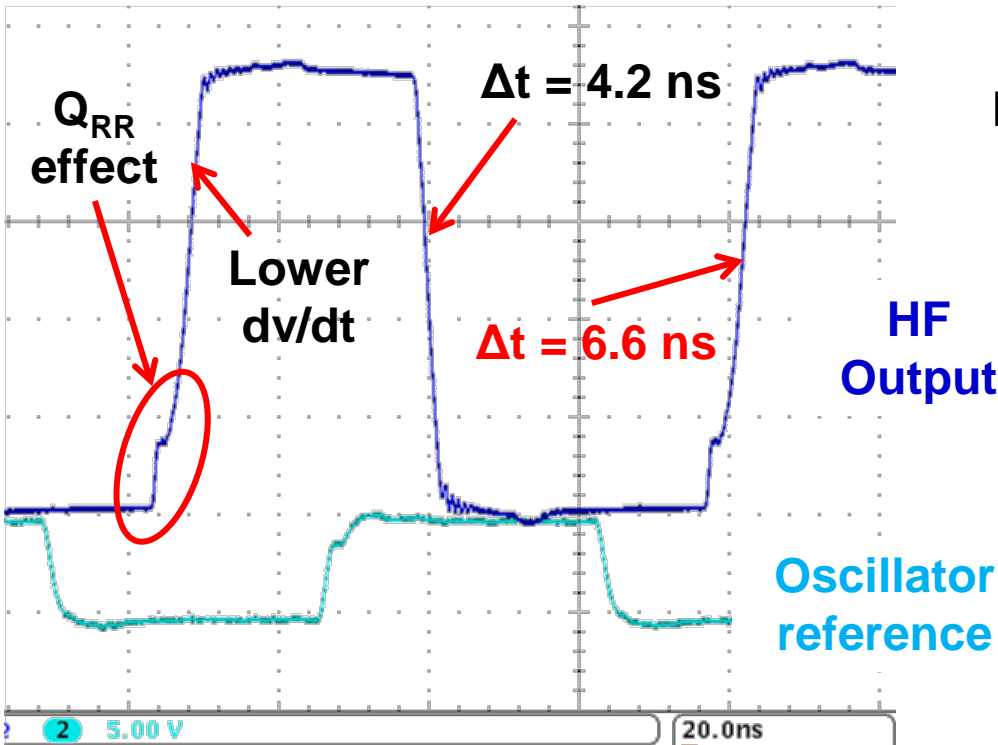

Original Internal Bootstrap Diode

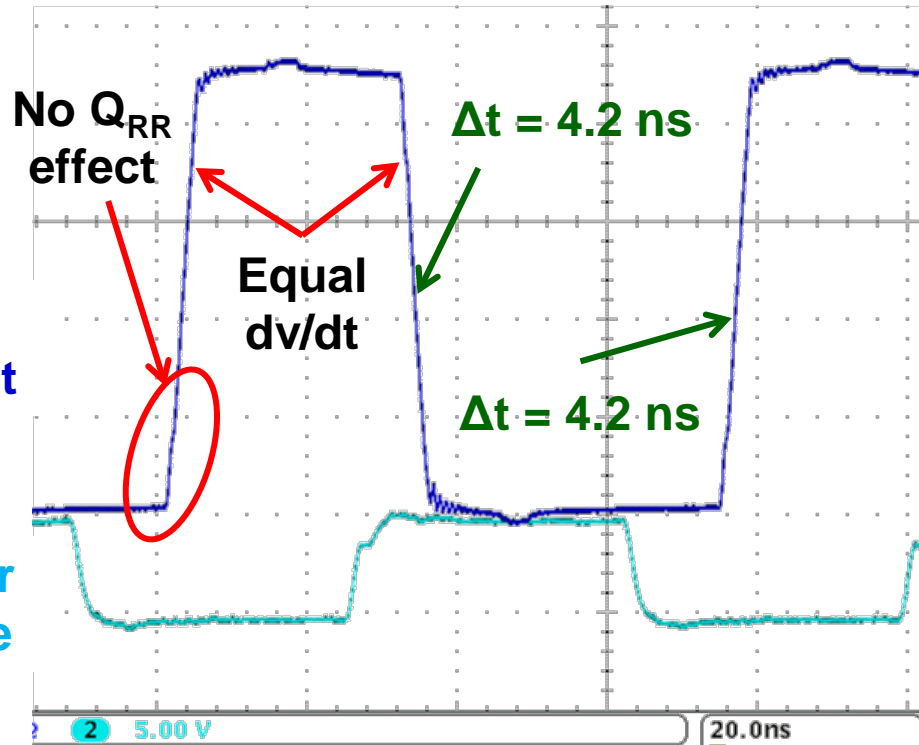

eGaN FET Synchronous Bootstrap FET



# Summary



eGaN FETs in a ZVS Class D amplifier were tested to the A4WP Class-3 specifications :


- eGaN FETs always yield higher efficiency than best-in-class MOSFETs
- Gate driver and eGaN FET temperature remain below 100°C
- eGaN FET's lower  $C_{OSS}$  reduces the ZVS current needed, resulting in lower power dissipation for both FET and  $L_{ZVS}$
- eGaN FETs reduce board space by 40 %
- eGaN FETs enable a wider impedance drive range than MOSFETs


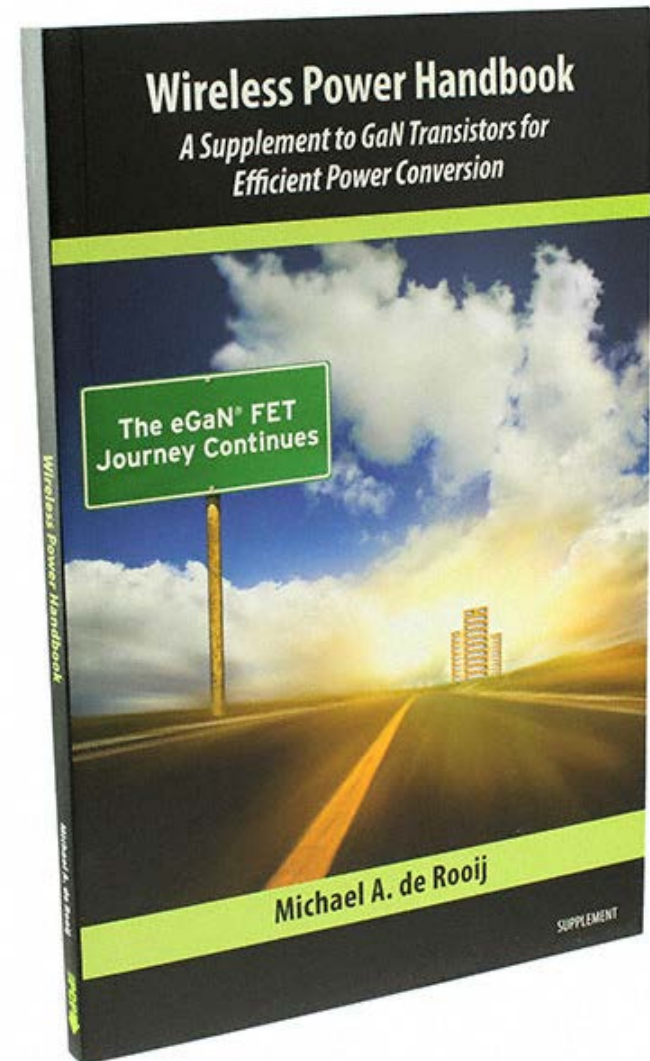
# Wireless Power Handbook



Handbook on wireless power that covers this work and much more – available at Digi-Key (917-1098-ND)





# EPC

EFFICIENT POWER CONVERSION

## Where is GaN going...

