

eGaN® FET Drivers and Layout Considerations



Alex Lidow PhD, CEO and Johan Strydom, PhD, Vice President Applications Engineering, Efficient Power Conversion Corporation

eGaN FETs differ from their silicon counterparts because of their significantly faster switching speeds and consequently have different requirements for gate drive, layout, and thermal management which can all be interactive.

DRIVING eGaN® FETS

When considering gate drive requirements, the three most important parameters for eGaN FETs are (1) the maximum allowable gate voltage, (2) the gate threshold voltage, and (3) the “body diode” voltage drop. The maximum allowable gate-source voltage for an eGaN FET of 6 V is low in comparison with traditional silicon. Secondly, the gate threshold is also low compared to most power MOSFETs, but does not suffer from as strong a negative temperature coefficient as MOSFETs. Thirdly, the “body diode” forward drop can be higher than comparable silicon MOSFETs, which requires additional attention to timing for the gate drive as compared to MOSFETs.

Table 1 highlights some of these key parameters as compared with a power MOSFET.

Gate pull-down resistance

A great advantage of eGaN FETs is their switching speed. However, the accompanying higher di/dt and dv/dt require a layout with less parasitic capacitance, resistance, and inductance, which will require some new considerations for the gate driver. To understand this further we will look at a half-bridge with a high dv/dt turn-on of a complementary device as shown in Figure 1. The current from the Miller charge flows from the drain through C_{GD} and C_{GS} to the source as well as through C_{GD} to the internal gate resistance (R_G) and the gate driver sink resistance (R_{Sink}) to the source. The requirement for avoiding dv/dt (Miller) turn-on is then given by:

$$C_{GD} \times dv/dt \times (R_G + R_{Sink}) \times (1 - e^{-dt/\alpha}) < V_{TH} \quad (1)$$

Where α is the passive network time constant $(R_G + R_{Sink}) \cdot (C_{GD} + C_{GS})$ and dt is the dv/dt switching time. Therefore, to avoid Miller turn-on of an eGaN FET, it is necessary to limit the total resistance path ($R_G + R_{Sink}$) between the device gate and source for some second generation devices.

For devices with good Miller ratios ($Q_{GD}/Q_{GS} \cdot (V_{TH}) < 1$), this is not required. It should be noted that, since Q_{GD} increases with V_{DS} , this ratio will get worse with increasing drain-source voltage and may therefore lead to Miller turn-on. On the other hand, Eq. (1) improves at very low bus voltages where $Q_{GD}/Q_{GS} \cdot (V_{TH})$ is much less than one. To be safe, a gate drive pull-down resistance of 0.5 Ω or less is recommended for higher voltage devices.

Even with a low resistance pull down, the maximum drain node dv/dt that will avoid Miller turn-on will still be limited by:

$$dv/dt_{max} \approx V_{TH} / (Z_{pull-down} \cdot C_{GD})$$

where $Z_{pull-down}$ is the impedance of the external gate driver loop between gate and source of the device. This includes the Device gate resistance R_G , gate driver pull-down resistance R_{Sink} as well as the loop inductance. Keeping the loop inductance low is further complicated by traditional designing long narrow leads between the gate driver and the device gate. This can be avoided by widening and shortening the traces between the gate driver and gate of the device.

FET Type	Typical 100 V Silicon	100 V eGaN FET
Maximum gate-source voltage	± 20 V	+6V / -5V
Reverse body diode voltage	~ 1 V	~ 1.5 -2.5 V
Gate threshold	2 V – 4 V	0.7 V – 2.5 V
dv/dt capacitance (Miller) ratio $Q_{GD}(50V)/Q_{GS}(V_{TH})$	0.5-0.8	0.8
Internal gate resistance	$> 1 \Omega$	$< 0.6 \Omega$
Change in $R_{DS(ON)}$ from 25°C to 100°C	$> +50\%$	$< +40\%$
Change in V_{TH} from 25°C to 100°C	-20%	+3%
Gate to source leakage	few nA	few mA
Body diode reverse recovery charge	high	none
Avalanche capable	Yes	not rated

Table 1: Comparison between 100 V Si MOSFETs and 100 V eGaN FETs.

GATE PULL-UP RESISTANCE

Because the total Miller charge (Q_{GD}) is much lower for an eGaN FET than for a similar on-resistance power MOSFET, it is possible to turn on the device much faster. Too high a dv/dt can reduce efficiency by creating shoot-through during the ‘hard’ switching transition. It would therefore be an advantage to adjust the gate drive pull-up resistance to minimize transition time without inducing other unwanted loss mechanisms. This also allows adjustment of the switch node voltage overshoot and ringing for improved EMI. In power MOSFET applications this is achieved by placing a resistor and anti-parallel diode in series with the gate drive output. For eGaN FETs, where the threshold voltage is low, this is not recommended. The simplest general solution is to split the gate pull-up and pull-down connections in the driver and allow the insertion of a discrete resistor as needed.

GATE DRIVE DEAD-TIME

The eGaN FET reverse bias or “body diode” operation has the benefit of no reverse-recovery losses. This advantage, however, can be offset by the higher body diode forward voltage drop [1]. The diode conduction losses can be significant, especially at low voltages and high frequencies. Unlike silicon diode reverse recovery losses, these conduction losses can be minimized through proper dead-time management that keeps the body diode conduction interval as short as possible. The shorter and less variable switching times of eGaN FETs allow for much tighter dead-time control which, in turn, reduces body diode conduction loss. A reduction of dead-time to just a few nanoseconds virtually eliminates body diode losses.

GATE DRIVE SUPPLY REGULATION

The maximum gate voltage limitation of 6V on the eGaN FET adds restrictions to the gate drive supply range, and requires some form of supply regulation. Of greatest concern is the floating or high-side supply in a half-bridge configuration. A simple implementation to improve matching between low-side (ground referenced) and high-side supplies is through the use of a ‘matching’ diode as shown for a discrete gate drive implementation in Figure 2.

This implementation is only suited for complementary switched, half-bridge applications where the dead-time and body diode conduction is minimal. For applications where the eGaN body diode conduction can be significantly longer than the bootstrap diode turn-on time, the approximately 2V body diode voltage drop will add to

the supply voltage and can cause overvoltage of the high-side supply. In such cases, some form of post-bootstrap supply regulation is required.

The LM5113, from Texas Instruments, is an example of an eGaN FET optimized half bridge driver that implements bootstrap regulation. Integrated in the undervoltage lockout is an over-voltage clamp that limits bootstrap voltage to 5.2 V ensuring sufficient reliable operation under all circuit conditions. In addition to the clamp, there are separate source and sink pins, >50V/ns dv/dt capability, matched propagation time, 0.5 Ω pull down, and separate high side and low side inputs to unlock the efficiencies the eGaN FETs enable.

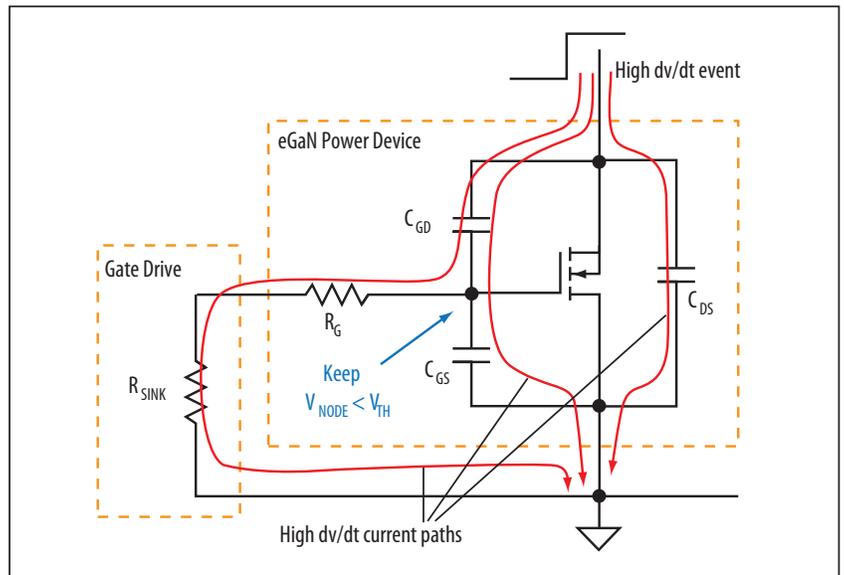


Figure 1: Effect of dv/dt on a device in the “OFF” state, and requirements for avoiding Miller-induced shoot-through.

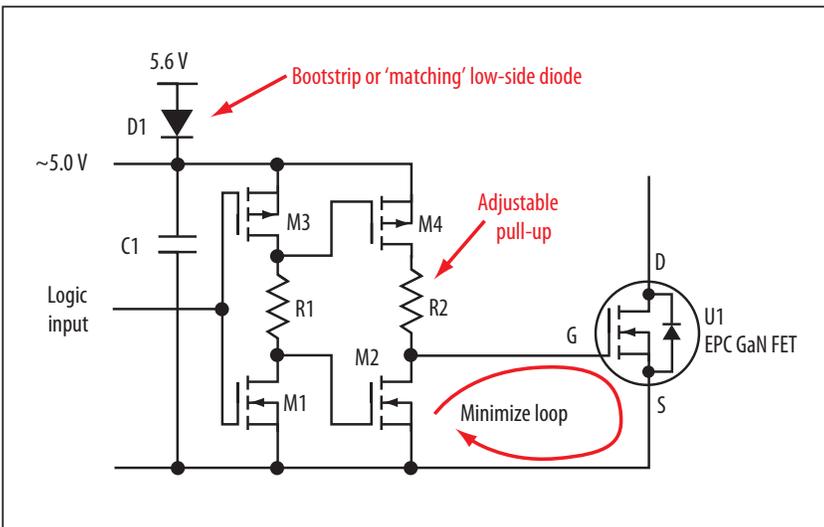


Figure 2: Discrete eGaN FET gate-driver solution showing method for complementary high-side and low-side supply voltage matching.

LAYOUT CONSIDERATIONS

Gate drive loop inductance

The maximum allowable gate voltage of 6 V is one and a half volts above the recommended 4.5 V drive voltage. This limited headroom requires an accurate gate drive supply, as well as a limited inductance between the eGaN FET and gate driver as the inductance can cause a voltage overshoot on the gate. Although some overshoot is acceptable, overshoot can be avoided entirely if the gate loop inductance is limited to:

$$1/4 \times (R_G + R_{Source})^2 \times C_{GS} \geq L_G \quad (2)$$

Where R_{Source} is the source resistance on the gate driver and L_G is the loop inductance between the gate driver and eGaN FET. Therefore, for a given gate loop inductance there will be a minimum source resistance value needed to keep V_{GS} from exceeding its maximum limit. Stated in another way, the pull-up resistance of the gate drive path should be adjusted for a given gate loop layout to ensure at least near critical damping to limit overshoot. Thus the inductance of the gate loop will directly limit the switching speed of the device and care should be taken to minimize it resulting in maximum efficiency.

Effect of common source inductance (CSI)

eGaN FETs in voltage ratings of 200 V or less come in LGA packages with very low package inductance and resistance. The impact of common source inductance could therefore be considered a layout issue rather than a gate driver requirement. The reality is not that simple.

The addition of CSI effectively reduces efficiency by inducing a voltage across the inductance that opposes the gate drive voltage during di/dt, thus increasing turn-on and turn-off times. It is therefore important to minimize common source inductance for optimum switching performance. In what seems to be a contradictory statement, the increase of CSI will decrease the possibility of Miller turn-on [2] by applying a voltage that adds to the V_{GS} if the designer is willing to accept the cost of increased switching loss. This is due to the fact that at the 'hard' turn-on of the complementary device, the current commutation di/dt across the CSI induces a negative voltage across the gate to help keep the device off during part of the voltage transition. What is not stated is that the CSI, gate capacitance, and gate drive pull down loop now forms an LCR resonant tank that needs to be damped to avoid an equivalent positive voltage ringing across the gate. This ringing could turn the device on again near the end, or even past the end of the voltage transition. Although increasing the gate drive sink resistance can help damp this LCR resonance at the cost of increased Miller turn-on sensitivity, the addition of a ferrite bead that is resistive at the resonant frequency can achieve the same result with less increase in Miller turn-on sensitivity. Figure 3 shows the equivalent circuit and Figure 4 shows switching waveforms.

In summary, CSI is more important to eGaN FETs than power MOSFETs due to the higher di/dt and dv/dt, and should be minimized through careful layout.

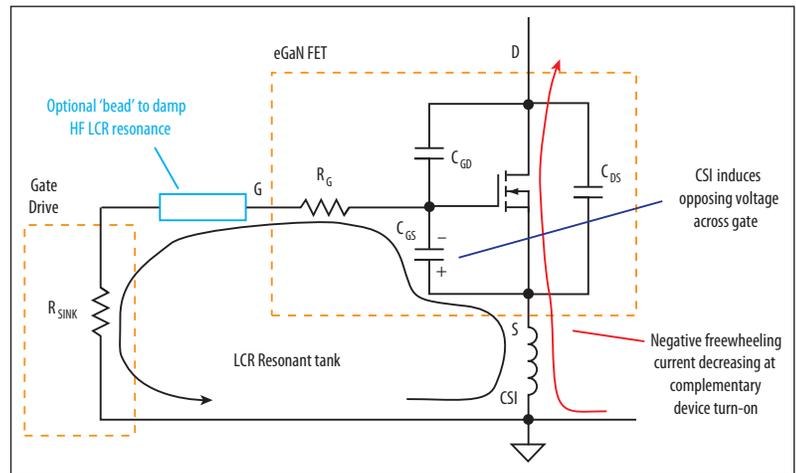


Figure 3: Equivalent partial power circuit showing the di/dt effect of 'hard' turn-on.

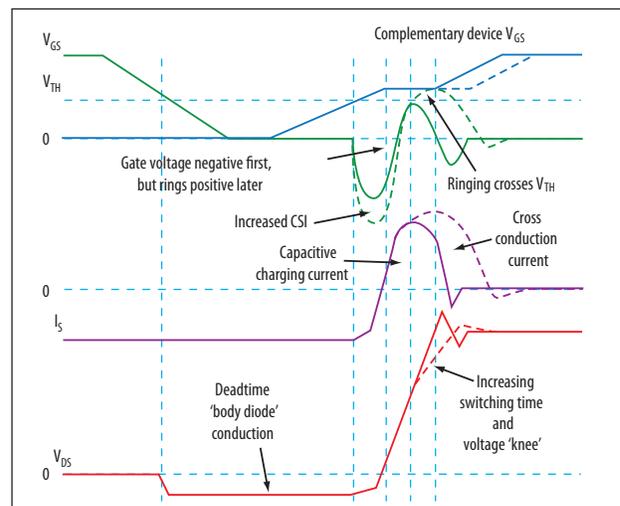


Figure 4: Waveforms for circuit in Figure 3 during 'hard' turn-on of complementary device showing effect of CSI ringing.

SUGGESTED LAYOUTS

Given the different considerations listed above, it is possible to develop some recommended PCB layouts for the eGaN FETs. In this section three levels of layout recommendations will be discussed, each with increasing performance metrics:

- 1) Single-sided termination suitable for PCB designs with 2 layers or more
- 2) Dual-sided termination PCB designs implementable with 4 layers or more
- 3) Filled-via dual-sided termination where the lowest possible CSI is required.

Single sided termination PCB layout

Where cost is an important factor in the design, a single-sided terminated design is recommended. This can be implemented on PCBs with 2 layers or more, an example of which is shown in Figure 5. The power connection to the drain and source are routed on the same layer of the PCB and terminate to one side of the FET. It is recommended that the drain and source terminals be connected, using vias, to additional layers to further enhance their current carrying capability. The recommended via design is a 10 mil (250 μm) hole diameter and 20 mil (500 μm) annular ring. Two vias per pad are recommended and should be sufficiently spaced based on PCB design guidelines and common source inductance design limits. To further reduce common source inductance, it is recommended to place a solid copper plane, connected to source, one layer below the top layer (Die pad layer). This source plane serves as both a power plane for the main current and gate return and shown as the gold color plane in Figure 5. Further reduction in coupling between the gate-source circuit and drain-source circuit can be achieved by designing the two circuit's current's to be orthogonal with respect to each other. Using at least 2 oz thick copper for all layers will ensure the lowest possible connection resistance.

For lower voltage dies (40 V and 100 V) with small trace width and spacing specifications recommend for the land pattern [3], designers may need to consult with their board manufacturers to determine options to meet the all design requirements. In most cases, reducing the copper thickness to 1 oz will satisfy most board manufacturer's tolerance requirements.

The EPC9001 and EPC9002 series of demonstration boards have been designed using this technique [4,5].

Dual-sided termination PCB layout

When performance and cost are important factors in the design, a dual-sided terminated design is recommended. This design can be implemented on PCBs with 4 layers or more. Two examples for this layout method are shown in Figure 6. The first option is with the source terminal on the top (pad) layer and the drain one layer below. The second option is with the drain terminal on the top (pad) layer and the source connection one layer below. Power connection to the drain and source are routed on different layers of the PCB and terminate on both sides of the Die as shown in Figure 6. It is recommended that the drain and source terminals be connected using vias to additional layers to further enhance current carrying capability. The preferred via design is a 6 mil (150 μm) drilled hole diameter and a 8 mil (200 μm) annular ring for the low voltage devices (40 V and 100 V) and 8 mil (200 μm) drilled hole with 12 mil (300 μm) annular ring for medium voltage devices (200 V). Two vias per pad side are recommended and should be sufficiently spaced based on PCB design guidelines and common source inductance design limits. This design will tend to cluster the vias very close to each other and the designer needs to stagger the vias to prevent a tear zone from forming on the PCB. Alternatively, the designer can request the board manufacturer to rotate the PCB fiber grain of the PCB by 45° (This may add cost to the PCB).

To further reduce common source inductance, it is recommended to place a solid copper plane connected to gate return source one layer below the top layer (Die pad layer). Further reduction in coupling between the gate-source circuit and drain-source circuit can be achieved by designing the two circuit's current's to be orthogonal to each other as depicted in Figure 6. Using 2 oz thick copper for all layers will ensure the lowest possible connection resistance. The gate return need only be routed on one layer, leaving more room on other layers for high-current planes.

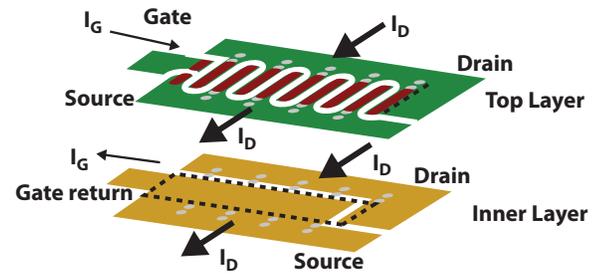


Figure 5: Example of a single-sided terminal layout configuration.

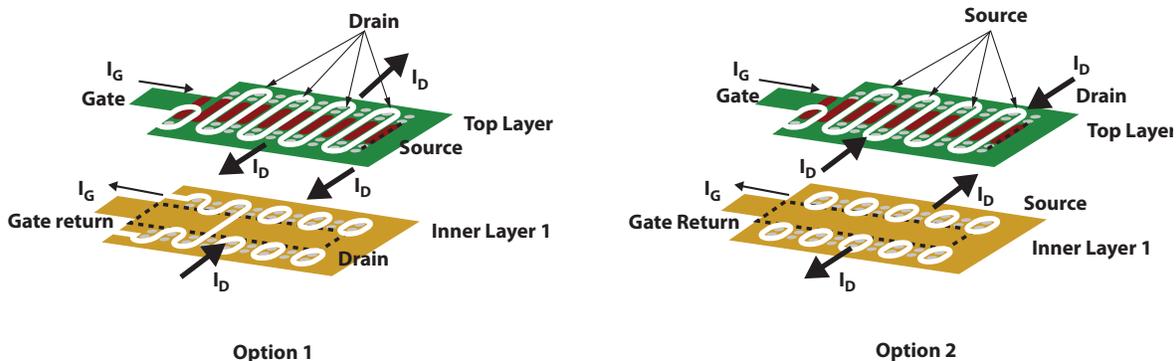


Figure 6: Example of a Dual-sided terminal layout configuration with 2 options for layer assignment.

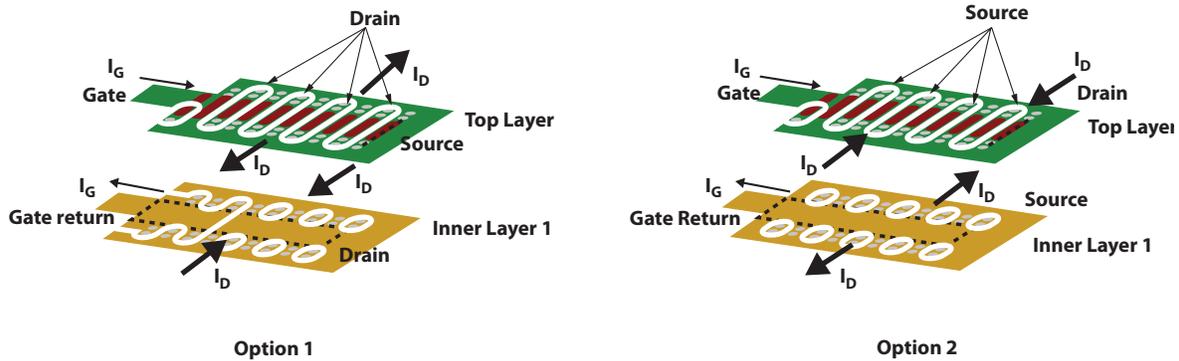


Figure 7: Example of a filled via dual-sided terminal layout configuration with 2 options for layer assignment.

Filled via dual-sided termination PCB layout

When performance drives the design, a filled via dual-sided terminated design is recommended. This can be implemented on PCBs with 4 layers or more. Two examples for this layout method are shown in Figure 7. The first option is with the source terminal on the top (pad) layer and the drain one layer below. The second option is with the drain terminal on the top (pad) layer and the source connection one layer below. Power connections to the drain and source are routed on different layers of the PCB and terminate on both sides of the die as shown in Figure 7. It is recommended that the drain and source terminals be connected using vias to additional layers in order to further enhance the current carrying capability. The recommended via design is a 6 mil (150 μm) drilled hole diameter and a 8 mil (200 μm) annular ring for the low voltage devices (40 V and 100 V) and 8 mil (200 μm) drilled hole with 12 mil (300 μm) annular ring for medium voltage devices (200 V). Two vias per pad side are recommended and should be sufficiently spaced based on PCB design guidelines and common source inductance design limits. This design will tend to cluster the vias very close to each other and the designer needs to stagger the vias to prevent a tear zone from forming on the PCB. Vias placed in the pad areas of the die need to be micro vias with a hole of 6 mils (150 μm) drilled and 8 mil (200 μm) annular ring diameter not to exceed the pad width and must be filled with either a non-conductive, or conductive filler (This may add to cost). Vias with holes located directly under the source, gate, or drain solder bars will cause wide variation in the die stand-off distance to the PCB. Variation in stand-off distance could (1) affect the user's ability to thoroughly clean between the FET and the PCB, (2) could add to die tilt variation, and (3) might reduce the transistor's temperature cycling performance.

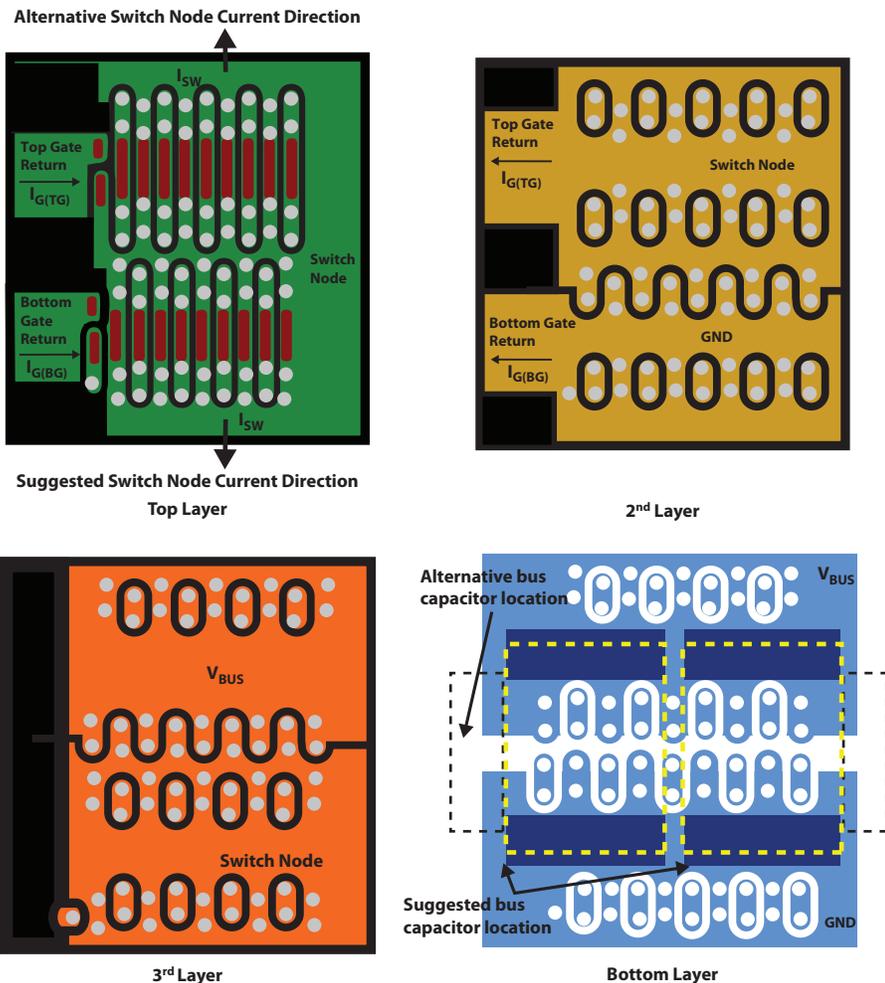


Figure 8: Example of a half-bridge layout using 4-layer PCB.

To further reduce CSI, it is recommended to place a solid copper plane, connected to gate return source, one layer below the top layer (Die pad layer). Further reduction in coupling between the gate-source circuit and drain-source circuit can be achieved by designing the two circuit's current paths to be orthogonal with respect to each other as depicted in Figure 7. Using 2 oz thick copper for all layers will ensure the lowest possible connection resistance. The gate return need only be routed on one layer, leaving more room on other layers for high current planes.

Interconnecting the devices PCB layout

Designs such as half bridge topologies will require devices to be interconnected with each other. The recommended method to interconnect two devices is shown in Figure 8 based on a 4 layer design. The copper thickness needs to be maximized to limit resistive losses and improve thermal spreading (2 oz copper on outer layers is recommended). In this layout example, the source connection of each part is brought underneath to act as an E-field shield (especially under the device gate structure) and minimize additional parasitic gate drain capacitance (C_{gd}). Every source is connected through Layer Two to the shield that now doubles as the gate drive return path. Drain connections are brought out on the third layer. The tradeoff is that to achieve a much lower common source inductance and overall layout inductance, the geometry requires increased parasitic capacitance – in particular output capacitance (C_{oss}) – as there is still the need to minimize the parasitic C_{gd} . The main supply bus decoupling capacitors can be located directly beneath the device pair, or to one side (see Figure 8) and as close as possible to minimize loop inductance. The gate driver output needs to be located as close as possible to the gates of their respective FETs. The long sides of the FETs need to be placed side by side to further reduce inter-device inductance.

PARALLELING

Paralleling switching devices enables increased power performance for switching converters. Paralleling eGaN FETs poses many new challenges as these devices can be switched ten times faster than commercial MOSFETs. These challenges discussed in detail in references [6] and [7] where recommendations are made to ensure the highest possible performance from a paralleled eGaN FET switch converter.

THERMAL CONSIDERATIONS

Due to the fundamentally lower eGaN FET on-resistance [8] per die area, these devices are only a fraction of the size of an equivalent on-resistance power MOSFET die, and therefore have a higher equivalent thermal resistance. However, eGaN FETs also have a much lower FOM and will therefore have offsetting lower switching power losses.

Can this improvement in power loss make up for the higher thermal resistance?

To answer this question we need to look at two common scenarios; (1) devices mounted as “flipchips” on a printed circuit board without additional heatsinking, and (2) devices mounted with dual-sided cooling.

SINGLE-SIDED COOLING:

eGaN FETs are constructed on a very thin layer of heterojunction material on top of a standard silicon wafer and when mounted directly onto PCBs without any backside cooling behave thermally like any similarly mounted silicon device. The variables needed to completely understand the resulting thermal performance are, (1) PCB copper area, (2) Copper thickness, (3) PCB material, and (4) airflow over the device and PCB.

Reference [9] tests several industry standard packages mounted directly onto FR-4 PCB material. Measurements were made on one square inch, 2-ounce Cu, and on devices with only enough Cu to make electrical contact to the leads. This methodology separated the effect of device footprint from the cooling that comes from the copper on the PCB. Relatively little impact was seen when different packages were mounted on one square inch Cu (the minimum R_{JA} was 18 °C/W for a D²PAK and the maximum was 34 °C/W for an SO-8) because the dominant thermal resistance factor was the heat dissipating through the PCB. Consistent with these tests, it is estimated that R_{JA} for eGaN FETs mounted to one square inch of 2 ounce Cu should be about 40 °C/W in still air [10,11,13]. This performance can be improved significantly with increased airflow.

DOUBLE-SIDED COOLING:

To determine the best possible top-side cooling for EPC’s eGaN FETs, the setup in Figure 9 was constructed. $R_{DS(ON)}$ was used as the temperature sensitive parameter and the heatsink was water cooled for these “best-case” thermal measurements. Across the family of eGaN FETs, the data suggests a 12-14 °C-mm² normalized R_{JA} when cooling is primarily through the silicon substrate beneath the eGaN FET active area. Under these conditions, large area eGaN FETs (EPC2015, EPC2001, and EPC2010) have an R_{JC} of about 2 °C/W and the small area FETs (EPC2014, EPC2007, and EPC2012) have an R_{JC} of about 8 °C/W.

Practical implementations of double sided cooling are certainly less elaborate than the one shown in Figure 9, but can result in higher final thermal impedance. In Figure 10, one such configuration where two devices are simultaneously cooled by one heat sink is illustrated. In the case where multiple die are placed under the same heatsink, however, care must be taken to avoid mechanical damage from uneven pressure on die that might be slightly tilted

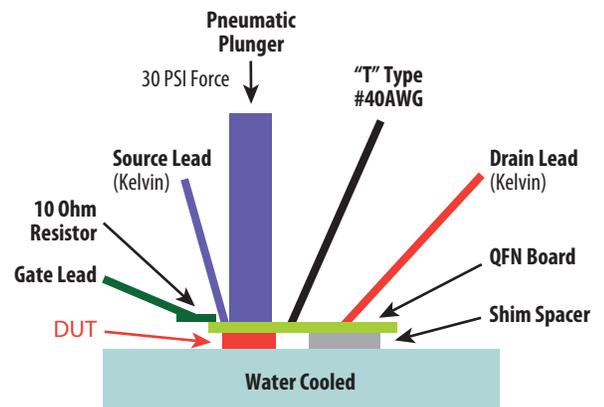


Figure 9: Test setup for measuring EPC eGaN FET “best-case” thermal resistance.

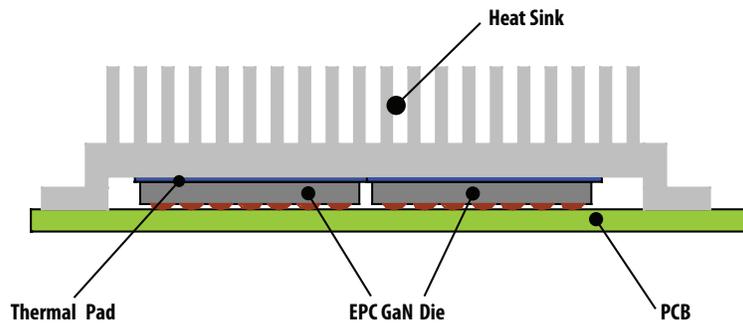


Figure 10: Dual die under one heat sink with thermal pad.

or at different heights off the PCB. Thermally conductive materials such as from 3M [11], Dow Corning [12], or Bergquist [13] have been successfully used to double-side cool multiple die under one heatsink attaining $6\text{ }^{\circ}\text{C/W}$ into the heatsink and $15\text{ }^{\circ}\text{C/W}$ into the board [15]. Thermal models for all of our devices are also available from our website, www.EPC-co.com. Because the FET substrates must be connected to source potential, the heatsink, must be electrically isolated from at least one of the die or thermal interface material must also be an electrical insulator.

SUMMARY

EPC's eGaN FETs give the designer a whole new spectrum of performance compared with silicon power MOSFETs. To extract full advantage from this new technology, designers must understand how to design cost-effective drive circuitry that works on a cost-effective PCB. In this paper, we looked at gate drive requirements, layouts, and thermal design considerations that are important to final system performance and reliability.

References:

- [1] EPC2001 Datasheet: http://epc-co.com/epc/documents/datasheets/EPC2001_datasheet_final.aspx
- [2] Fairchild Semiconductor AN-7019, "Limiting Cross-Conduction Current in Synchronous Buck Converter Designs", <http://www.fairchildsemi.com/an/AN/AN-7019.pdf#page=1>
- [3] Alana Nakata, "Assembling eGaN FETs", http://epc-co.com/epc/documents/product-training/Appnote_GaNassembly.pdf
- [4] EPC9001 demo board at: <http://epc-co.com/epc/Products/DemoBoards.aspx>
- [5] EPC9002 demo board at: <http://epc-co.com/epc/Products/DemoBoards.aspx>
- [6] J. Strydom, M. deRoos, "Shootout Volume 5: Paralleling eGaN® FETs", Power Electronics Technology, October 2011
- [7] A. Lidow, J. Strydom, M. deRoos, Y. Ma, "GaN Transistors for Efficient Power Conversion", Power Conversion Press, 2012, Chapter 4.
- [8] Steve Colino, Robert Beach, "Fundamentals of Gallium Nitride Power Transistors", http://epc-co.com/epc/documents/product-training/Appnote_GaNfundamentals.aspx
- [9] International Rectifier, <http://www.irf.com/technical-info/whitepaper/thermalpcim02.pdf>
- [10] Edgar Abdoulin, Steve Colino, Alana Nakata, "Using Enhancement Mode GaN-on-Silicon Power Transistors", http://epc-co.com/epc/documents/product-training/Using_GaN_r4.aspx
- [11] 3M pads : http://solutions.3m.com/wps/portal/3M/en_WW/electronics/home/productsandservices/products/TapesAdhesives/ThermalInterface/
- [12] Dow Corning Pads: <http://www.dowcorning.com/content/etronics/etronicspadsfilm/>
- [13] Bergquist Pads: http://www.bergquistcompany.com/thermal_materials/gap_pad/pdfs/gap-pad-vo-soft/PDS_GP_VOS_12.08_E.pdf
- [14] John Worman and Yanping Ma, "Thermal Performance of EPC eGaN FETs", http://epc-co.com/epc/documents/product-training/Appnote_Thermal_Performance_of_eGaN_FETs.aspx
- [15] Johan Strydom, "The eGaN® FET- Silicon Power Shoot-Out Volume 8: Envelope Tracking", http://powerelectronics.com/power_semiconductors/gan_transistors/egan-fet-silicon-power-shoot-out-volume-8-0430/