




The eGaN[®] FET
Journey Continues

Paralleling eGaN[®] FETs for Efficient Power Conversion


Alex Lidow and Michael de Rooij
Efficient Power Conversion Corporation

- **What happens when eGaN[®] FETs are paralleled?**
- **What are the best solutions?**
- **Introducing the Parallel Impact Figure (PIF)**
- **Layout Do's and Don'ts**
- **Summary**

Half-Bridge topologies


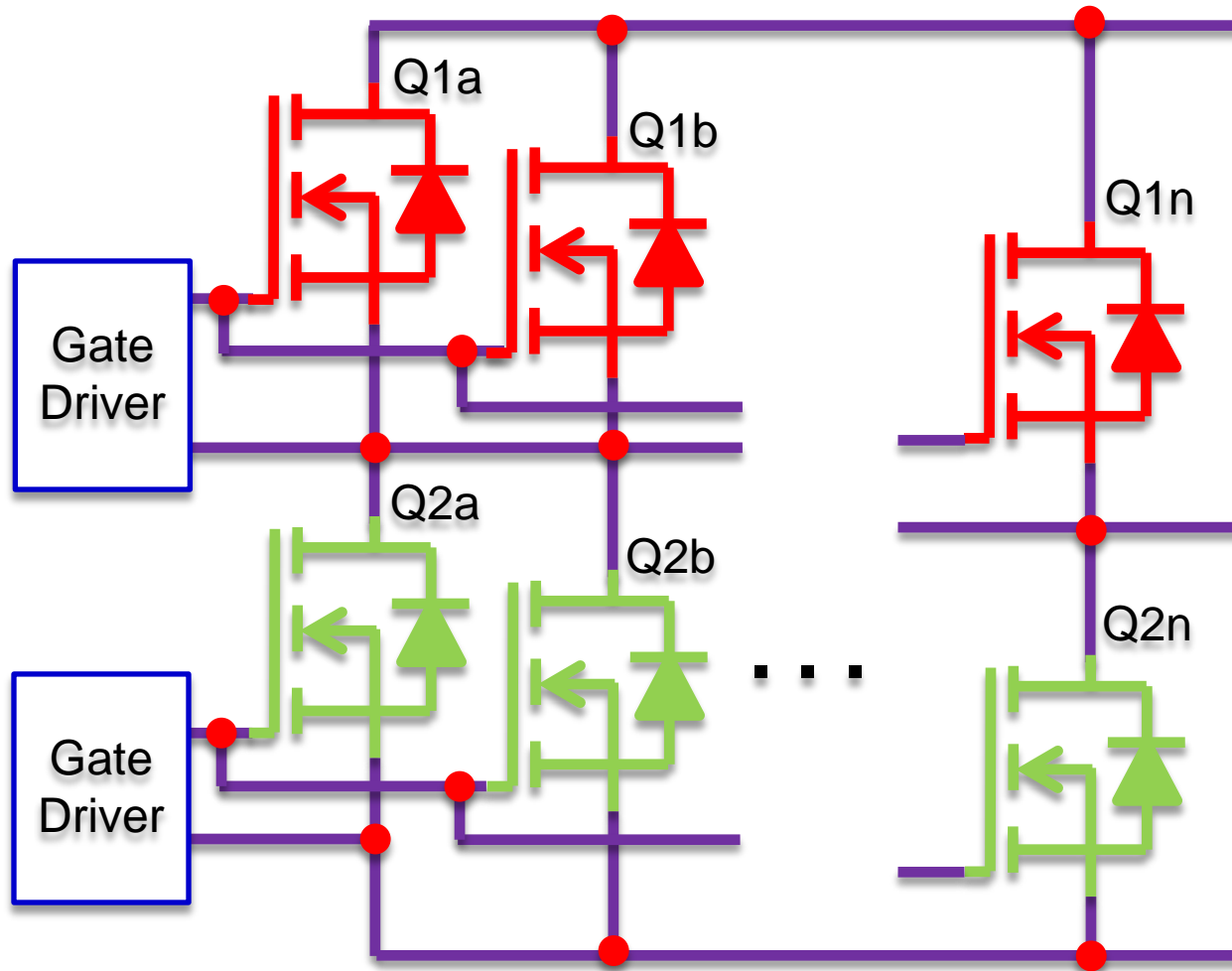


Switching Dynamics

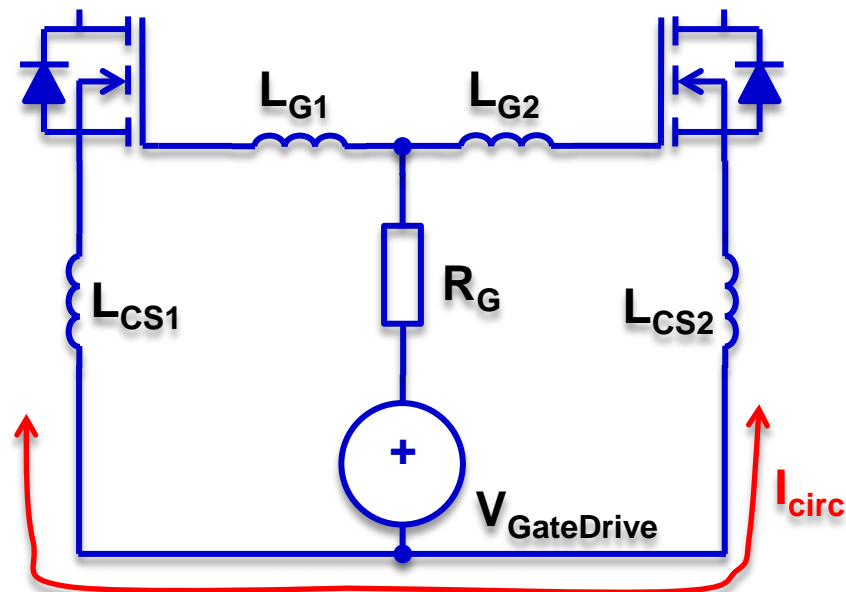



Switching Dynamics – Turn On

FET Turn-On

 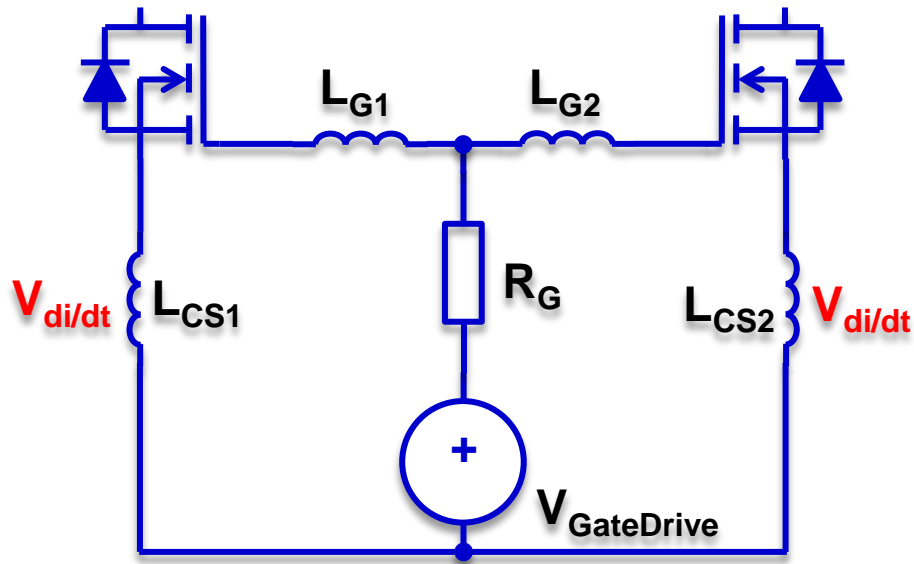


Switching Dynamics – Turn Off

FET Turn-off

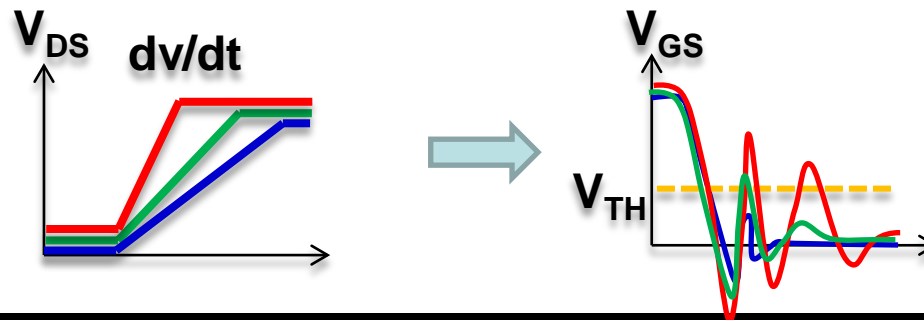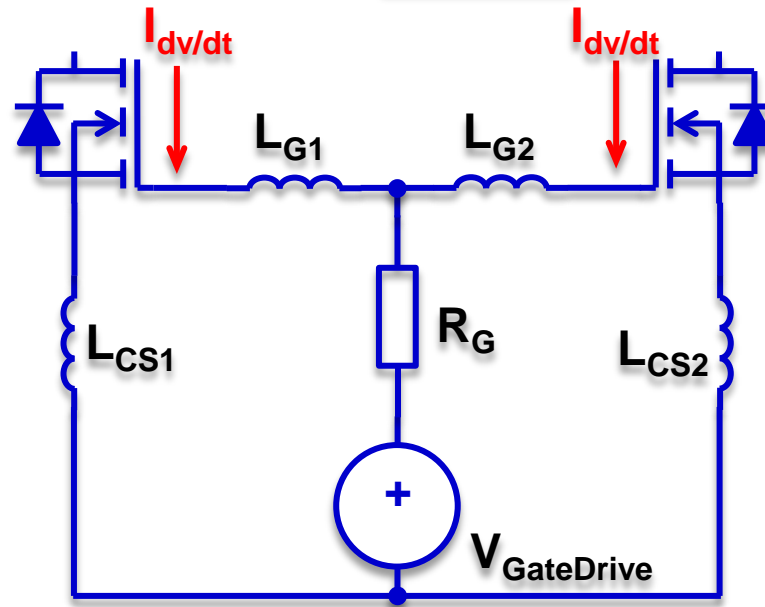

Half Bridge Layout Evaluations

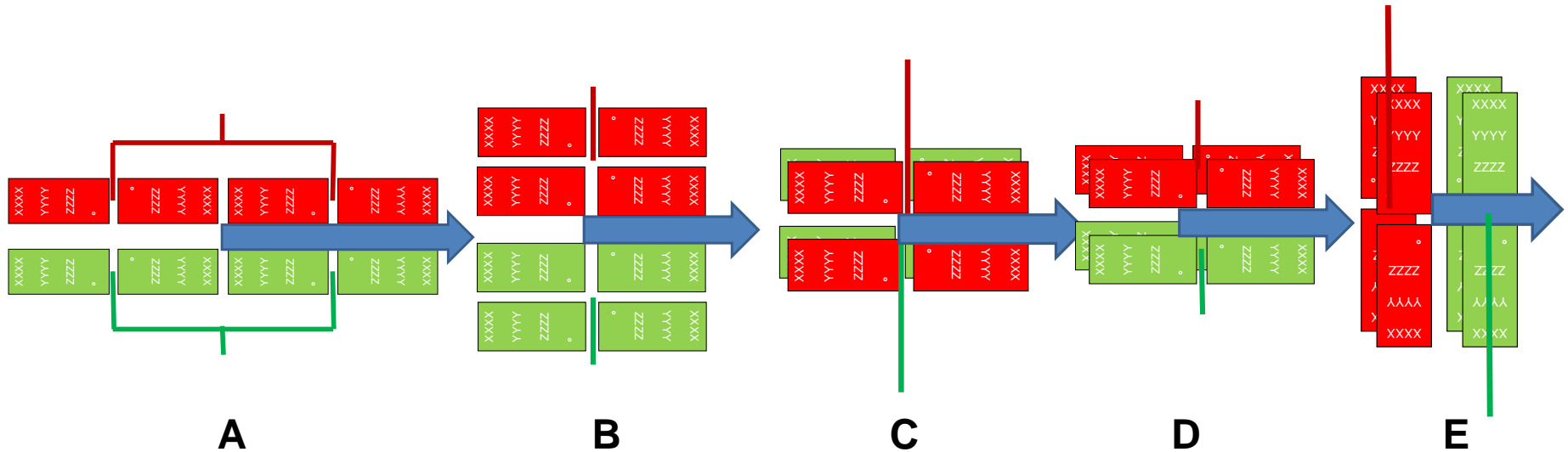


Single Component Sided

Double Component Sided

- **Based on dv/dt and di/dt immunity**
- **Normalizes evaluations relative to a single FET**
- **Can be used to predict switching performance**


$$PIF_n = \frac{\frac{dv_1}{dt} + \frac{di_1}{dt}}{\frac{dv_n}{dt} + \frac{di_n}{dt}}$$

PIF for Half Bridge Layouts

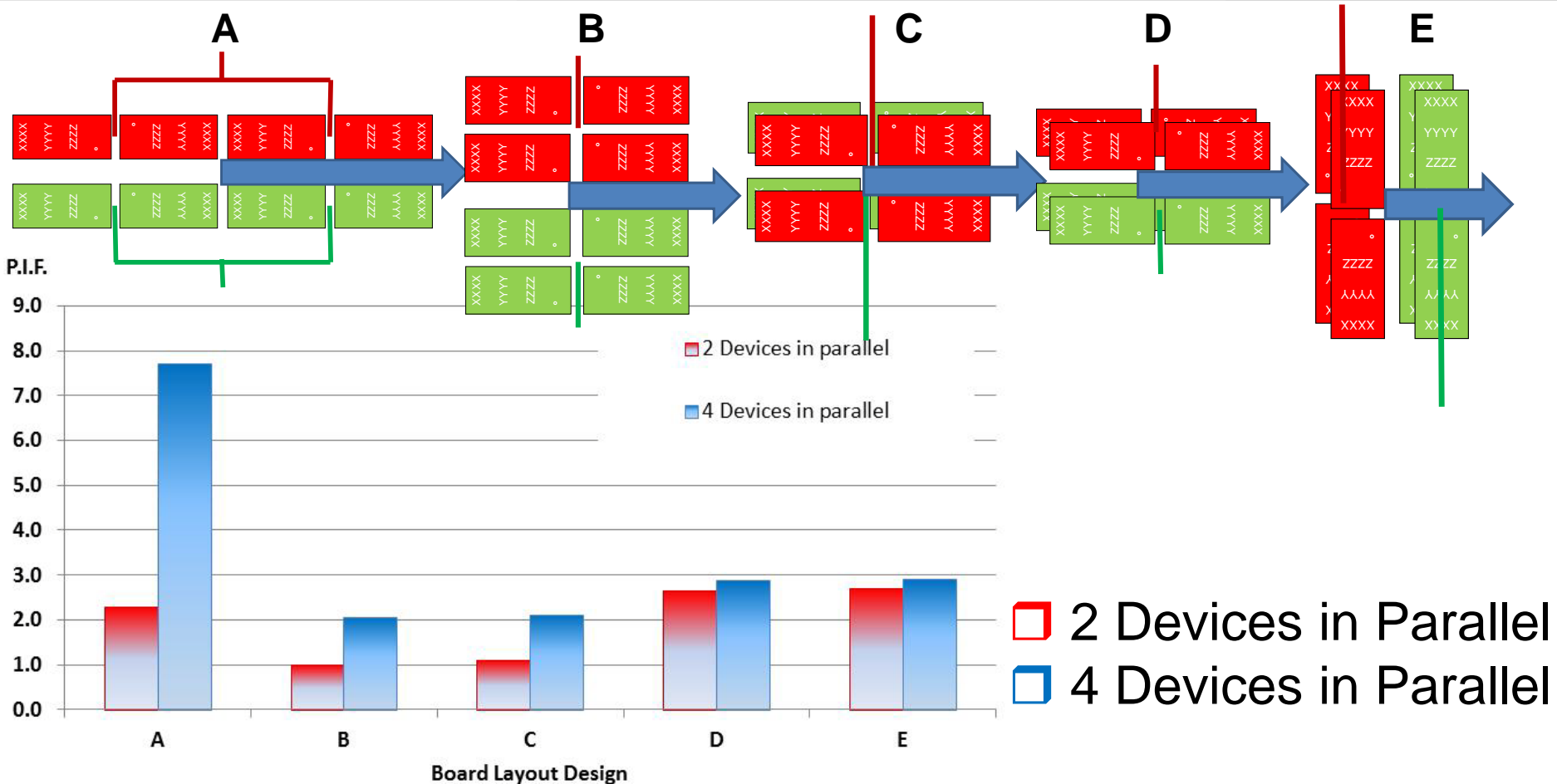


□ 2 Devices in Parallel
□ 4 Devices in Parallel

Best Layout Configuration

 


Layout Recommendation

 Half Bridge
Layout To
Minimize
And
Balance
Source
Inductance




Into The Drains

 


Layout Recommendation

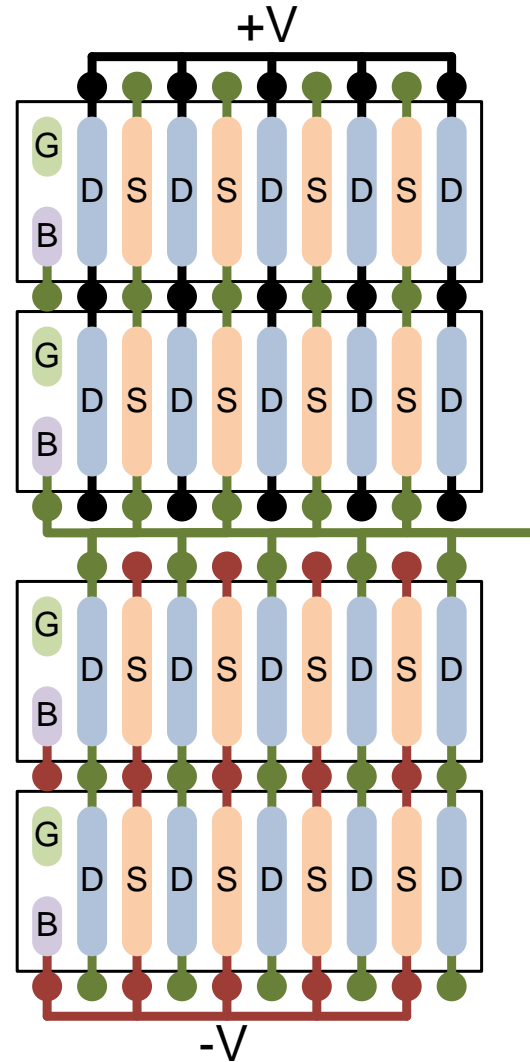Half Bridge
Layout To
Minimize
And
Balance
Source
Inductance




To The Drains
From Sources

 

Layout Recommendation

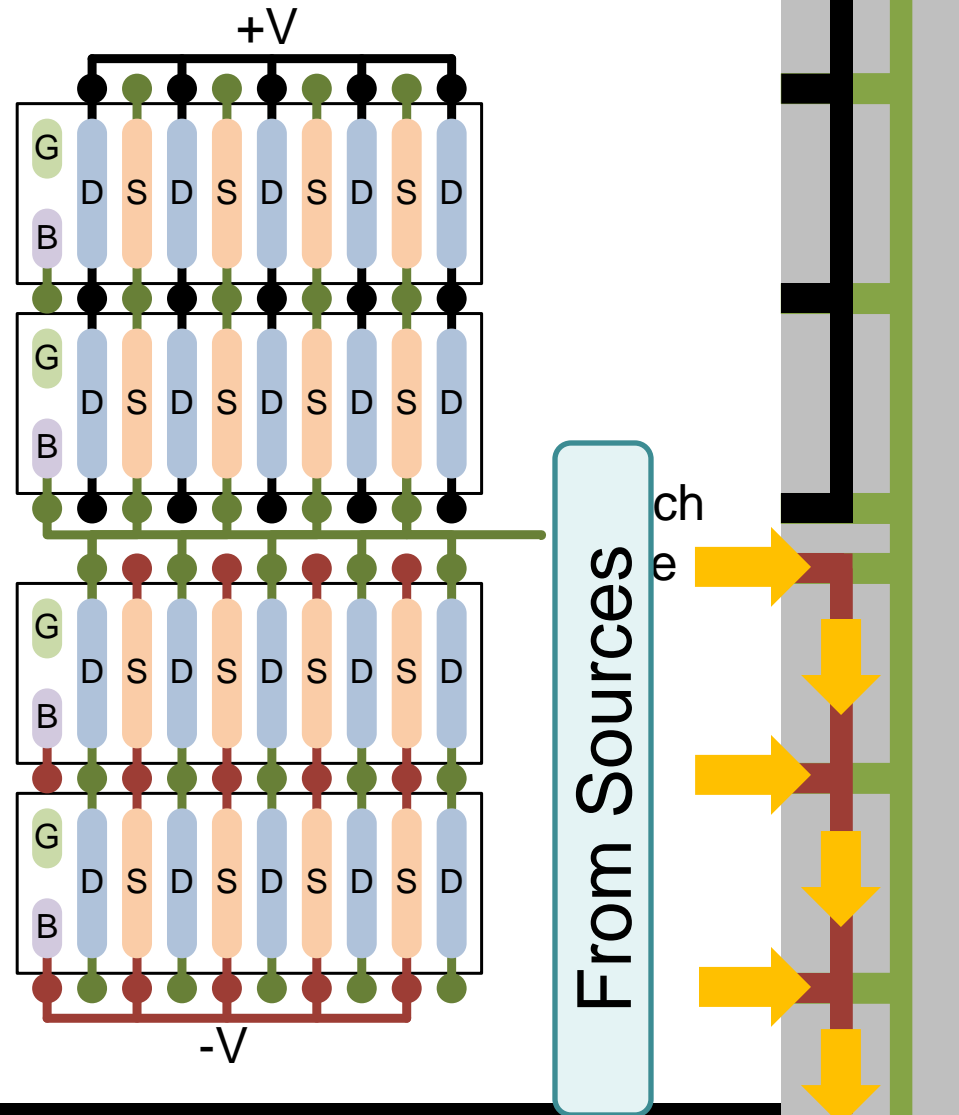
Half Bridge
Layout To
Minimize
And
Balance
Source
Inductance



Layout Recommendation

Use Lots Of Vias To Stitch The Contacts To Inner Planes

And Balance Source Inductance

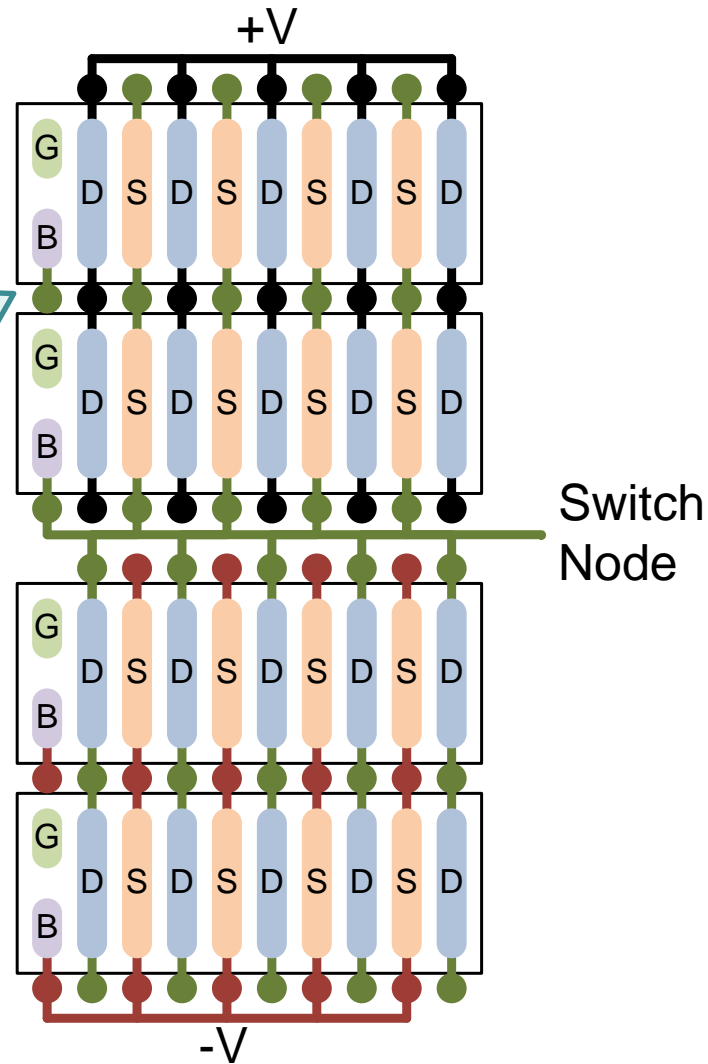

Layout Recommendation: Gates


Gate Return Planes
Connect To At Least
First Set Of Source Vias

High Gate


High Gate Return

Low Gate


Low Gate Return

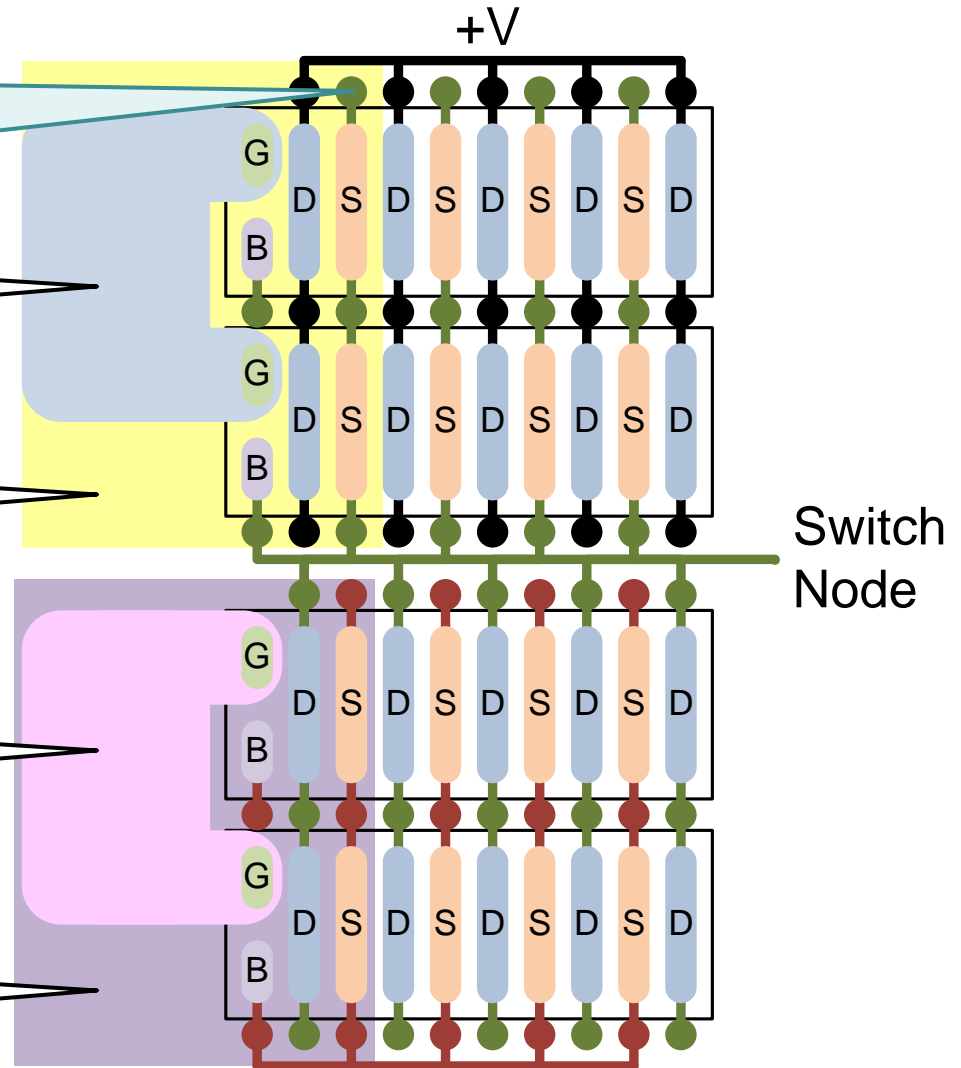


Layout Detail

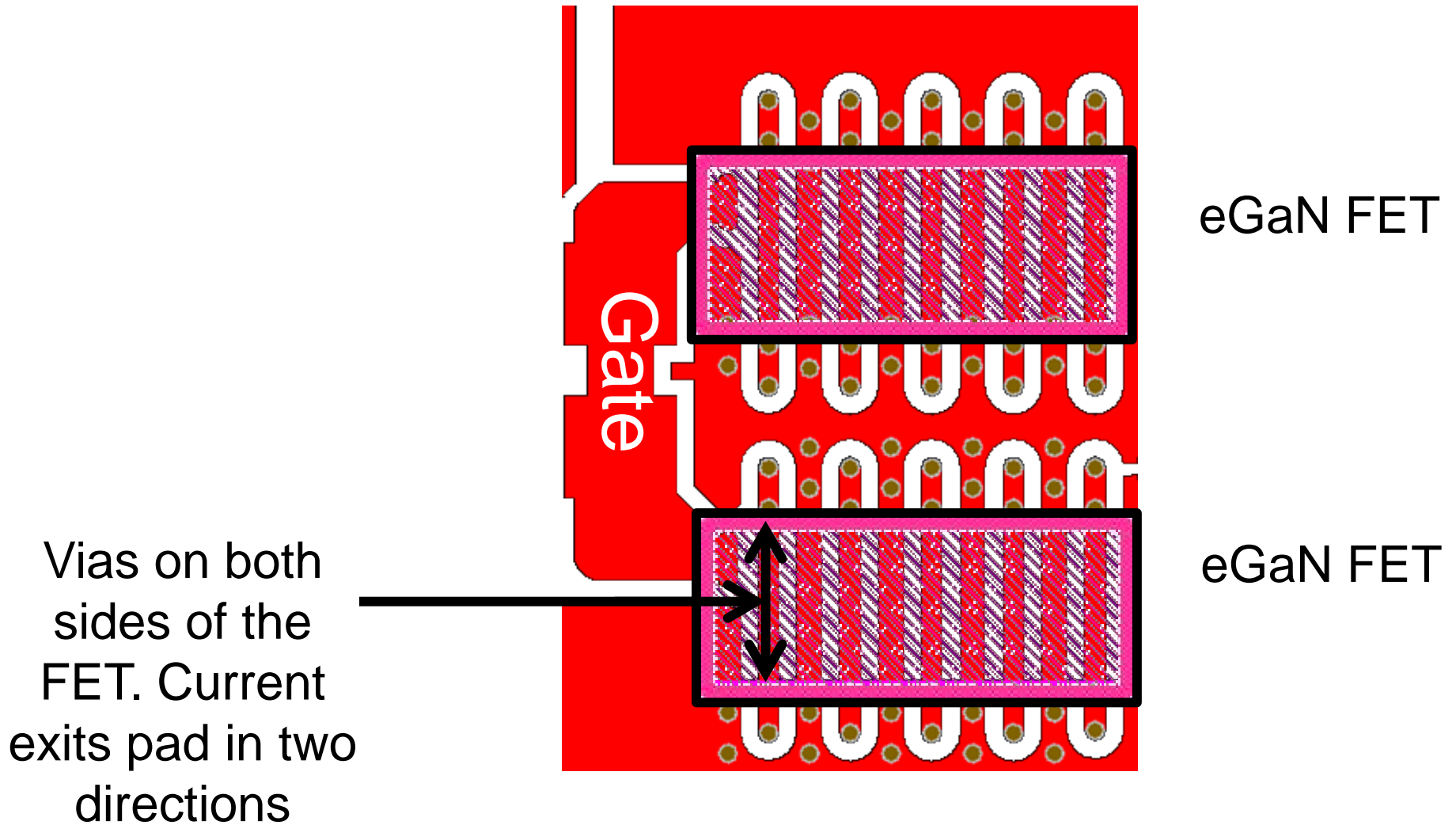



PIF for Best Layout

 

Board Layout Design B

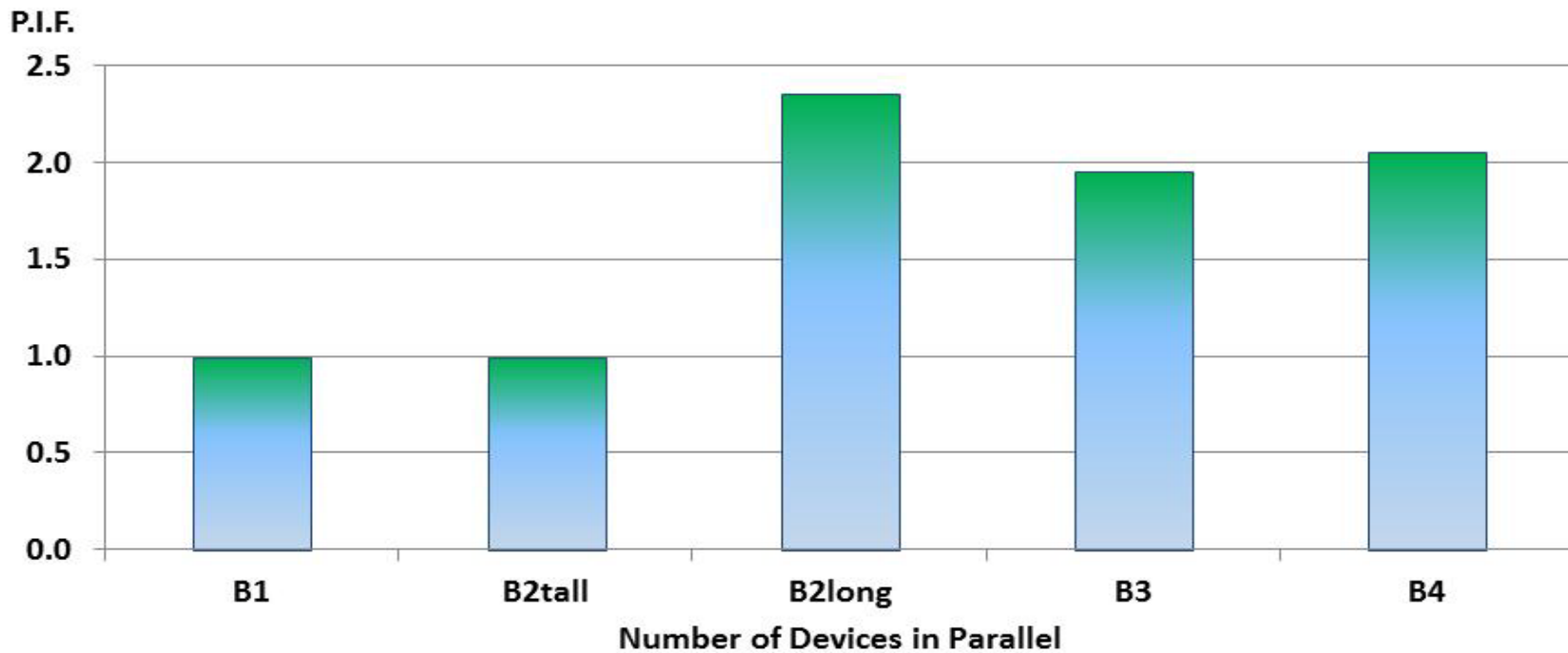


Parallel eGaN FET Buck Converter

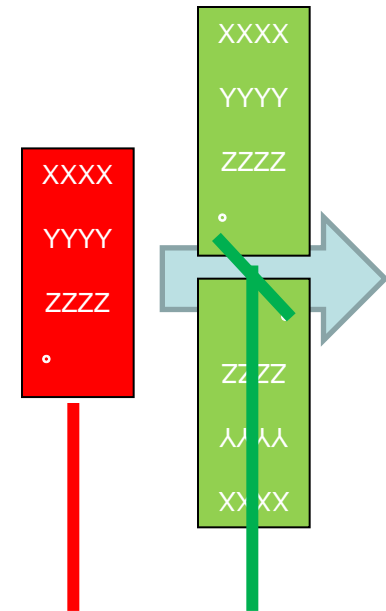 

Parallel eGaN[®] FET Buck Converter

Efficiency at 1 MHz

 


$$12 V_{IN} - 1.2 V_{OUT}$$

Half Bridge Layout *Best* Practice

4


6

8

 


Double Component Sided

Single Component Sided

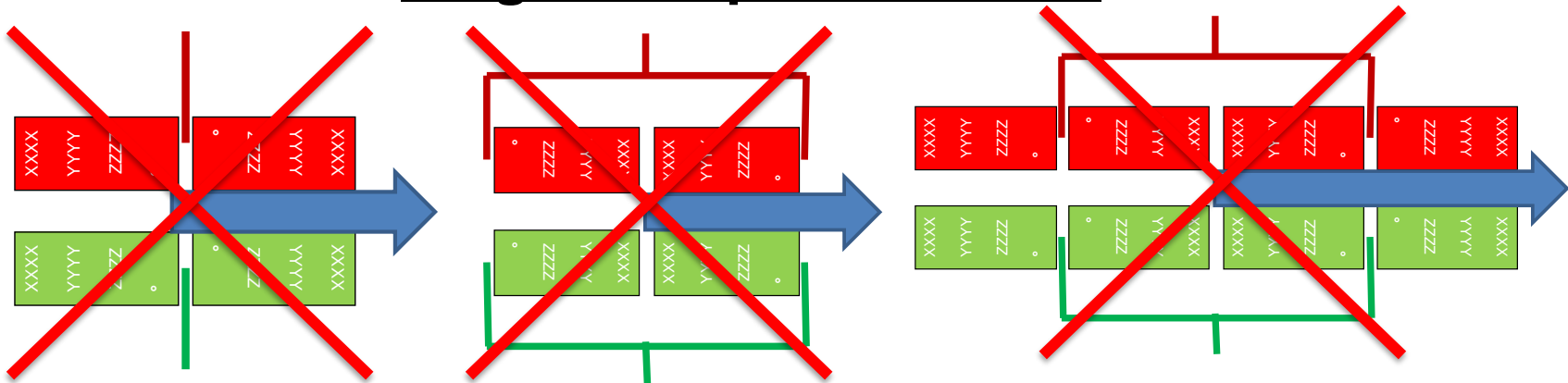

Double Component Sided

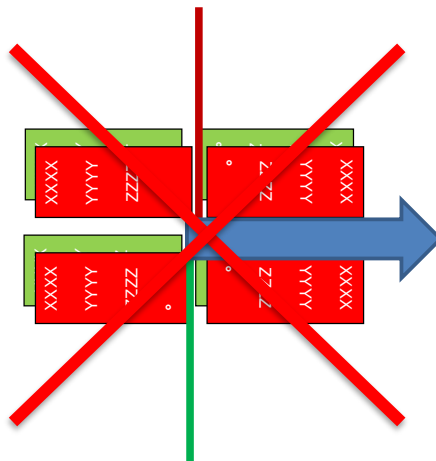

- **eGaN FETs can be paralleled**
- **Two devices can be paralleled without loss of performance**
- **The PIF is a useful tool for comparing layouts and predicting switching performance**



*The end of the road
for silicon.....*

*is the beginning of
the eGaN FET
journey!*