



designwest

center of the engineering universe

GaN Transistors for Efficient Power Conversion

April 22-25, 2013

McEnery Convention Center

San Jose, CA

www.ubmdesign.com



Agenda



- How GaN works
- Electrical Characteristics
- Design Basics
- Design Examples
- Summary




How GaN Works

The Ideal Power Switch



 - Block Infinite Voltage
- Carry Infinite Current
- Switch In Zero Time
- Zero Drive Power
- Normally Off




Power Switch Wish List



- Faster
- Lower Conduction Loss
- Less Capacitance
- Smaller
- Lower Cost

Material Comparison

 


Theoretical on-resistance vs blocking voltage capability for silicon, silicon-carbide, and gallium nitride


GaN + AlGaN



Spontaneous Polarization

 


GaN Magic

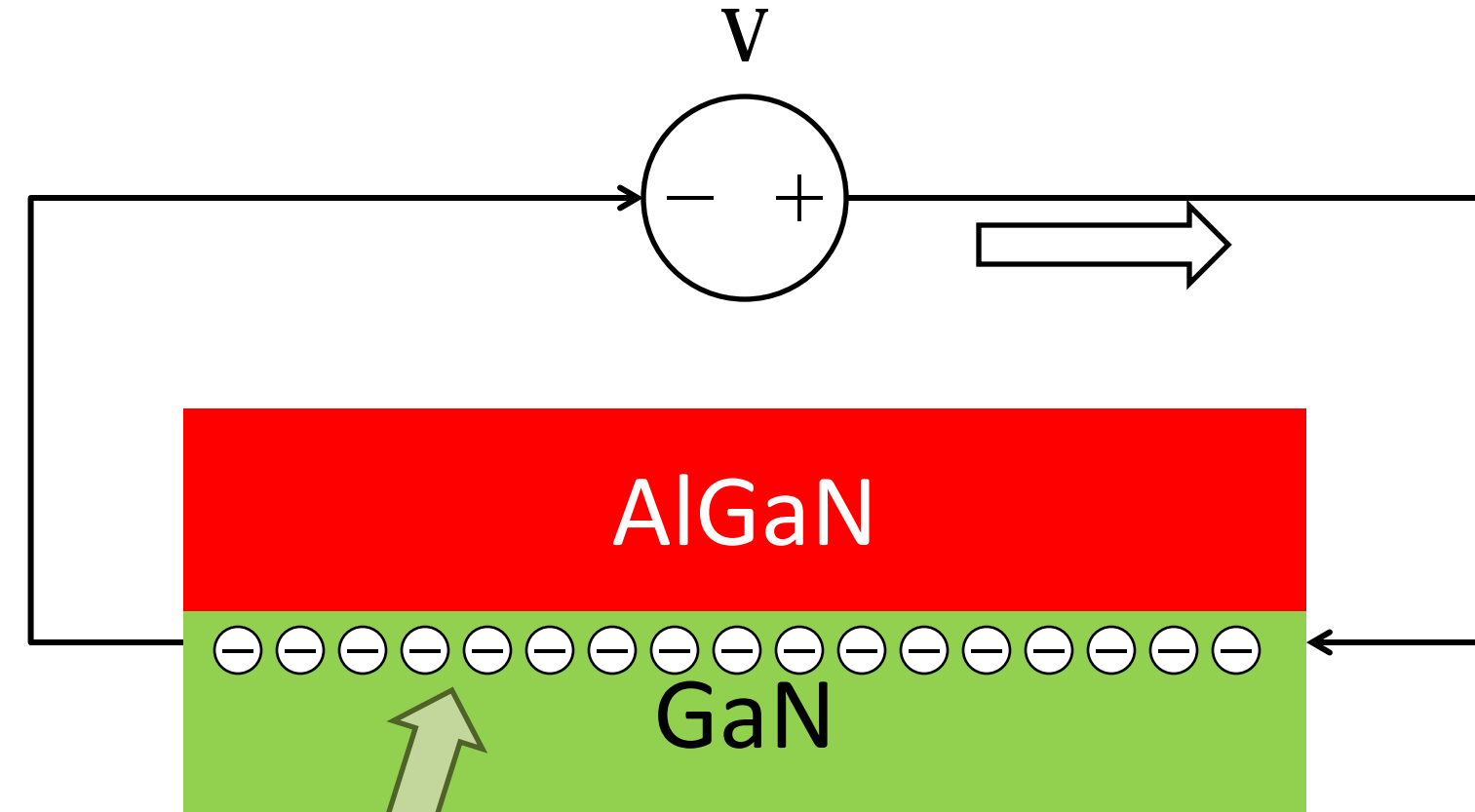


“2D Electron Gas”


GaN Switch

 

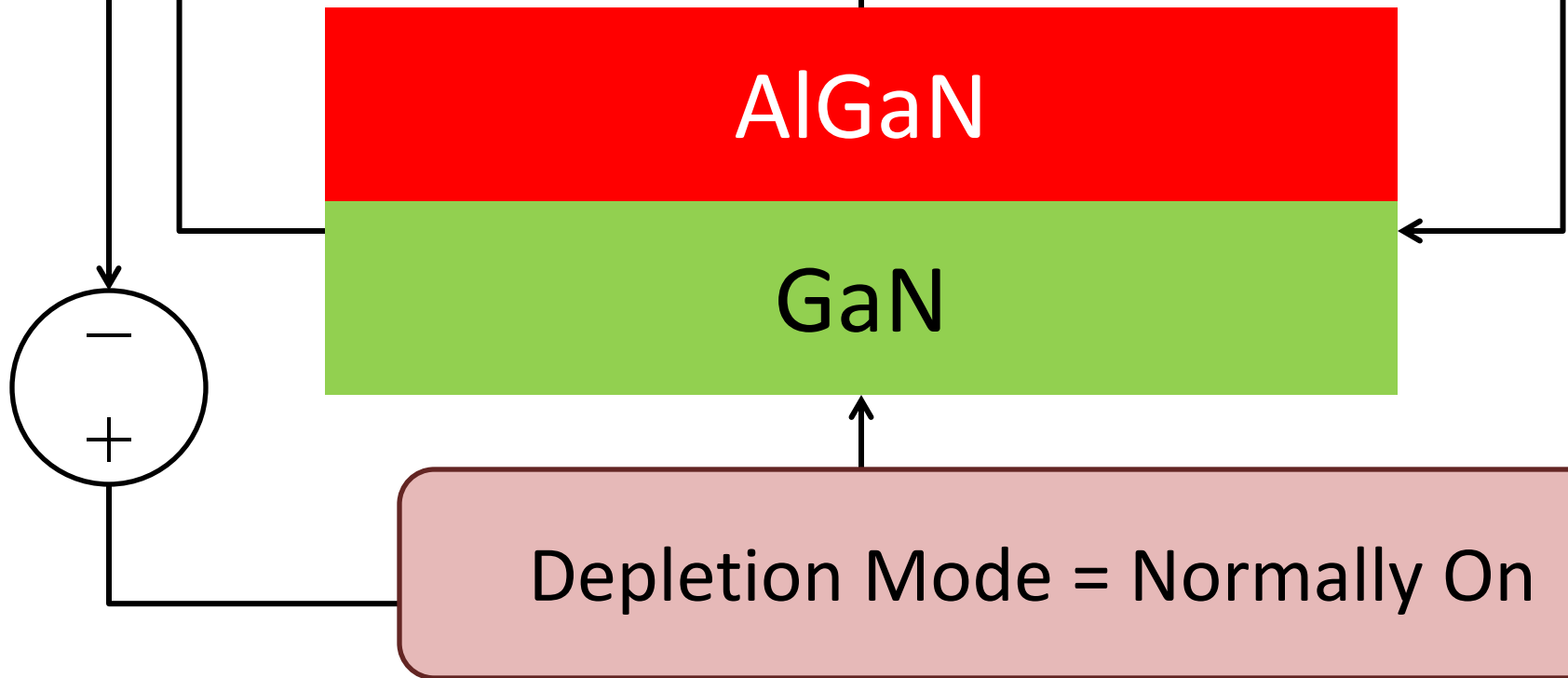Now we have a switch
That has high voltage blocking
capability,
low on resistance, and is
very, very fast.



Device Construction Concept

 


Early substrate materials: SiC and Sapphire
Are expensive and hard to manufacture. Silicon
substrates are much lower cost and allow
fabrication in a standard CMOS Fab.


What About Normally Off Devices?



 - True enhancement mode GaN HFETs have been around for years
- There are various methods for dissipating the electron gas under the gate




Enhancement Mode

 


A positive voltage from Gate-To-Source establishes an electron gas under the gate

State of the Art

 


Theoretical on-resistance vs blocking voltage capability for silicon, silicon-carbide, and gallium nitride

Body Diode?

 


A positive voltage from Gate-To-Drain also establishes an electron gas under the gate


eGaN[®] FET Reverse Conduction

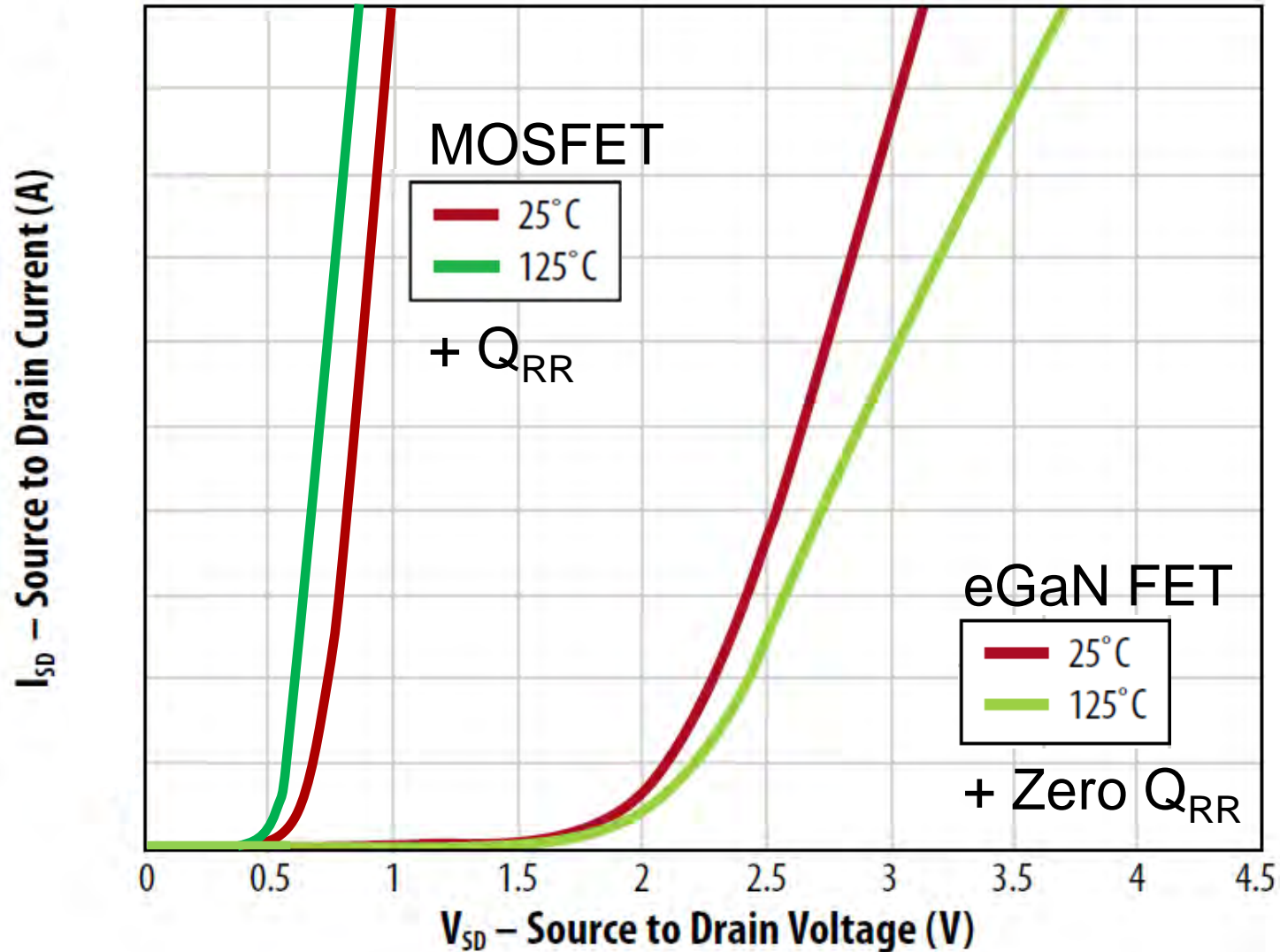

Threshold vs. Temperature

 

MOSFET Transfer Characteristics

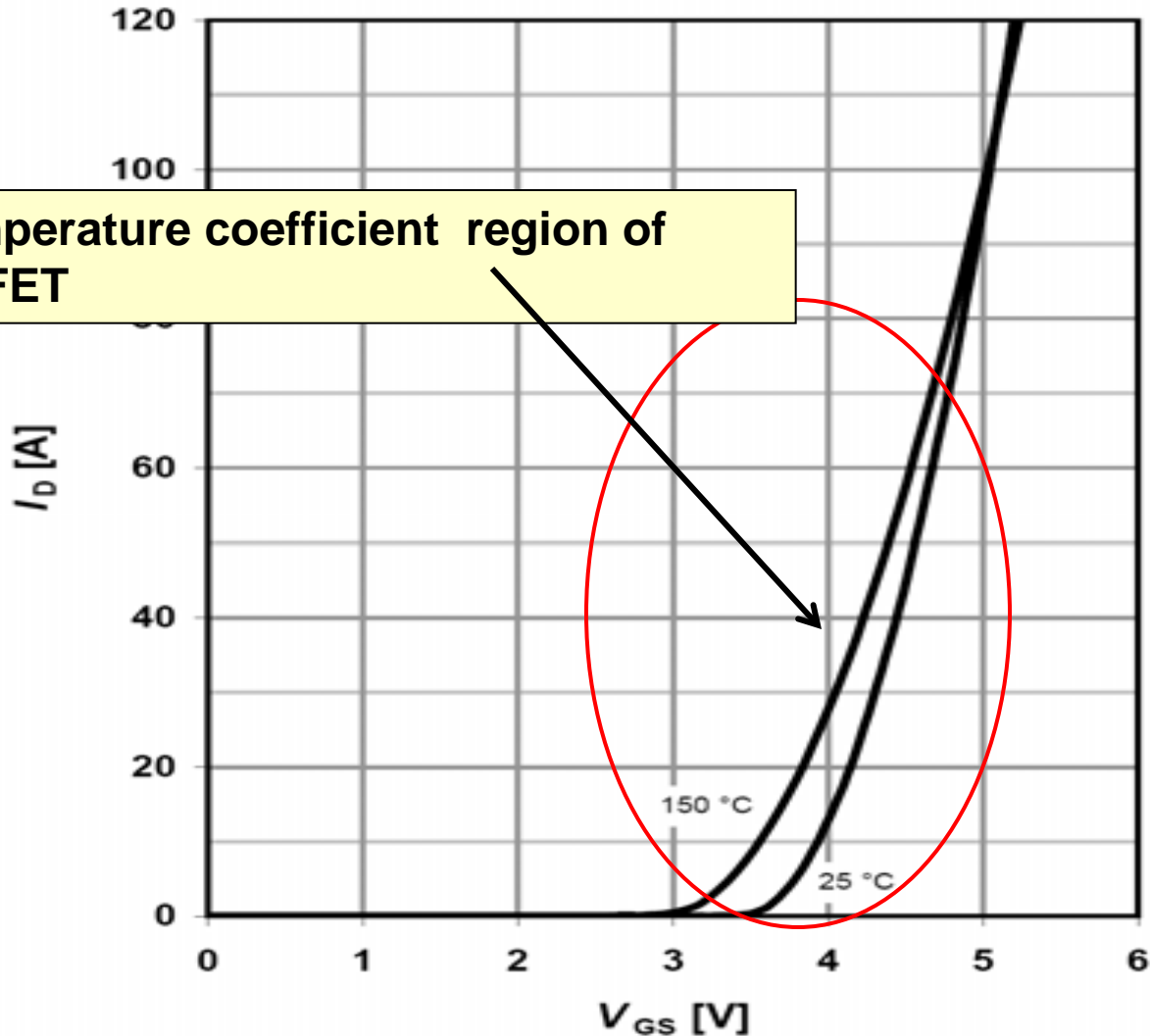


Negative temperature coefficient region of silicon MOSFET

eGaN[®] FET Transfer Characteristics




EPC2001

 

eGaN[®] FET Safe Operating Area



 
**EPC2001: MAXIMUM FORWARD BIAS
SAFE OPERATING AREA**




eGaN[®] FET Safe Operating Area



 
**EPC2001: MAXIMUM FORWARD BIAS
SAFE OPERATING AREA**



eGaN[®] FET Capacitances

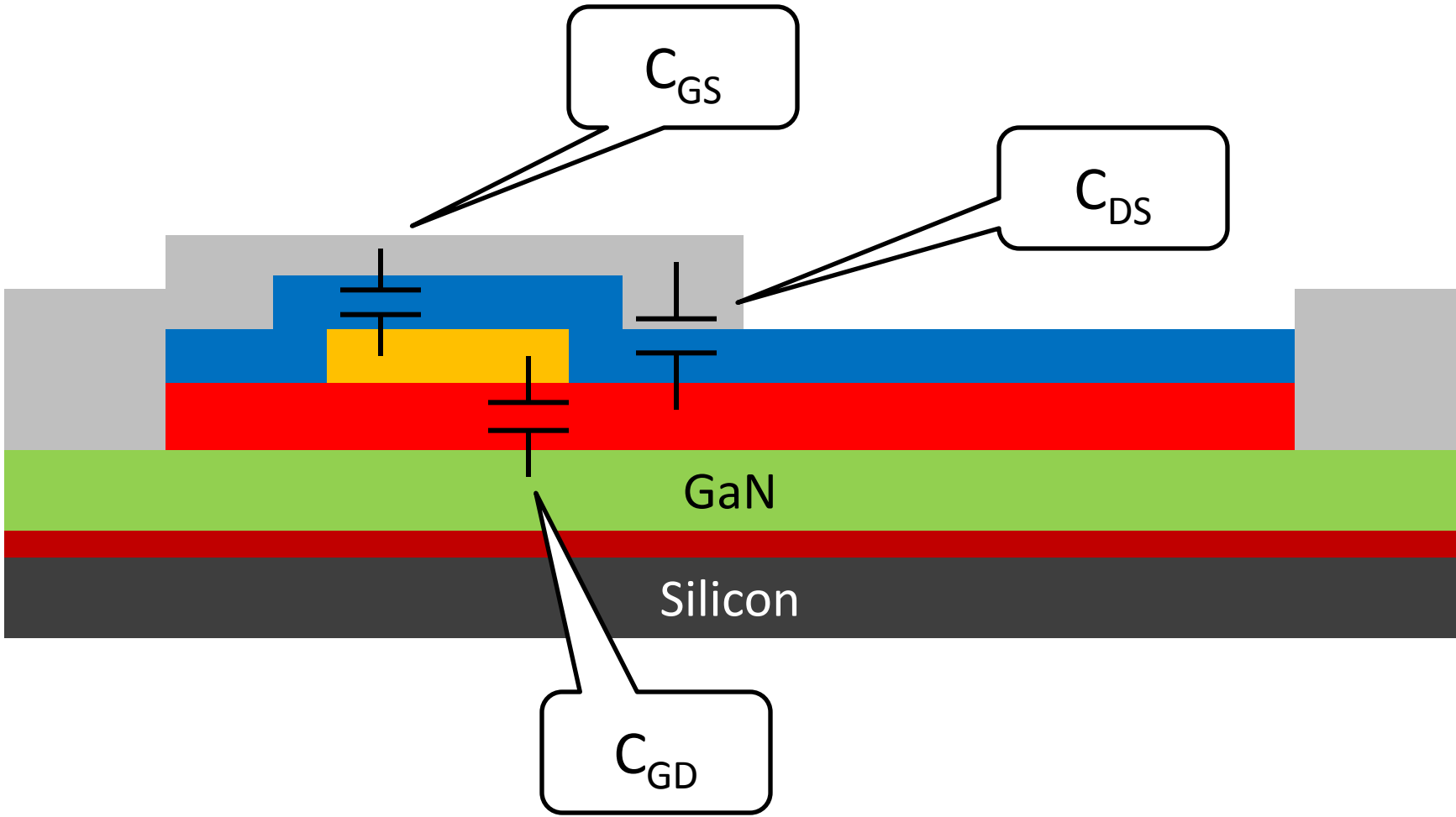

Total Gate Charge

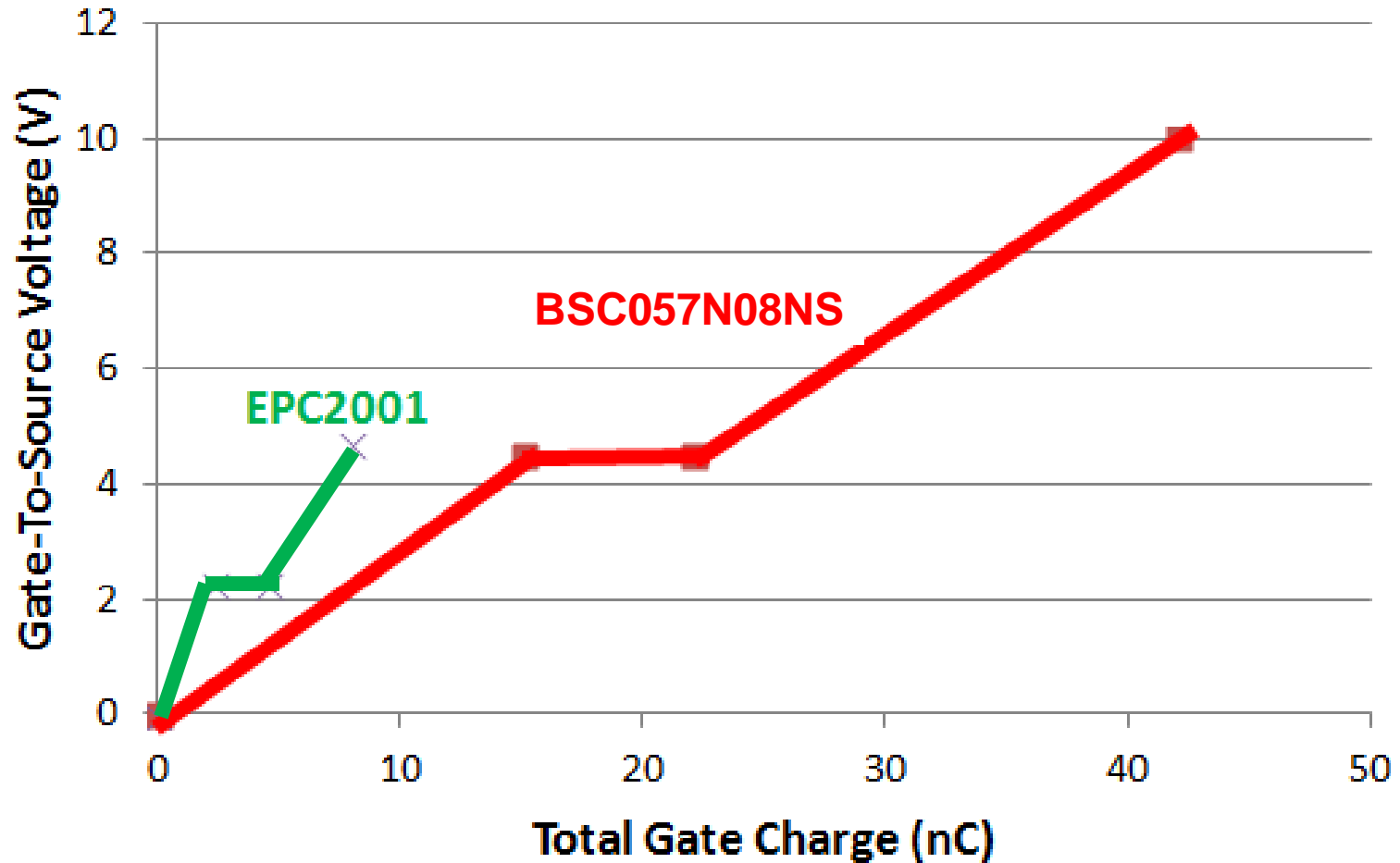


EPC2001 = 100 V, 5.6 m Ω typ

BSC057N08 = 80 V, 4.7 m Ω typ

Figure of Merit


 
$$\text{FOM} = R_{\text{dson}} \times Q_{\text{g}} (100\text{V})$$



eGaN[®] FET Loss Mechanisms



Like A MOSFET

- I^2R Conduction Loss
- Capacitive Switching Losses
- Gate Drive Losses
- $V \times I$ Switching Loss

Not Like A MOSFET

- High Reverse Conduction Loss
- No Body Diode Reverse Recovery Loss

eGaN[®] FET Loss Mechanisms



Like A MOSFET

- I^2R Conduction Loss
- Capacitive Switching Losses
- Gate Drive Losses
- $V \times I$ Switching Loss



Not Like A MOSFET

- High Reverse Conduction Loss
- No Body Diode Reverse Recovery Loss




Can be much, much better than
comparable silicon MOSFET

Package Wish List




- Low parasitic resistance
- Low parasitic inductance
- Low thermal resistance
- Small size
- Low cost

Flip-Chip LGA Construction

 

**Absolute minimum
lead resistance and inductance!**

LGA Construction

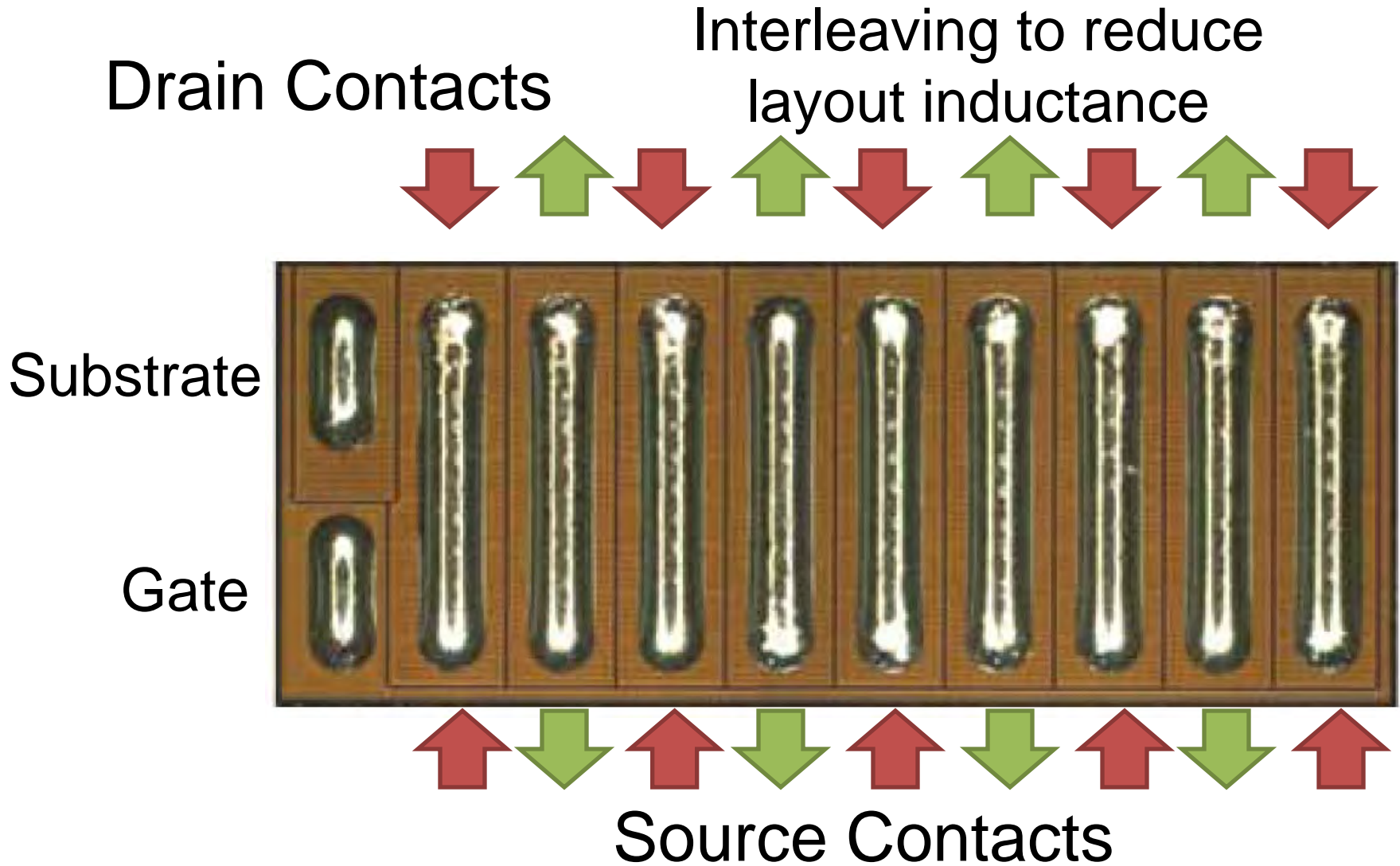

Size Comparison – 200 V



eGaN FET



5.76 mm²

D-PAK



65.3 mm²

Drawn To Scale

Key Applications




- Wireless Power Transmission – GaN Enabled
- RF DC-DC “Envelope Tracking” – GaN Enabled
- RadHard
- Power Over Ethernet
- RF Transmission
- Network and Server Power Supplies
- Point of Load Modules
- Energy Efficient Lighting
- Class D Audio

Design Basics Agenda



- Gate Driver Requirements
- Layout
- Thermal Management

 E-Mode Gate Drive - Low $V_{GS(ON)}$ Overhead




Gate Drive Solution




No overshoot:

$$R_G \geq \sqrt{\frac{4(L_G + L_S)}{C_{GS}}}$$

 
- Minimize inductance
 - Tight gate drive layout
 - BGA and LGA minimizes package inductance
 - Choose correct resistance
- Separate source and sink transistors allowing for separate drive paths.




Bootstrap Supply

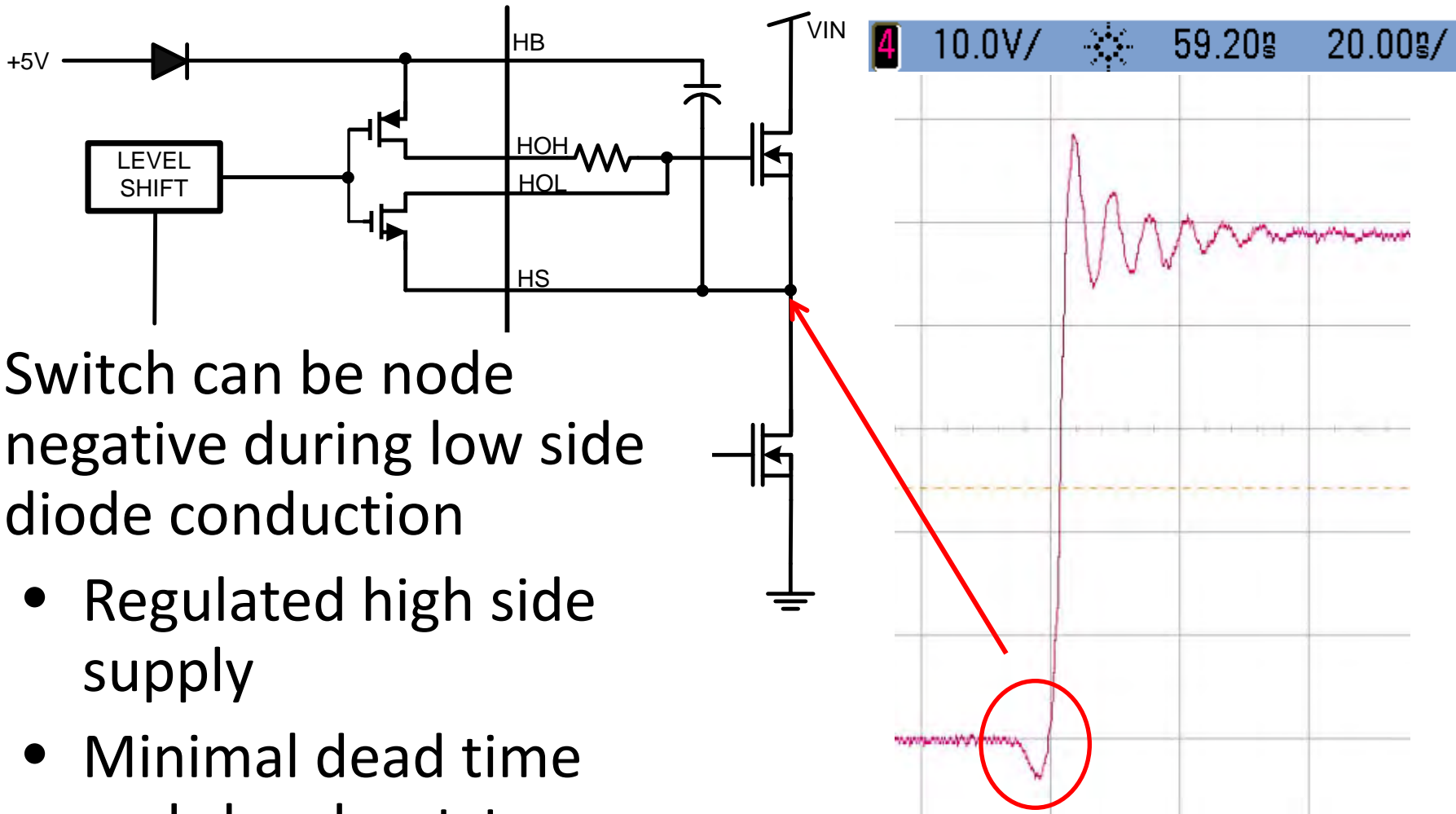

High Side Regulation – LM5113

 

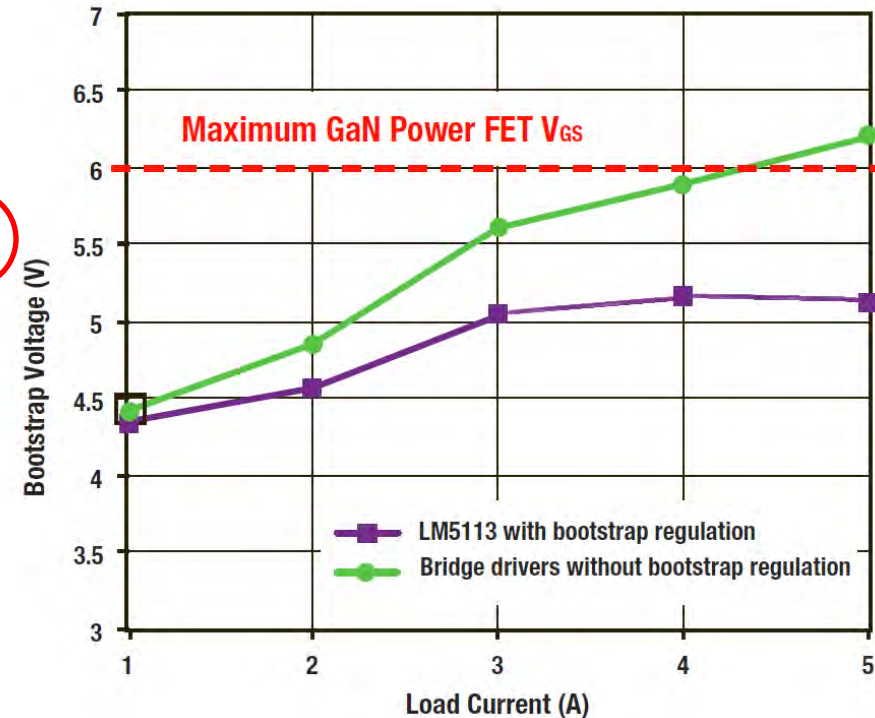- Bootstrap clamp limits floating (HS) power supply
- Separate control inputs allow accurate, flexible tuning to minimize dead-time
- Well matched channel-to-channel propagation delays are critical
- Optional Schottky in parallel




Texas Instruments, “Gate Drivers for Enhancement Mode GaN Power FETs 100 V Half-Bridge and Low-Side Drivers Enable Greater Efficiency, Power Density, and Simplicity”, SNVB001




Layout


Packaging Evolution

 


So-8

 

LFPACK


 


DirectFET


 


LGA eGaN

Device Loss Breakdown

  


Generating Kelvin Source Connection

  


Minimize Common Source Inductance

Buck Converter Parasitics

 

L_S : Common Source Inductance

 L_{Loop} : High Frequency Power Loop Inductance




$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$,
 $F_S=1\text{ MHz}$, $I_{OUT}=20\text{ A}$

Layout Impact on Efficiency



Measured Efficiency

 

Experimental Prototype L_{LOOP} ≈ 0.4 nH




$V_{IN}=12\text{ V}, V_{OUT}=1.2\text{ V},$
 $F_S=1\text{ MHz}, L=150\text{ nH}$


Layout Impact on Peak Voltage



$L_{Loop} \approx 1.0 \text{ nH}$

 

$L_{Loop} \approx 0.4 \text{ nH}$

 


Switching Node Voltage

$V_{IN}=12 \text{ V}$ $V_{OUT}=1.2 \text{ V}$ $I_{OUT}=20 \text{ A}$
 $F_S=1 \text{ MHz}$ $L=150 \text{ nH}$


Conventional Lateral Layout




Top View

 

Side View


 


Conventional Vertical Layout

 


Top View

Side View

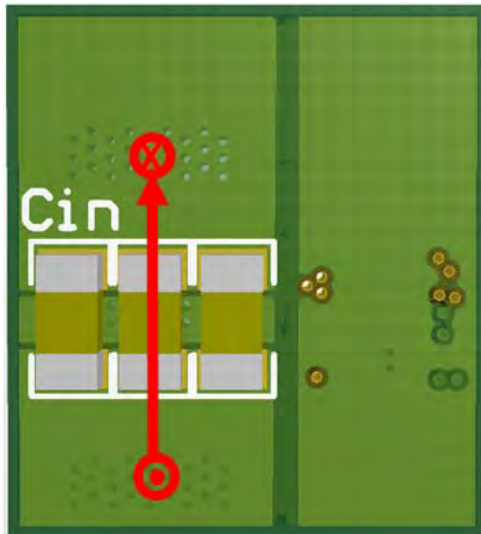 



Bottom View

Optimal Layout

 


Top View

Side View

  


**Top View
Inner Layer 1**

Power Loss Comparison

 


$V_{IN}=12\text{ V}$ $V_{OUT}=1.2\text{ V}$ $I_{OUT}=20\text{ A}$ $F_S=1\text{ MHz}$ $L=300\text{ nH}$
T/SR: EPC2015 Driver LM5113

Efficiency Comparison

 

$V_{IN}=12\text{ V}$ $V_{OUT}=1.2\text{ V}$ $F_S=1\text{ MHz}$ $L=300\text{ nH}$
T/SR: EPC2015 Driver LM5113

eGaN[®] FET vs. MOSFET

 

$V_{IN}=12\text{ V}$ $V_{OUT}=1.2\text{ V}$ $I_{OUT}=20\text{ A}$ $F_S=1\text{ MHz}$ $L=300\text{ nH}$ eGaN FET
T/SR: EPC2015 MOSFET T:BSZ097N04LS SR:BSZ040N04LS

Layout Summary



eGaN FETs improve performance in high switching frequency converters

- CSI is a critical component for maximizing switching performance
- Gate drive loop inductance limits switching speed
- Optimizing power loop inductance improves efficiency and minimizes voltage overshoot
- Current measurements affect performance
- Voltage measurements are bandwidth limited
- Reduced ringing reduces EMI




Thermal Management


Thermal Management



 Heat Is Generated In GaN Material
Essentially On The Surface Of The Die




Thermal Management

 


Two Paths For Heat: Through The Back Of The Die Or Through The Solder Contacts Into The PCB

Thermal Resistance with Heat Sink

 


Thermal Resistance with Heat Sink

 



Printed Circuit Board

Thermal Interface Material on sides of die too

Thermal Model with Heat Sink

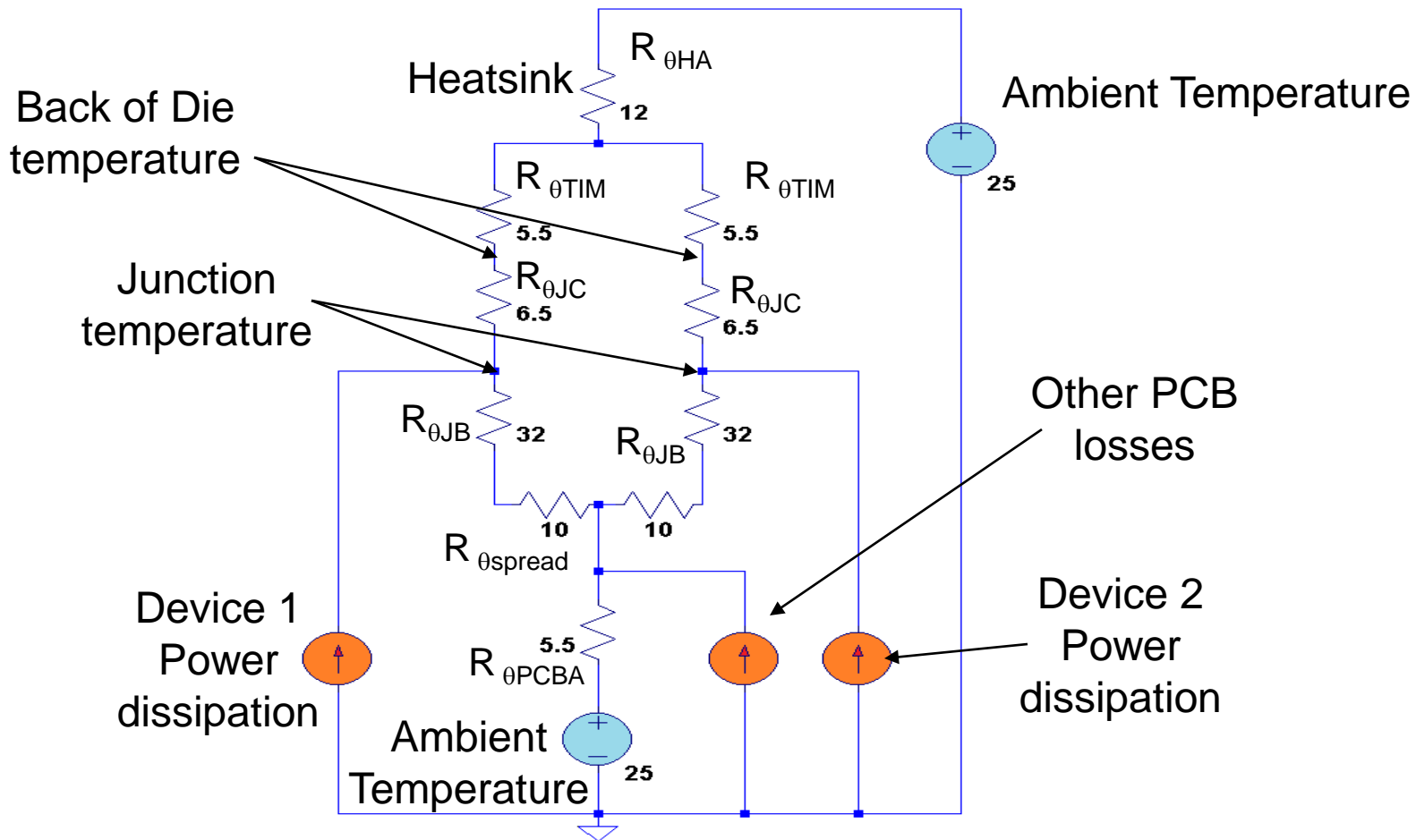

Thermal Results

  

Possible to remove up to 5 W from small EPC die with double sided cooling

Design Example Agenda



- Hard Switched Circuits
 - Buck Converter
 - Isolated Full Bridge
 - Envelope Tracking
- Resonant Circuits
 - Intermediate Bus Converter




Buck Converters

High Frequency Buck Converters




CPES Gen 1

 



$L_{Loop}=6.30nH$

CPES Gen 2

 


$L_{Loop}=2.90nH$

CPES Gen 3

  


L_{Loop} : High Frequency Power Loop

 


D. Reusch, D. Gilham, Y. Su, and F.C. Lee, C, "Gallium Nitride Based 3D Integrated Non-Isolated Point of Load Module", APEC 2012

EPC9107 Optimal Layout

 


Buck Module
Switching Node Voltage
 $V_{IN}=28\text{ V}$ $I_{OUT}=15\text{ A}$

 EPC9107
Demonstration Board
 $V_{IN}=12\text{-}28\text{ V}$ $V_{OUT}=3.3\text{ V}$
 $I_{OUT}=15\text{ A}$ $F_S=1\text{ MHz}$
2 x EPC2015



EPC9107 Demonstration Board

 


$V_{OUT}=3.3 \text{ V}$ $F_S=1 \text{ MHz}$
GaN T/SR: EPC2015 Driver LM5113



Isolated Full Bridge

100 V Hard Switching FOM

 



$V_{DS} = 0.5 * V_{DS} , I_{DS} = 15 A$

Regulated Full Bridge Converter




EPC9102 Demo board

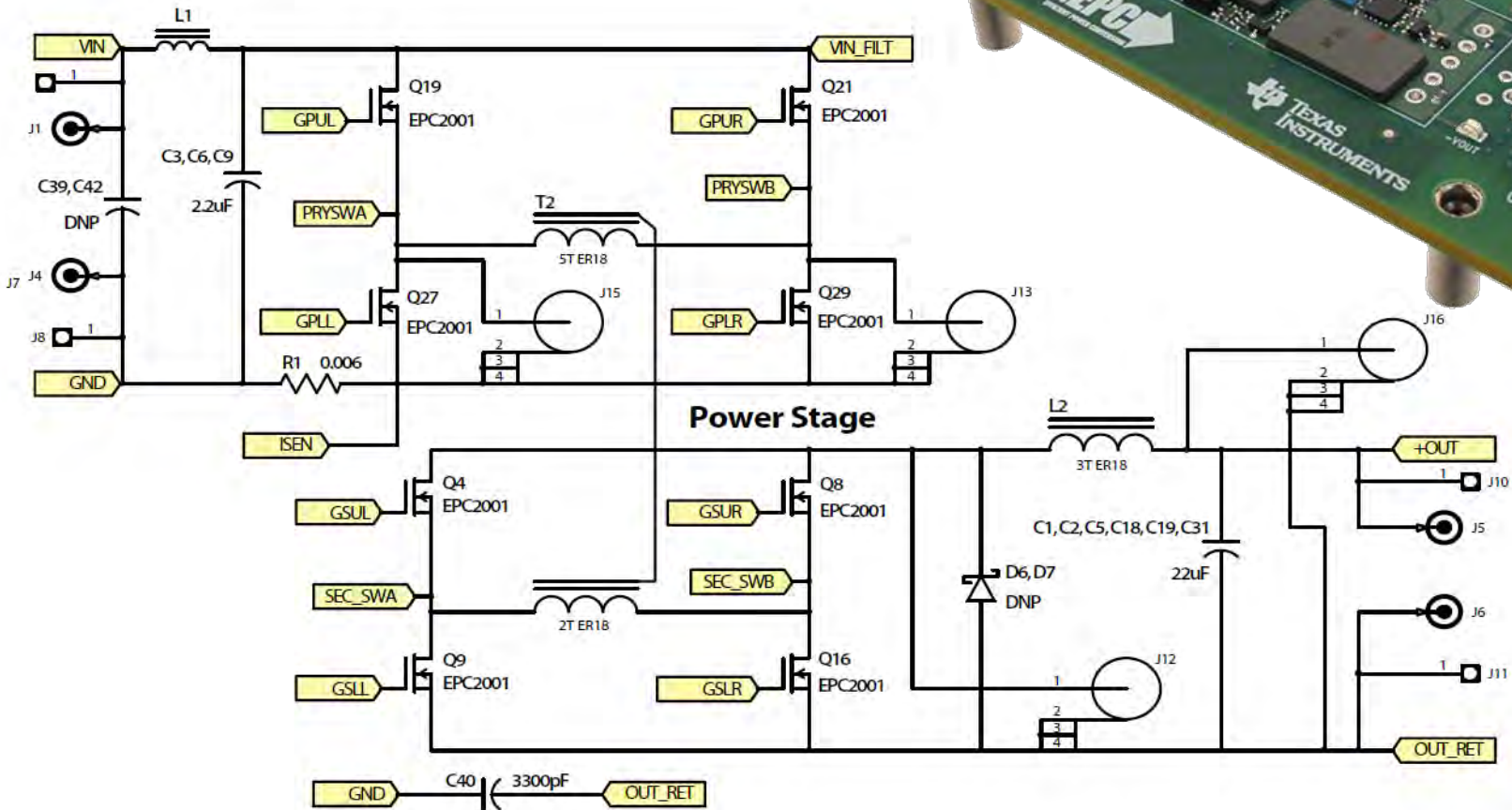 Full Bridge, 36 - 60 Vin, 12 V, 200 W, 375 kHz



Efficiency Comparison

 

Regulated 12 V Output

Brick Converter Summary




- Topologies varied
- Optimization as important as device selection
- Efficiency is key to power density
 - Maximum power loss is fixed.
- Good comparison requires identical designs
- Given topology, eGaN FETs will outperform MOSFETs based on superior FOM

Overview of Envelope Tracking




- World of Radio Frequency Power Amplifiers (RFPA) is changing.
- Increased efficiency driven by:
 - Improved battery life
 - Reduced cooling
 - Reduced size
 - Lower cost of operation


Peak to Average Power Ratio

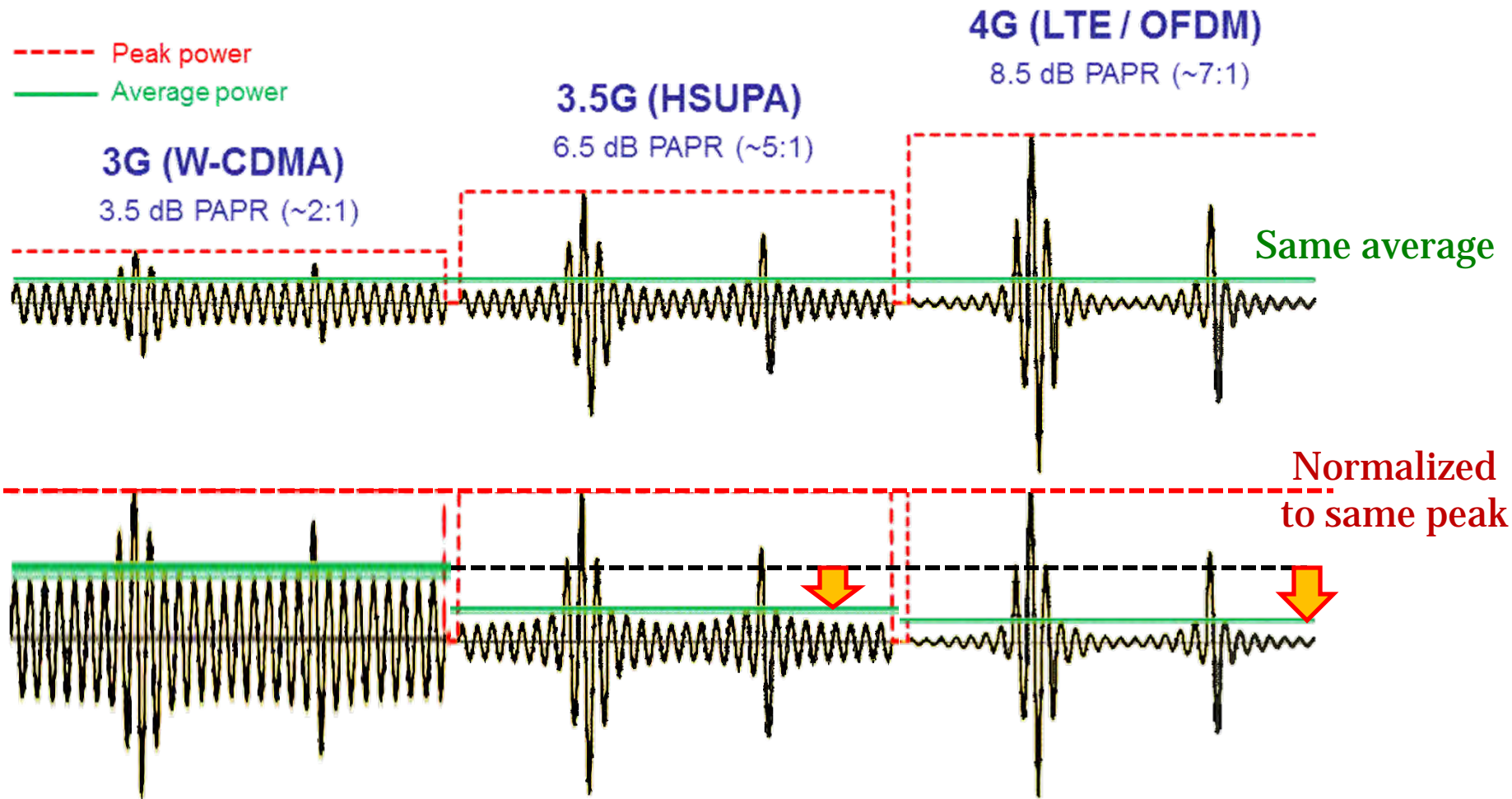

Effect of PAPR

 

Effect of Envelope Tracking

 

RFPA Standards*



	Standard	Launched	Typ. Carrier BW (MHz)	Typ. Spectral Efficiency (bps/Hz)	Approx. PAPR(dB)
2G cellular	GSM	1991	0.2	0.17	0.0
2.75G cellular	GSM + EDGE	2003	0.2	0.33	3.5
3G cellular	WCDMA FDD	2001	5	0.51	7.0
Digital TV	DVB-T	1997	8	0.55	8.0
Wi-Fi	IEEE 802.11a/g	2003	20	0.90	9.0
WiMAX	IEEE 802.16d	2004	20	1.20	8.5
Wi-Fi	IEEE 802.11n	2007	20	2.40	9.0
3.5G cellular	HSDPA	2007	5	2.88	8.0
3.9G cellular	LTE	2009	20	8.00	10.0


- Up to 20 MHz Carrier bandwidth required
- Required ET supply BW up to 5x higher if linear control

*Ref: www.open-et.org website

Envelope Tracking Supply



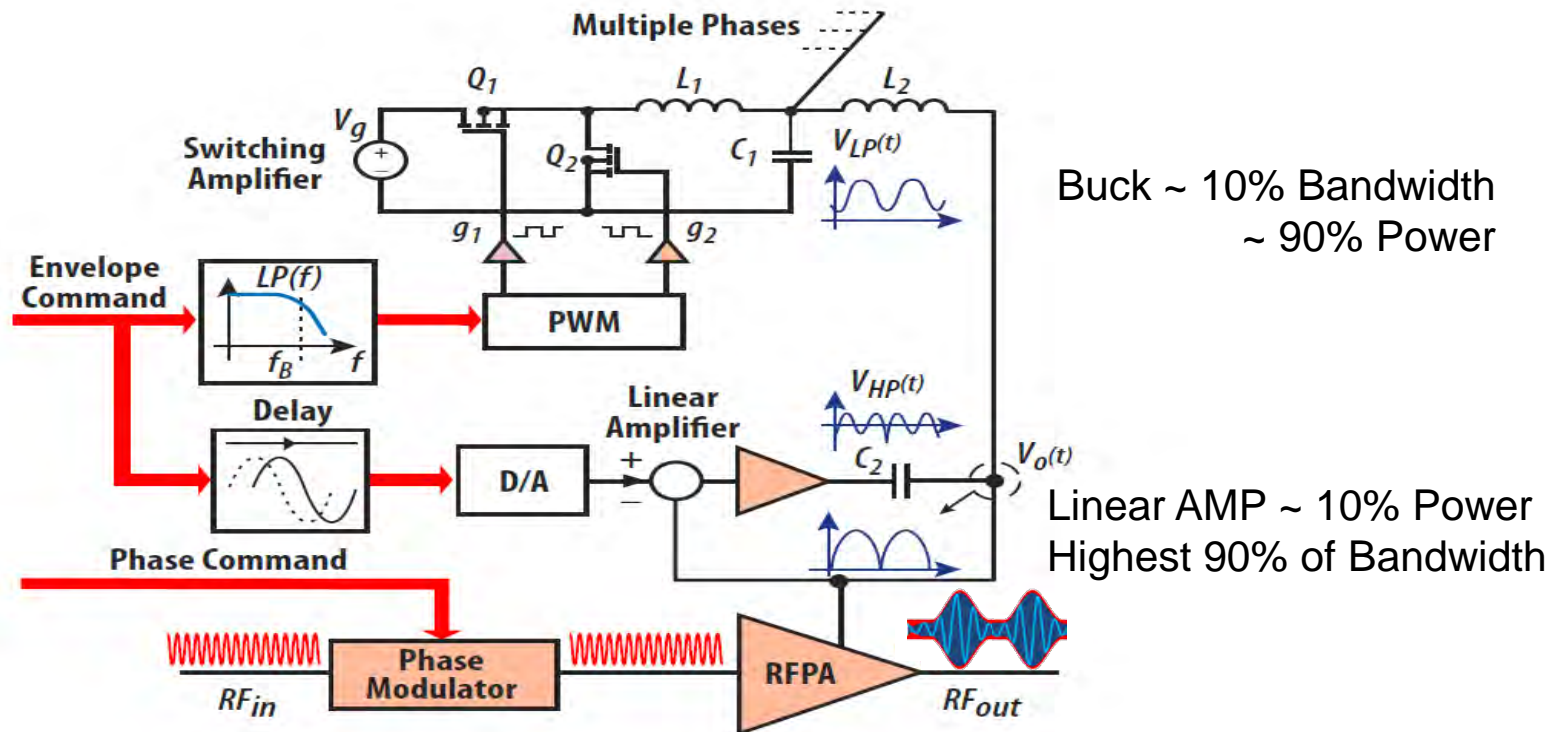- ET power supply topologies vary
 - Open loop boost – full BW required
 - Closed loop linear-assisted Buck*



*V. Yousefzadeh, et. Al, Efficiency optimization in linear-assisted switching power converters for envelope tracking in RF power amplifiers, ISCAS 2005

eGaN[®] FET based Buck(s) for ET



1300 W DVB* – 8 MHz BW and 8 dB PAPR

Linear-assisted Buck for ET

4 phase x 1 MHz Buck with up to 800 kHz band width

$45 V_{IN}$, $22 V_{OUT}$ / $15 A_{OUT}$ (Avg)

Pure Buck option for ET (Push frequency)

10 phase x 4 MHz Buck with up to 8 MHz band width


$45 V_{IN}$, $22 V_{OUT}$ / $6 A_{OUT}$ (Avg)

*Representative of a high power ET buck in HV LDMOS, such as that implemented by ET specialist Nujira.

6 A_{OUT} / 4 MHz Single ϕ Buck




- Modified an EPC9006 development board

 


45 V_{IN}

22 V_{OUT}



Common

 

Efficiency Results

 

Loss Breakdown

  


1 MHz EPC9002

4 MHz EPC9006

Future die size optimization possible

Higher Frequency ET Results*

 

*D. Čučak, et. al, "Application of eGaN FETs for highly efficient Radio Frequency Power Amplifier", CIPS 2012

Envelope Tracking Summary




- eGaN FETs are an enabling technology for ET
 - Low charge reduces delay and switching times
 - Thermally possible - with double sided cooling
- Results are representative, but not optimized
 - Improve inductor selection
 - Improve thermal design
 - Reduce high side peak device temp by reducing low side device size to reduce Q_{OSS} losses
- Power and # of phases application specific




Resonant Converters

100 V Soft Switching FOM

 


$V_{DS} = 48 \text{ V}$

eGaN[®] FET vs. MOSFET

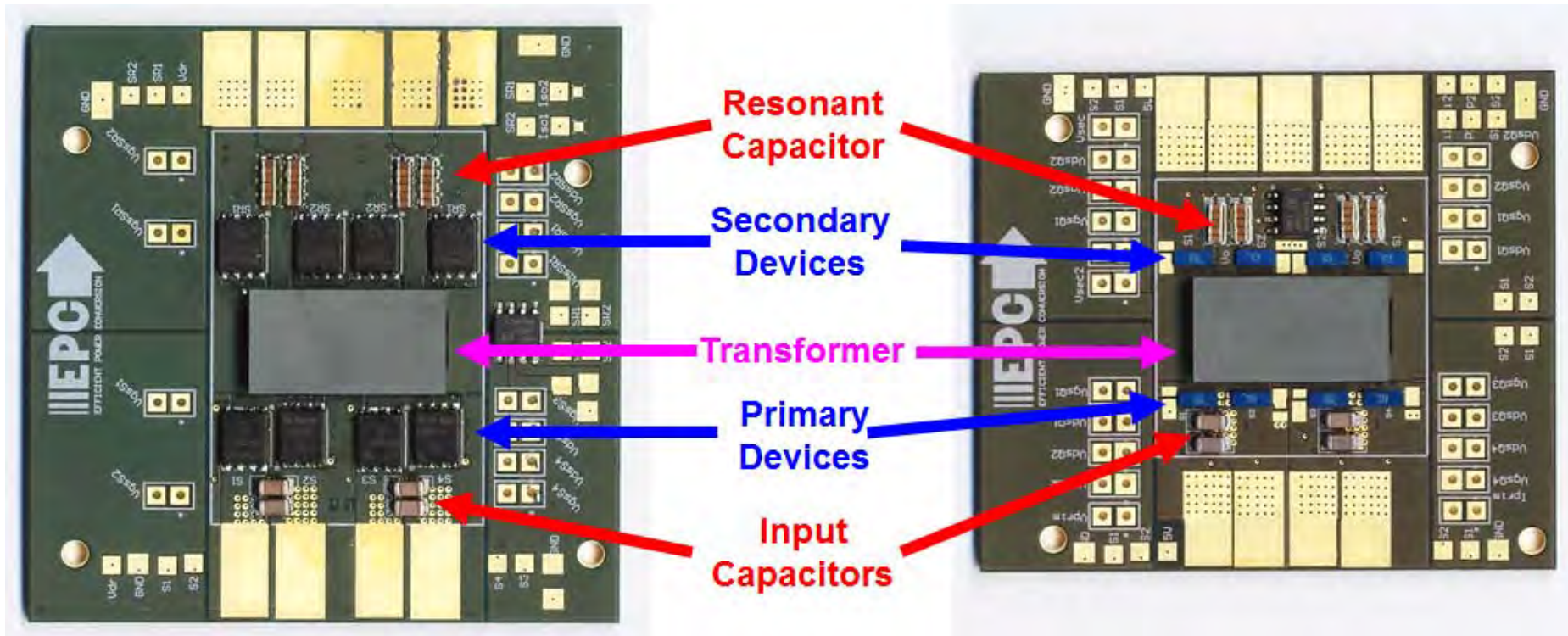


ZVS Switching Comparison

 



$F_S = 1.2 \text{ MHz}$, $V_{IN} = 48 \text{ V}$, and $V_{OUT} = 12 \text{ V}$

Duty Cycle Comparison

 


$F_S = 1.2 \text{ MHz}$, $V_{IN} = 48 \text{ V}$, and $V_{OUT} = 12 \text{ V}$

Efficiency Comparison

  

$F_S = 1.2 \text{ MHz}$, $V_{IN} = 48 \text{ V}$, and $V_{OUT} = 12 \text{ V}$

Loss Breakdown

 



$F_S = 1.2 \text{ MHz}$, $V_{IN} = 48 \text{ V}$, and $V_{OUT} = 12 \text{ V}$

EPC9105 Bus Converter



EPC9105 Demonstration Board

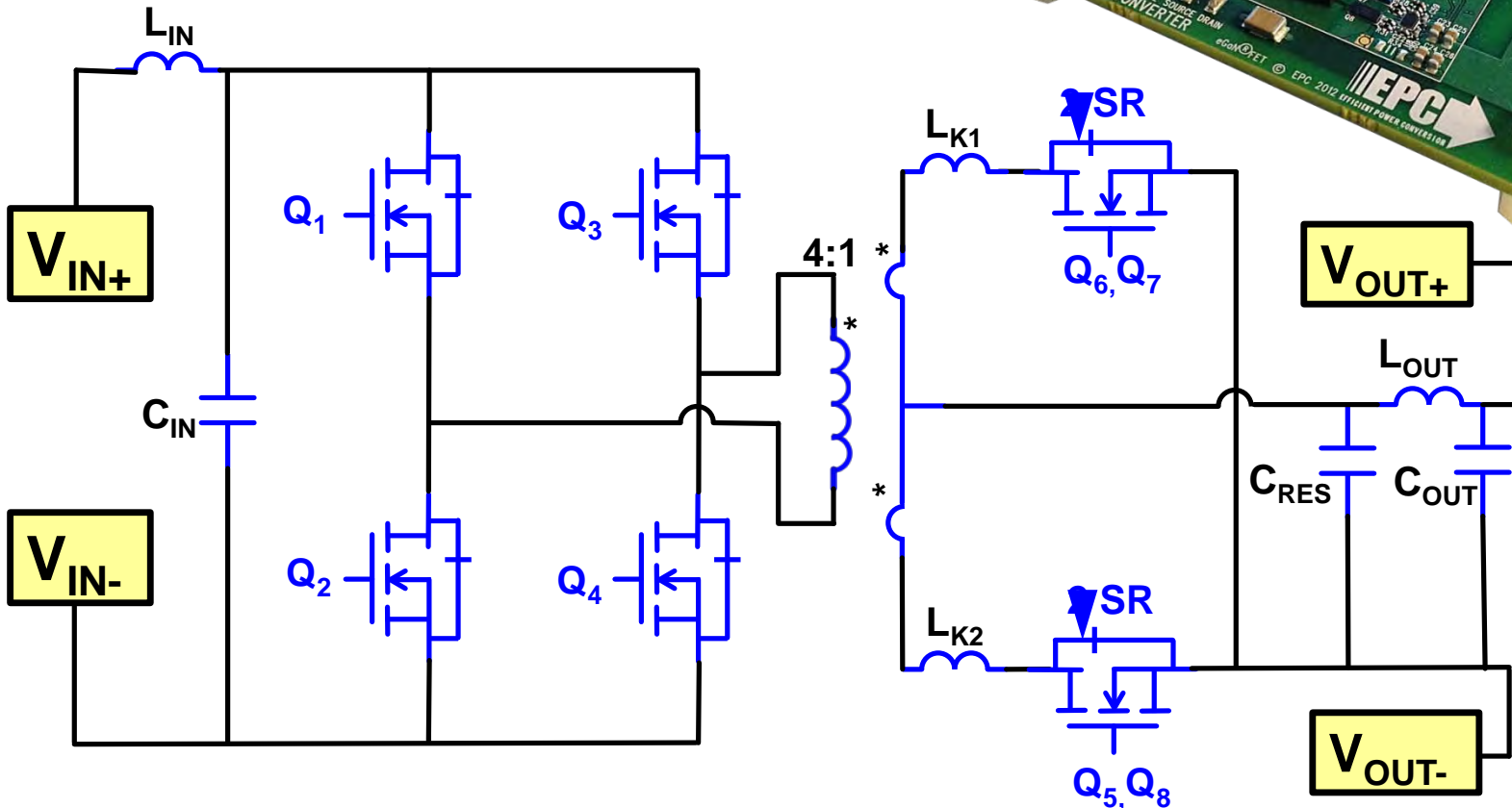 36 - 60 V_{IN}, 12 V_{OUT}, 350 W, 1.2 MHz



Resonant Converter Summary



- eGaN FETs improve high frequency resonant converter performance
 - Lower output charge
 - Lower gate charge
 - More power delivery per cycle

Summary



- GaN transistors have the potential to replace silicon power MOSFETs in power conversion applications with a low-cost and higher efficiency solution
- eGaN FETs are straightforward to use, but care must be taken due to the higher switching speeds compared with power MOSFETs
- GaN transistors enable exciting new applications such as RF Envelope Tracking