



The eGaN® FET
Journey Continues

National Taiwan University

How to use eGaN Correctly

Peter Cheng

Manager, Asia FAE

Efficient Power Conversion Corporation

2012 Nov. 16



Agenda




- **What is the Ideal Switcher?**
- **eGaN FETs Features & Benefits**
- **eGaN FETs Drivers**
- **Layout, Layout, Layout !**
- **Design Example**



The Ideal Power Switch



 - Block Infinite Voltage
- Carry Infinite Current
- Switch In Zero Time
- Zero Drive Power
- Normally Off





eGaN FETs

Key Features & Benefits



- Enhancement-Mode devices
- $R_{ds(on)}$ per unit area is much smaller
- Much faster switching (t_r/t_f) time
- Very low Q_g and capacitance
- Provide much higher light load efficiency
- No parasitic PN junction body ($Q_{rr}=0$)



eGaN Characteristics



Note:

All curves here use [EPC2001](#) (100V, 7mΩ)

Figure 2: Transfer Characteristics

 


Figure 4: R_{DS(on)} vs V_{GS} for Various Temperature

 


Figure 9: Normalized Threshold Voltage vs. Temperature

 


Figure 6: Gate Charge




 


Figure 8: Normalized On Resistance Vs Temperature

 

 

 8 * EPC2010 paralleling 500A, 10uS, 100Hz





eGaN® FETs are Easy to Use



It's just like a MOSFET

except for TWO things

(1)

The hyper high frequency capability makes circuits using eGaN® FET very sensitive to layout

(2)

eGaN® FET are more sensitive to gate rupture than power MOSFETs





Gate Drive Constraints



- V_{GS} = 6V max, but **4.5V needed** to fully enhance
- High frequency layout required
 - switching time 2-5ns range
- Fast switching causes opportunity for false turn on. dv/dt immunity decreases as device voltage rating increases. A gate drive with a low resistance turn-off (pull-down) is needed.
- The diode V_f is higher than silicon and therefore the gate drive needs to help minimize diode conduction.
- Zero reverse recovery allows very short pulse widths




Layout

  

Minimize Common Source Inductance (CSI)




Switching Interval

 

- Assumes turn-on / off symmetrical
- Neglects RMS loss effect of C_{OSS} dv/dt current
- Neglects di/dt effect of C_{OSS} dv/dt current
- Neglects miller effect of di/dt across L_{loop}
- Neglects gate inductance



Effect on Common source inductance

 




PCB Land Pattern



RECOMMENDED LAND PATTERN (measurements in μm)

 The land pattern is solder mask defined
Solder mask is 10um smaller per side than bump




Pad no. 1 is Gate

Pad no. 2 is Substrate

Pad no. 3 and 5 are Drain

Pad no. 4 is Source

 


Recommended Land Pattern is Defined in the Datasheet



PCB Top View



 Relative Sizes (Cu trace, Solder mask, Bump, Stencil)






PCB Cross Section



 Relative Dimensions (Cu trace, solder mask, Bump, stencil)
EPC2001, EPC2007, EPC2014, EPC2015



No Stencil Bench Mount - Tacky flux part number: Kester TSF-6502





Drivers







LM5113

  


  LM5113 bootstrap voltage regulation, synchronous buck converter evaluation board.
Input 48V; output 10V; switching frequency at 800 KHz.







LM5113 layout reference

 


Without Gate Resistors

 

 TI driver layout recommendation
4 external components placement!
Close to driver IC





Without Gate Resistors

 




Example: Buck Converter

  



Ideal Hard Switching

 


$$P_{T_R} \approx \frac{V_{IN} * I_{OFF} * Q_{GD}}{2 * I_G}$$

$$P_{T_F} \approx \frac{V_{IN} * I_{OFF} * Q_{GS2}}{2 * I_G}$$




Buck Converter Parasitics

 

L_s : Common Source Inductance


 
L_{Loop} : High Frequency Power Loop Inductance





$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$,
 $F_s=1\text{ MHz}$, $I_{OUT}=20\text{ A}$



Lloop & CSI impact on turn on

  

 
 
Impact of high frequency loop inductance, L_{Loop} , on turn on. Ideal waveforms: Solid line, Waveforms with parasitic influence: Dashed line





Impact of common source inductance, L_s , on turn on. Ideal waveforms: Solid line, Waveforms with parasitic influence: Dashed line



Lloop & CSI impact on turn off

  

 
 
Impact of high frequency loop inductance, L_{Loop} , on turn off. Ideal waveforms: Solid line, Waveforms with parasitic influence: Dashed line



Impact of common source inductance, L_s , on turn off. Ideal waveforms: Solid line, Waveforms with parasitic influence: Dashed line



Packaging Evolution

  




Layout Impact on Efficiency



Experimental Efficiency

 

$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$,


$F_s=1\text{ MHz}$, $L=150\text{ nH}$

Optimal Layout Prototype






Peak Voltage Comparison

 

$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$, $F_s=1\text{ MHz}$, $L=150\text{ nH}$




Experimental Waveforms

 

$V_{IN}=12\text{ V}$, $V_{OUT}=1.2\text{ V}$, $F_s=1\text{ MHz}$, $L=300\text{ nH}$




Experimental Waveforms

 

$V_{IN}=24\text{ V}$, $V_{OUT}=1.2\text{ V}$, $F_s=1\text{ MHz}$, $L=300\text{ nH}$



Optimal Layout Efficiency

 


$V_{OUT}=1.2\text{ V}$, $F_s=1\text{ MHz}$, $L=300\text{ nH}$

eGaN FET: Top: EPC2015 SR: EPC2015

Si MOSFET: Top: BSZ097N04 SR: BSZ04N04



Optimal Layout Power Loss

 

$V_{OUT}=1.2\text{ V}$, $F_s=1\text{ MHz}$, $L=300\text{ nH}$

eGaN FET: Top: EPC2015 SR: EPC2015

Si MOSFET: Top: BSZ097N04 SR: BSZ04N04



Summary



eGaN FETs can improve high frequency hard switching converter performance:

- Lower Switching Charge ($Q_{GD} + Q_{GS2}$)
- Lower Gate Charge (Q_G)
- Improved Packaging
- Improved Layout Capability



What Other Advances are Needed?



- High speed digital controller ICs and integrated controller/driver ICs.
 - Application specific controllers to reduce time-to-market
 - Dynamic deadtime control with ~1ns resolution
 - Synchronous PFCs
 - Envelope Tracking Controllers
- Note: Improvements in magnetics would be helpful...



*The end of the road
for silicon.....*

*is the beginning of
the eGaN FET
journey!*