



RFIC2014, Tampa Bay  
June 1-3, 2014



# WSC: GaN-based Power Supplies and Power Supply Modulators for Efficient Powering of RF PAs


M.A. de Rooij, J.T. Strydom, S. Colino




International Microwave Symposium  
IEEE 1-6 June 2014, Tampa Bay, FL MTT-S
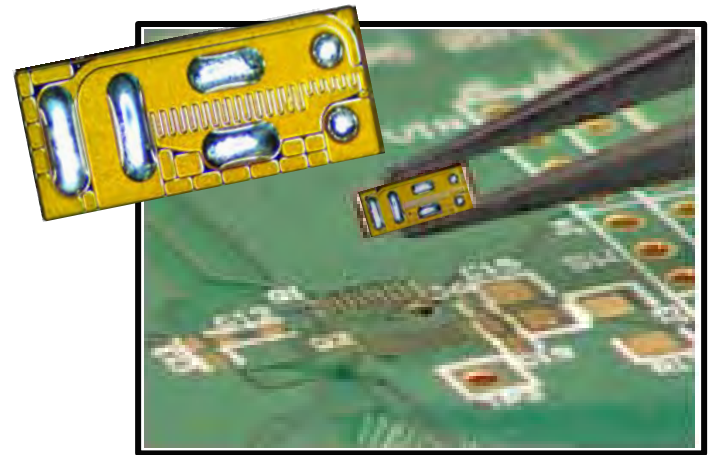
# Agenda

- Background to eGaN FETs
- EPC8000 Series Parts
- Envelope Tracking
- Experimental Results
- Limiting Factors
- Summary



# Why Gallium Nitride?

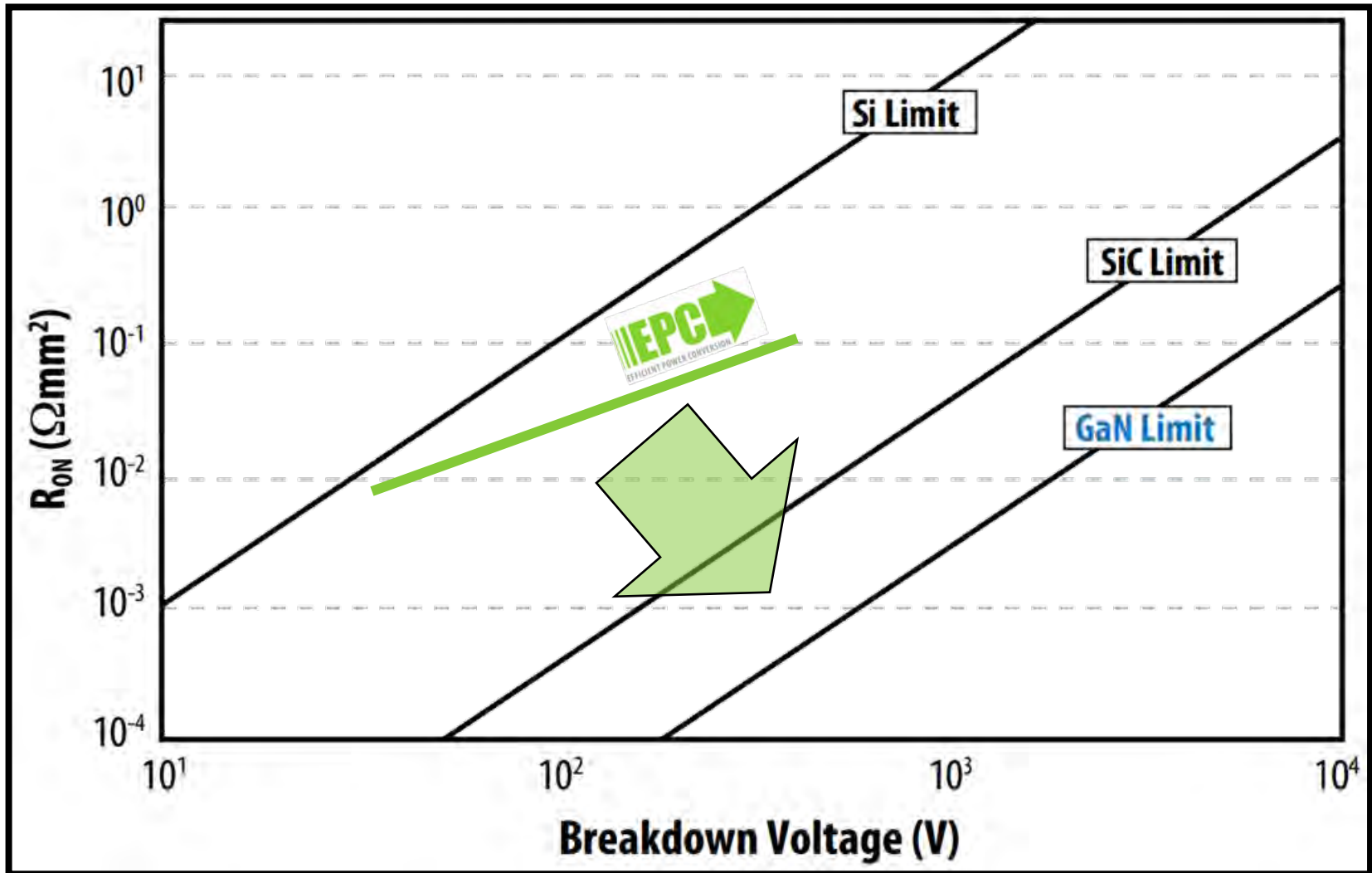


# eGaN FETs are LGA




**Land Grid Array**  
**Solder bump under die**


# Flip Chip Assembly

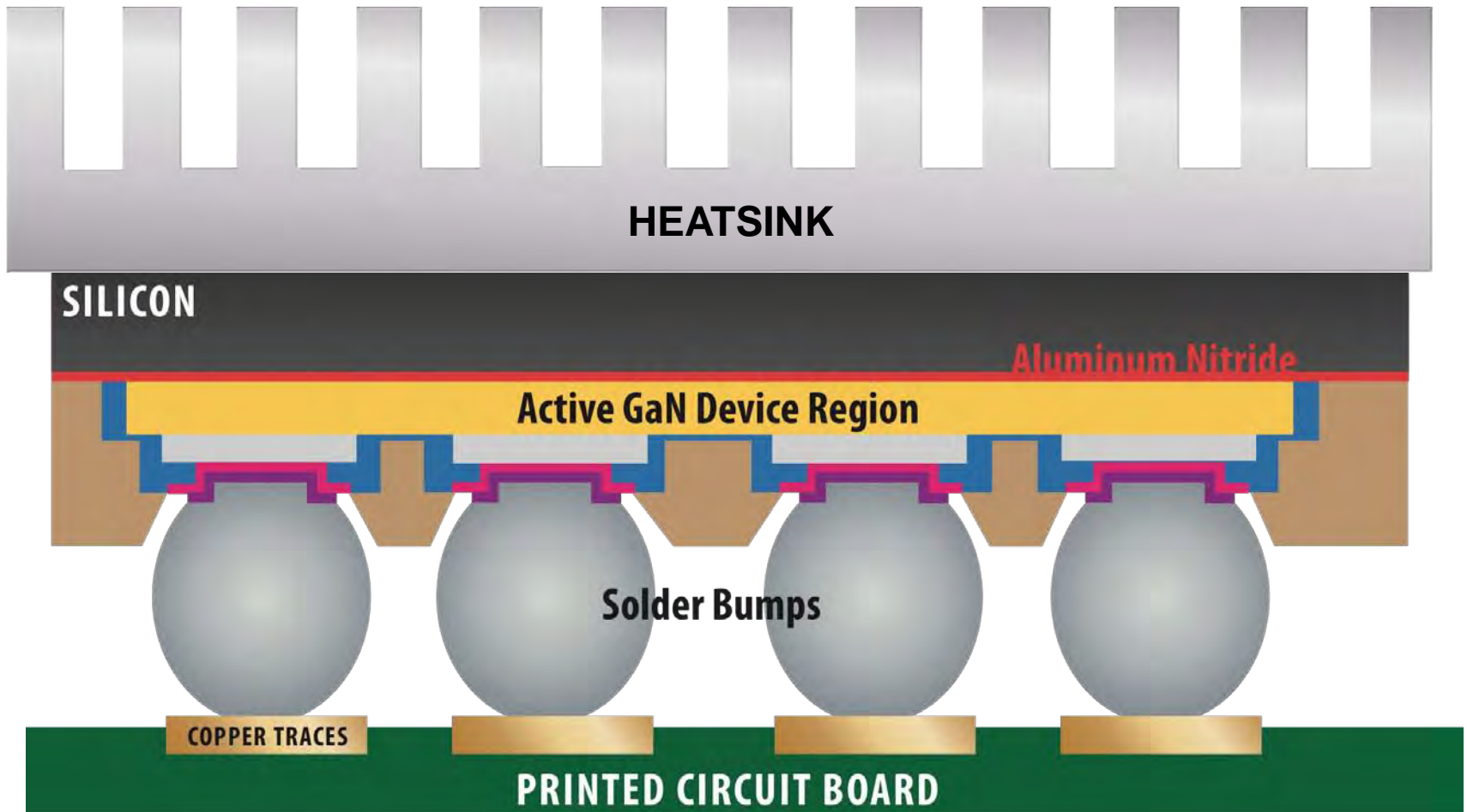


# Cross Section of an eGaN FET

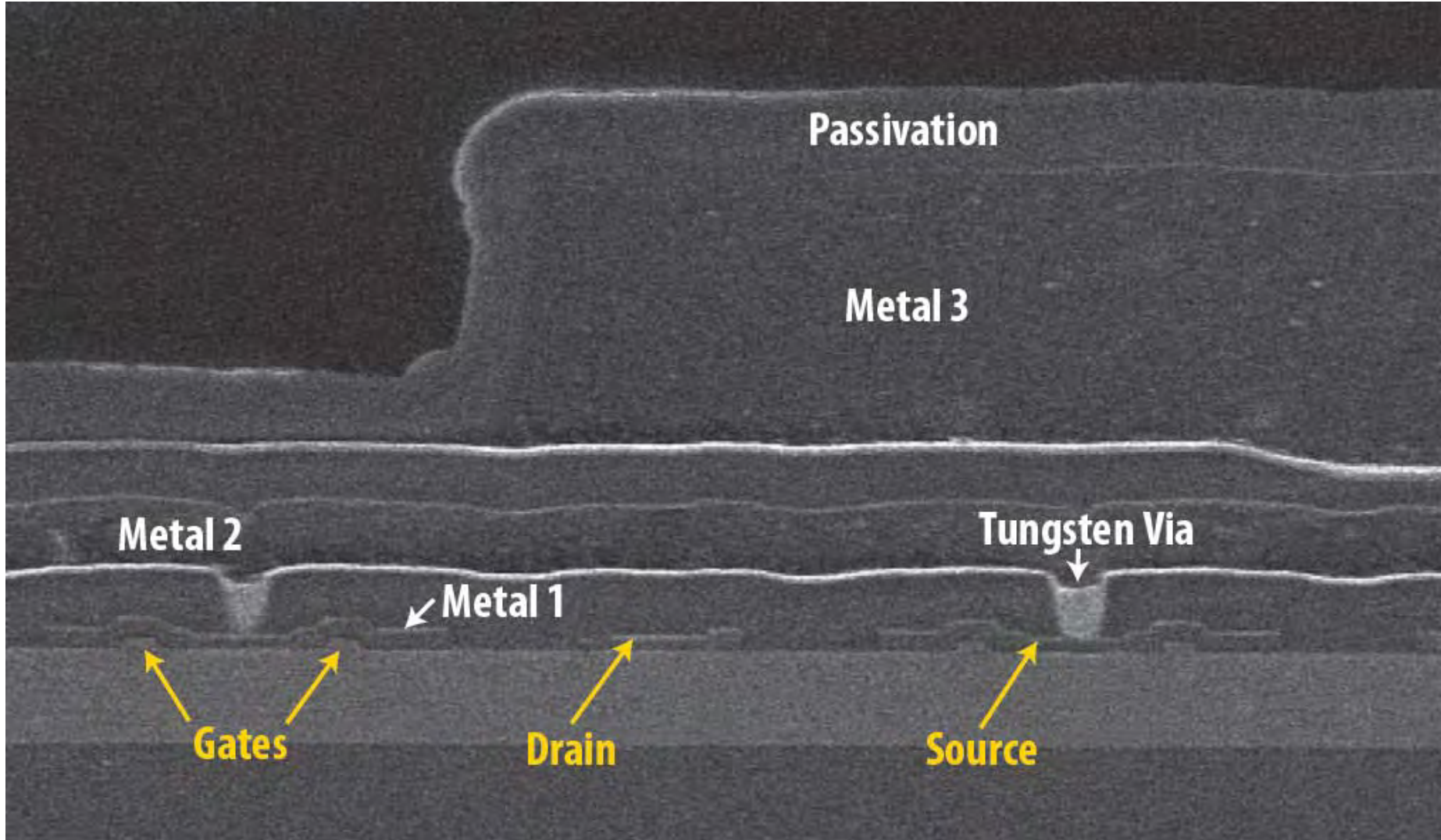

# Threshold vs. Temperature

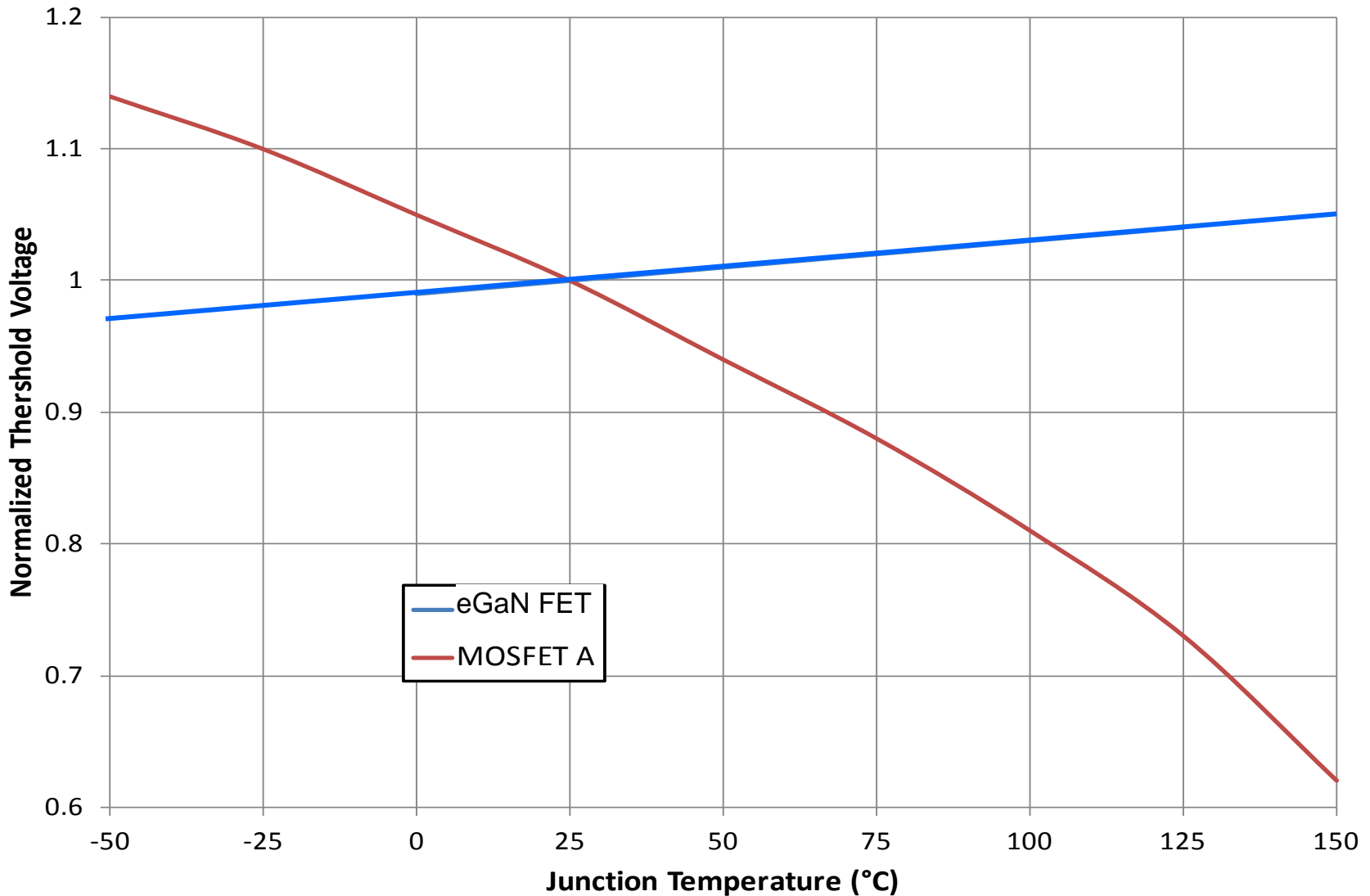


# eGaN<sup>®</sup> FETs vs. MOSFETs

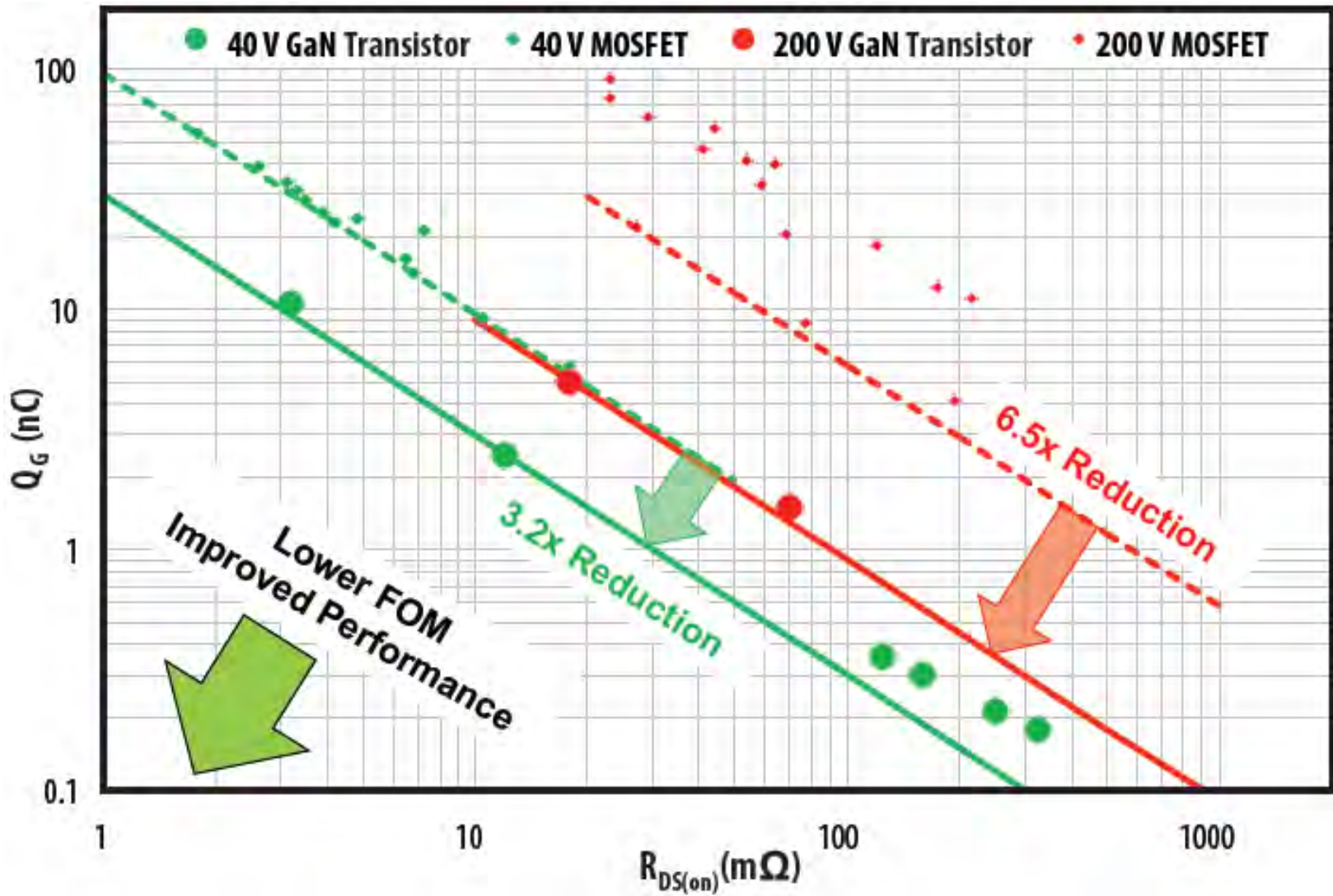





# Why Envelope Tracking?

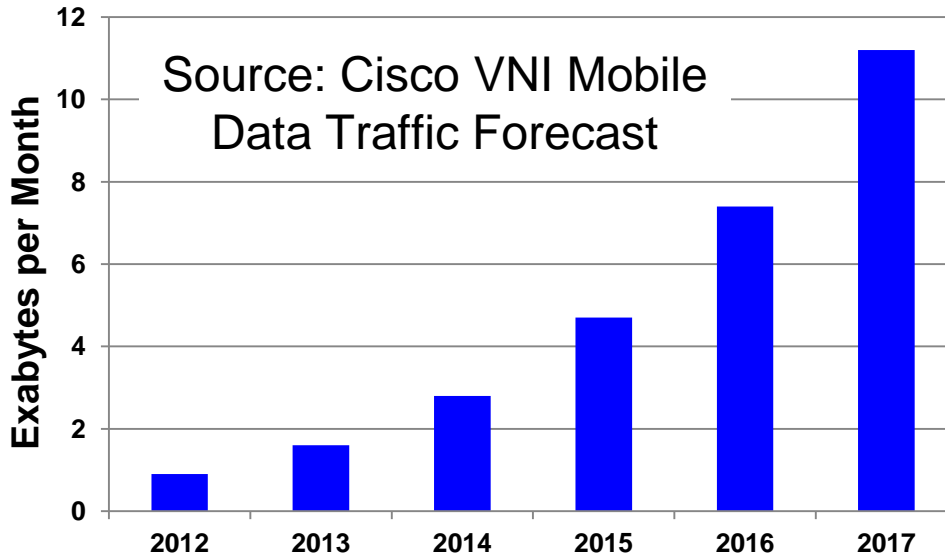


66% Compound annual growth rate

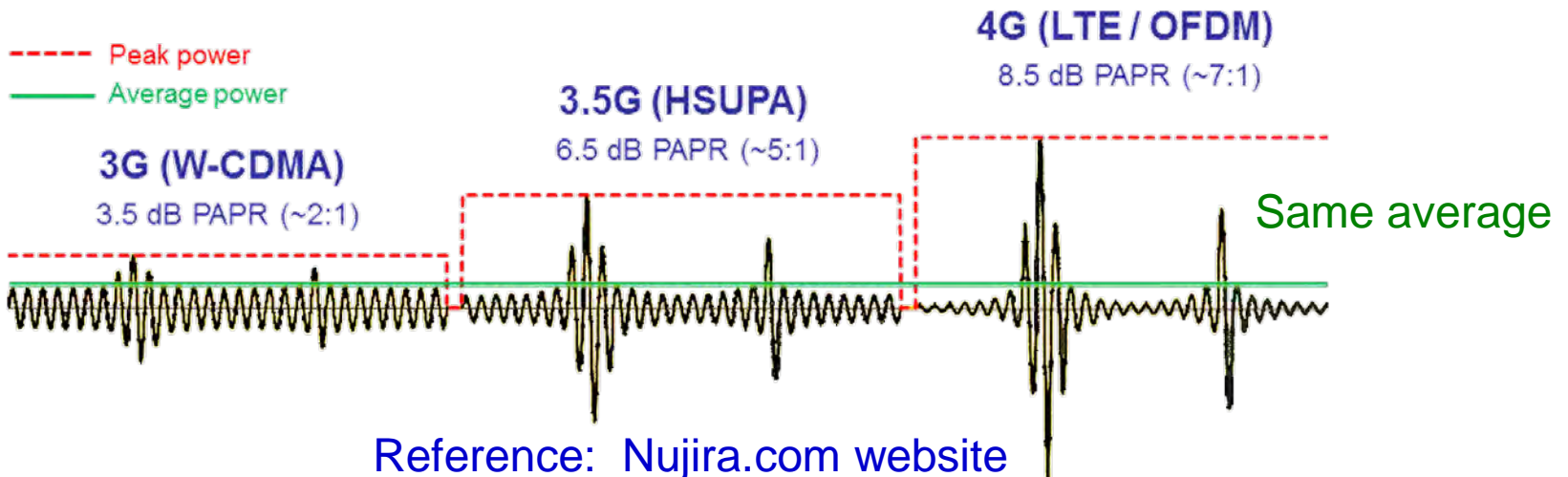

# Effect of PAPR

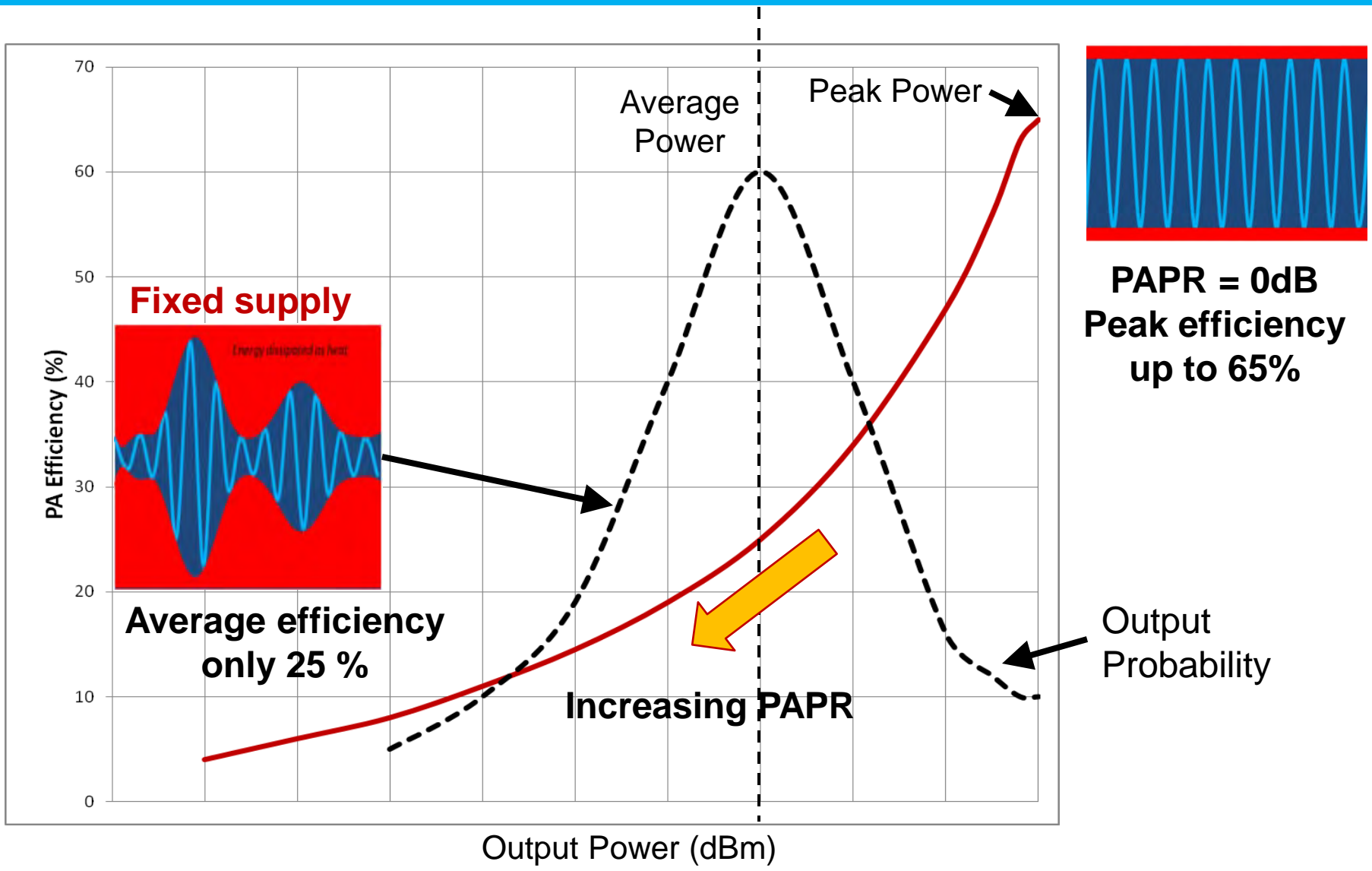

# Effect of Envelope Tracking

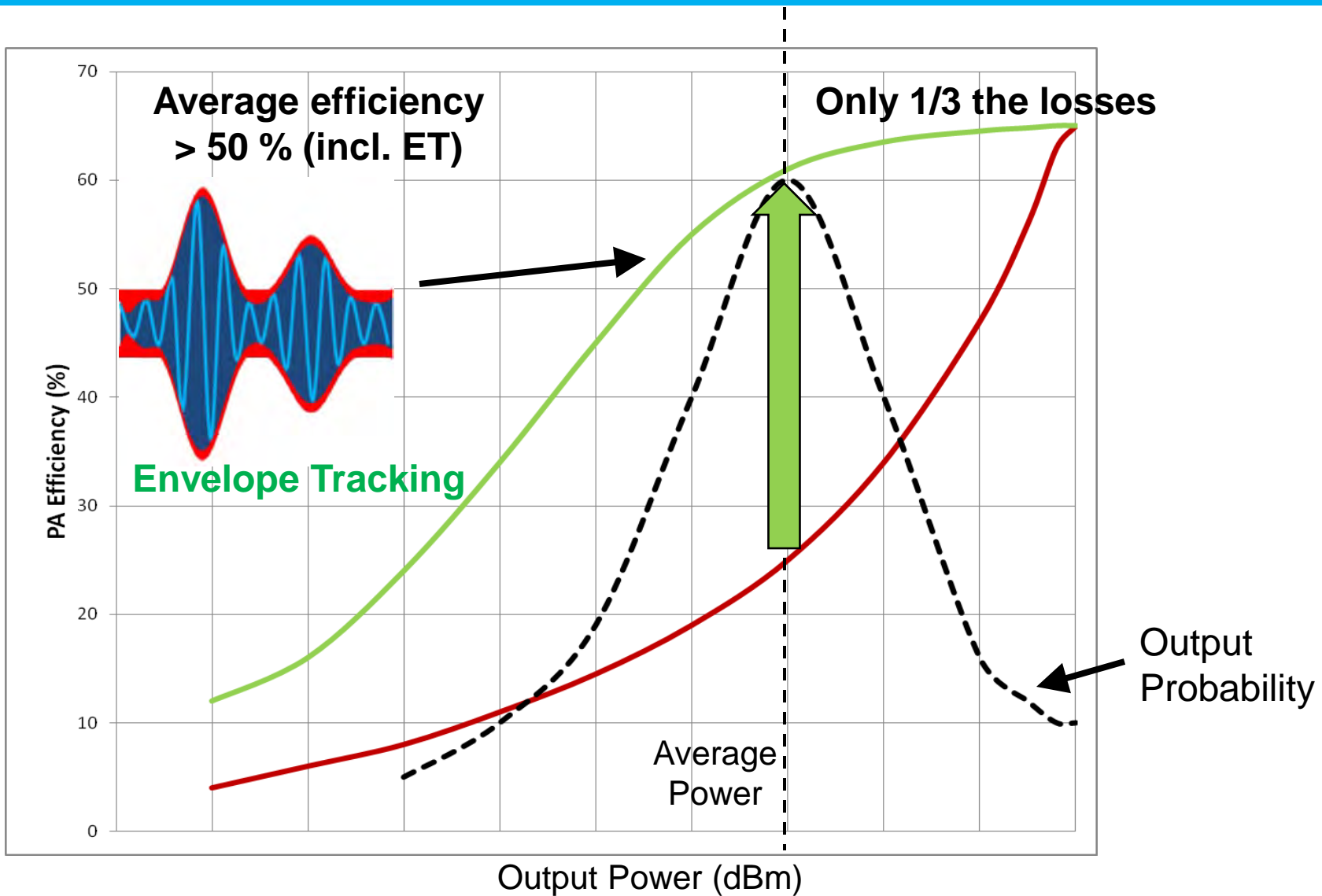


# RFPA Standards\*

	Standard	Launched	Typ. Carrier BW (MHz)	Typ. Spectral Efficiency (bps/Hz)	Approx. PAPR(dB)
2G cellular	GSM	1991	0.2	0.17	0.0
2.75G cellular	GSM + EDGE	2003	0.2	0.33	3.5
3G cellular	WCDMA FDD	2001	5	0.51	7.0
Digital TV	DVB-T	1997	8	0.55	8.0
Wi-Fi	IEEE 802.11a/g	2003	20	0.90	9.0
WiMAX	IEEE 802.16d	2004	20	1.20	8.5
Wi-Fi	IEEE 802.11n	2007	20	2.40	9.0
3.5G cellular	HSDPA	2007	5	2.88	8.0
3.9G cellular	LTE	2009	20	8.00	10.0

- Up to 20 MHz Carrier bandwidth required
- Required ET supply BW about 5x higher than carrier BW


\*Ref: [www.open-et.org](http://www.open-et.org) website

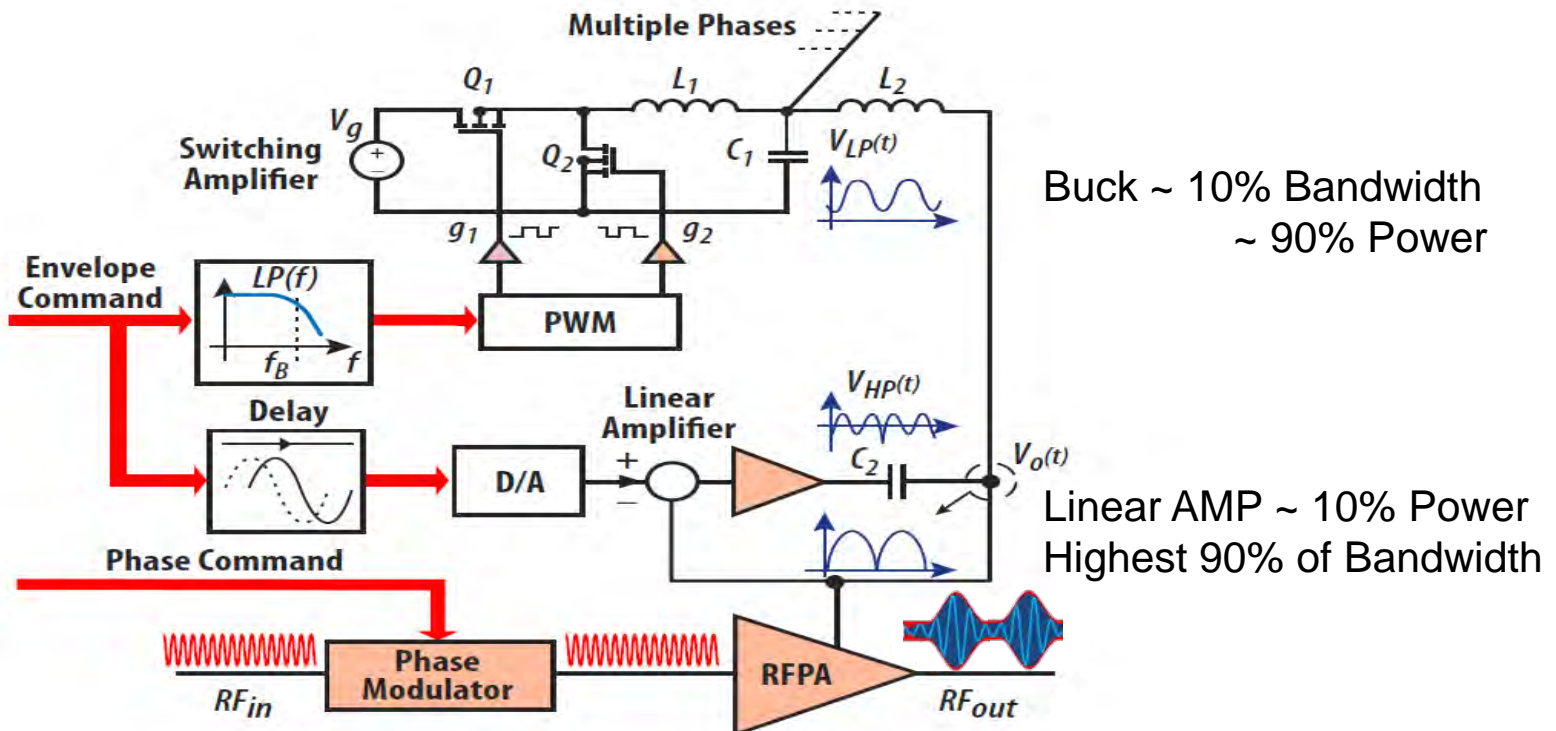- **ET power supply topologies vary**
  - Open loop boost – full BW required
  - Closed loop linear-assisted Buck\*





\*V. Yousefzadeh, et. Al, Efficiency optimization in linear-assisted switching power converters for envelope tracking in RF power amplifiers, ISCAS 2005

# Initial Efficiency Results

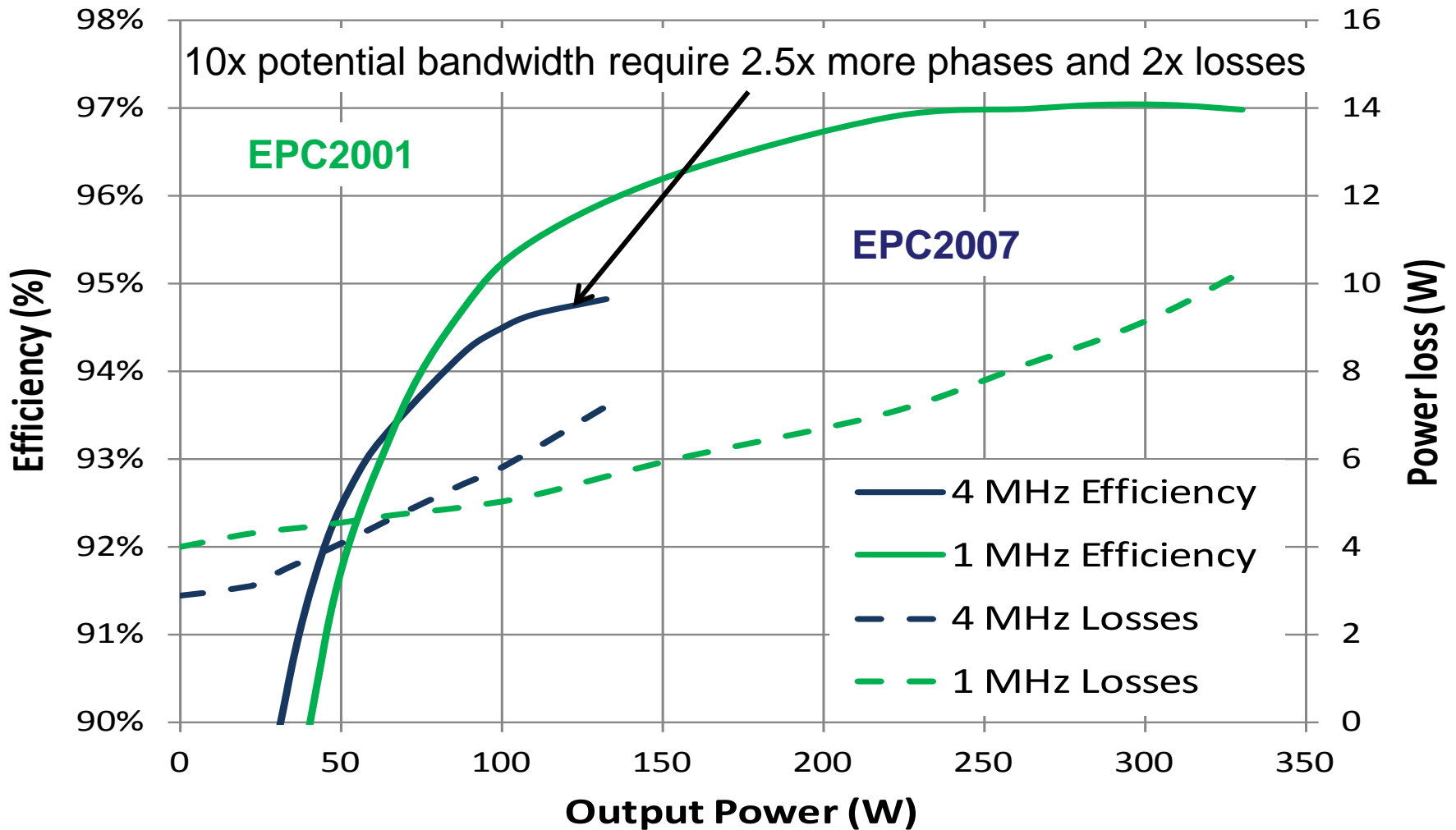

# Loss Breakdown

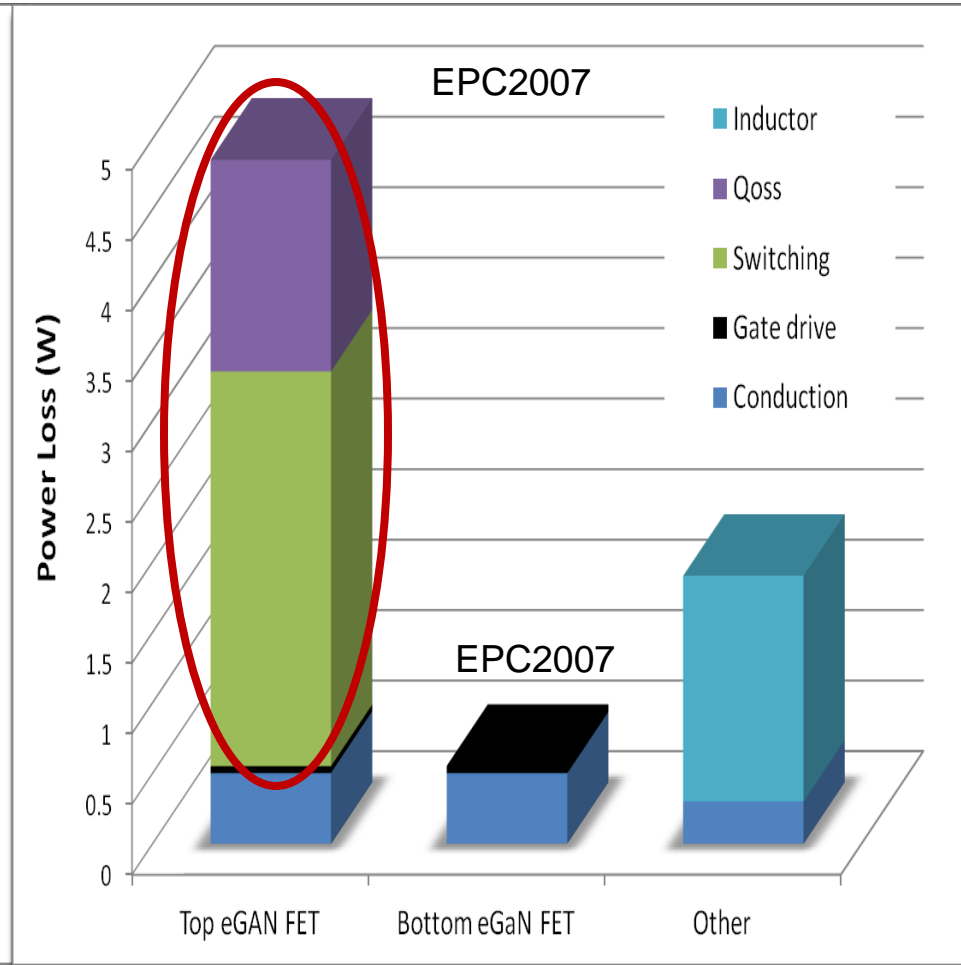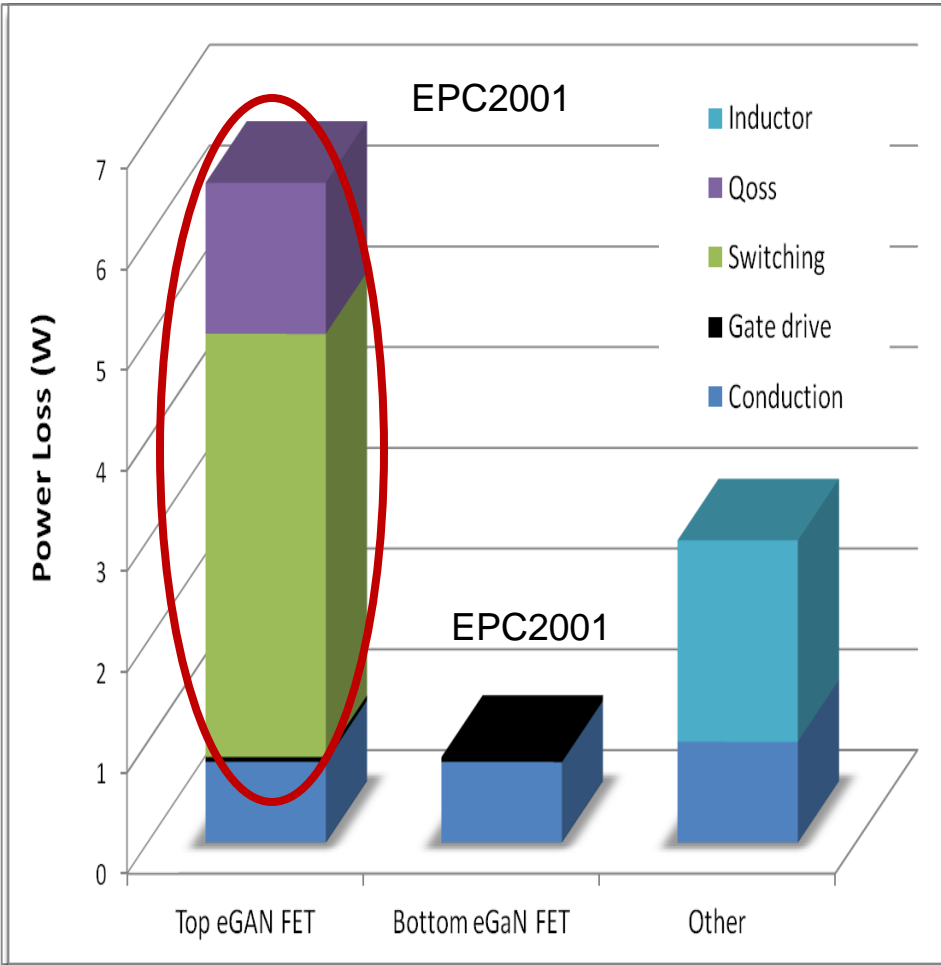


1 MHz EPC9002

4 MHz EPC9006

Future die size optimization possible

# Lower Voltage ET Results\*

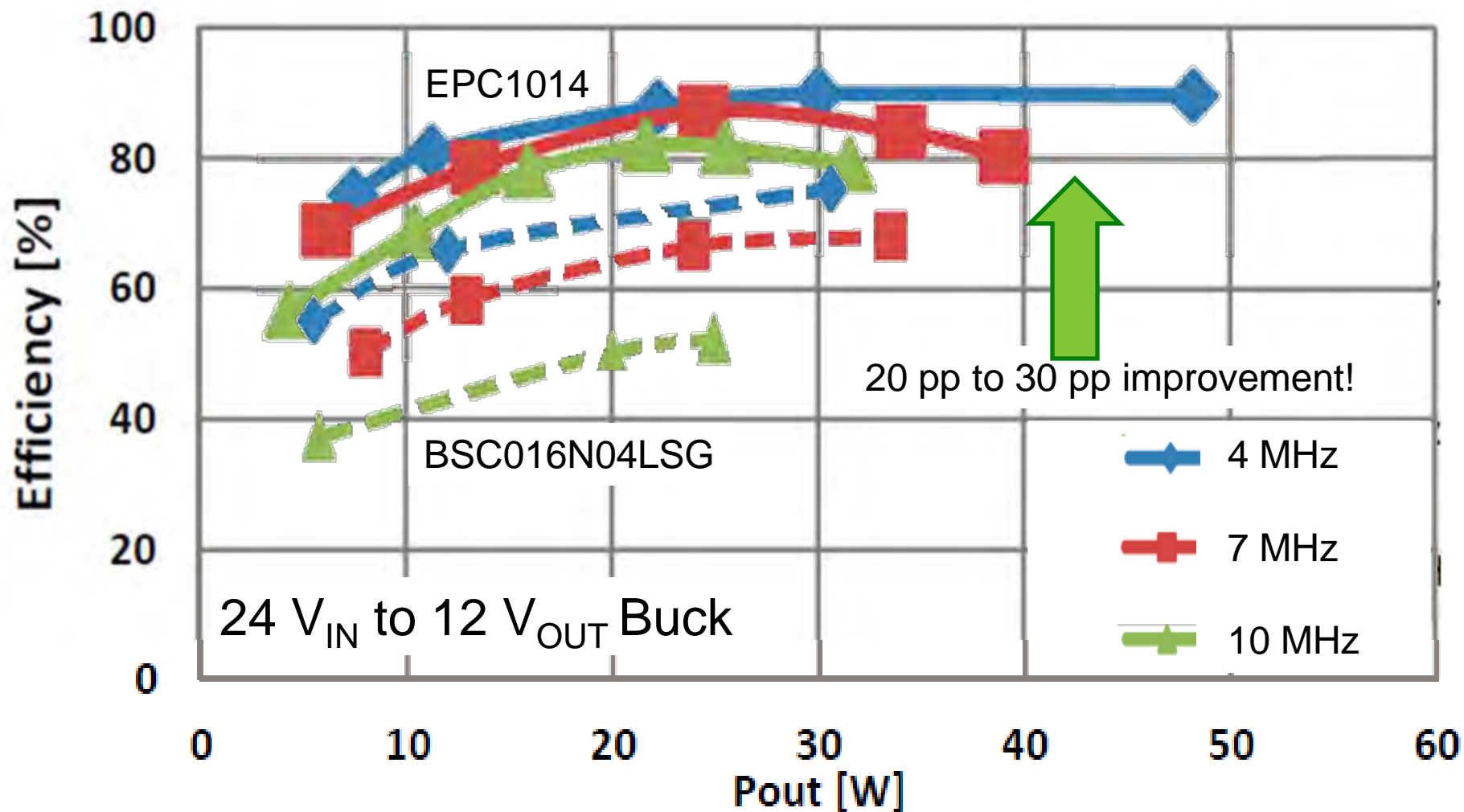

\*D. Čučak, et. al, "Application of eGaN FETs for highly efficient Radio Frequency Power Amplifier", CIPS 2012





# Higher Frequency Lower Power Devices



RFIC 2014

- **Improve Device Bandwidth**
- **Reduce device size**
- **Minimize  $Q_{GD}$  / HS-FOM**
- **Complete dv/dt immunity**
- **Minimize gate loop inductance**
- **Minimize power loop inductance**
- **Separate gate and power loops**

# Ultra High Frequency eGaN<sup>®</sup> FETs




EPC Part No.	BV (V)	Max. R <sub>DS(ON)</sub> (mΩ) (V <sub>GS</sub> = 5V, I <sub>D</sub> = 0.5 A)	Min. Peak Id (A) (Pulsed, 25 °C, T <sub>pulse</sub> = 300 μs)	Typical Charge (pC)					Typical Capacitance (pF) (V <sub>DS</sub> = 20 V; V <sub>GS</sub> = 0 V)		
				Q <sub>G</sub>	Q <sub>GD</sub>	Q <sub>GS</sub>	Q <sub>OSS</sub>	Q <sub>RR</sub>	C <sub>ISS</sub>	C <sub>OSS</sub>	C <sub>RSS</sub>
EPC8004	40	125	7.5	358	31	110	493	0	45	17	0.4
EPC8007	40	160	6	302	25	97	406	0	39	14	0.3
EPC8008	40	325	2.9	177	12	67	211	0	25	8	0.2
EPC8009	65	138	7.5	380	36	116	769	0	47	17	0.4
EPC8005	65	275	3.8	218	18	77	414	0	29	9.7	0.2
EPC8002	65	530	2	141	9.4	59	244	0	21	5.9	0.1
EPC8003	100	300	5	315	34	110	1100	0	38	18	0.2
EPC8010	100	160	7.5	354	32	109	1509	0	47	18	0.2




2.05 mm x 0.85 mm

\* Preliminary Data – Subject to Change without Notice

# Small Signal Performance

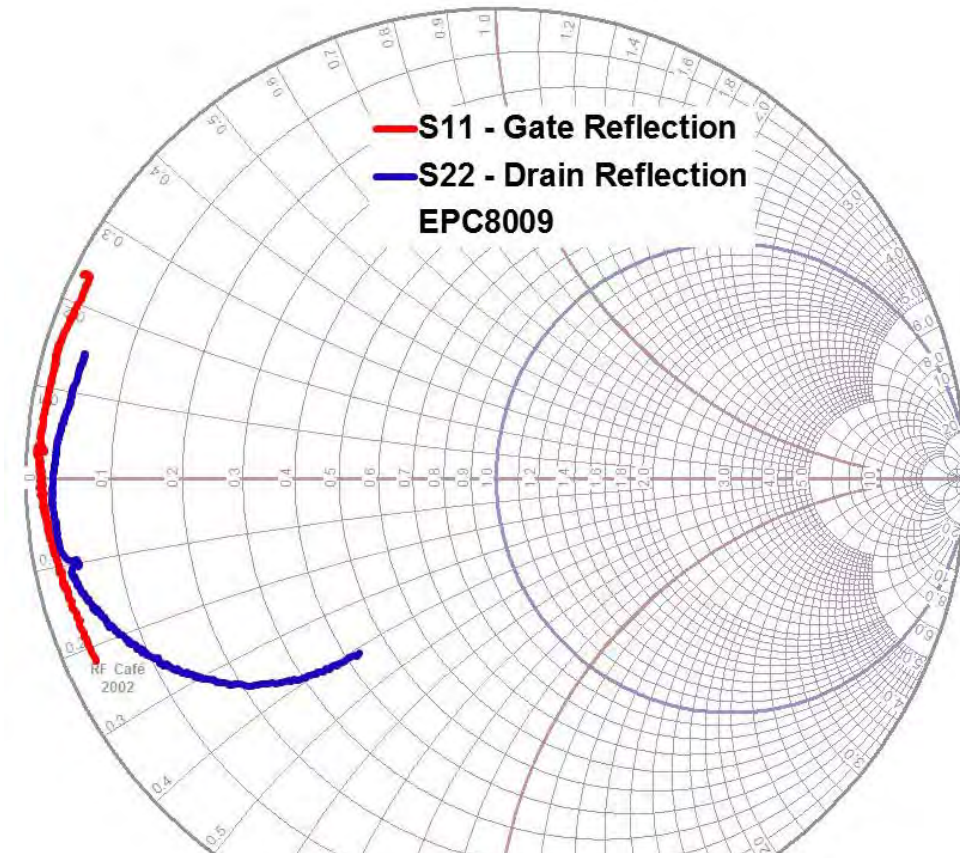


Bias: 30 V, 500 mA

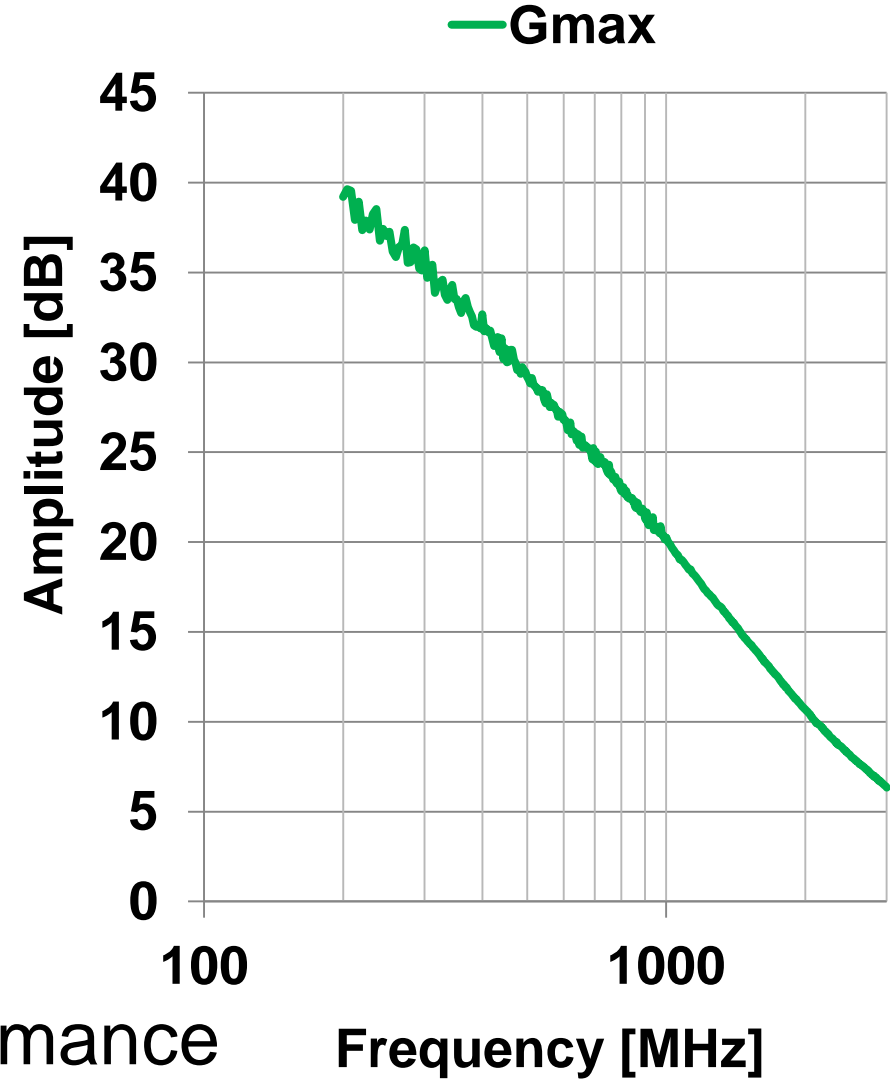

Designed for switching Performance


Frequency [MHz]

# Large Signal Performance

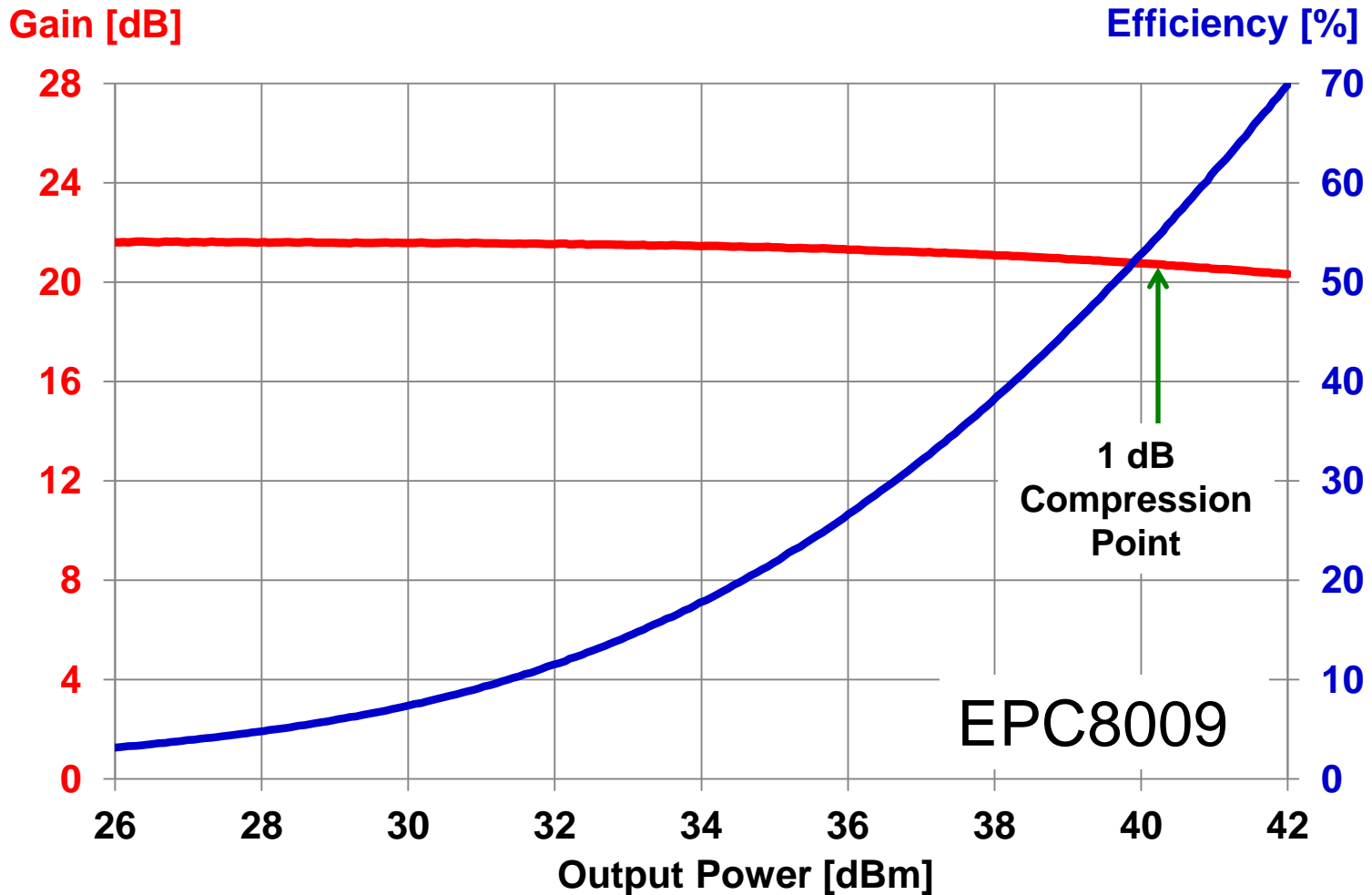


**500 MHz, Class A, Bias = 30 V, 500 mA**


# Die Size - Gate Charge

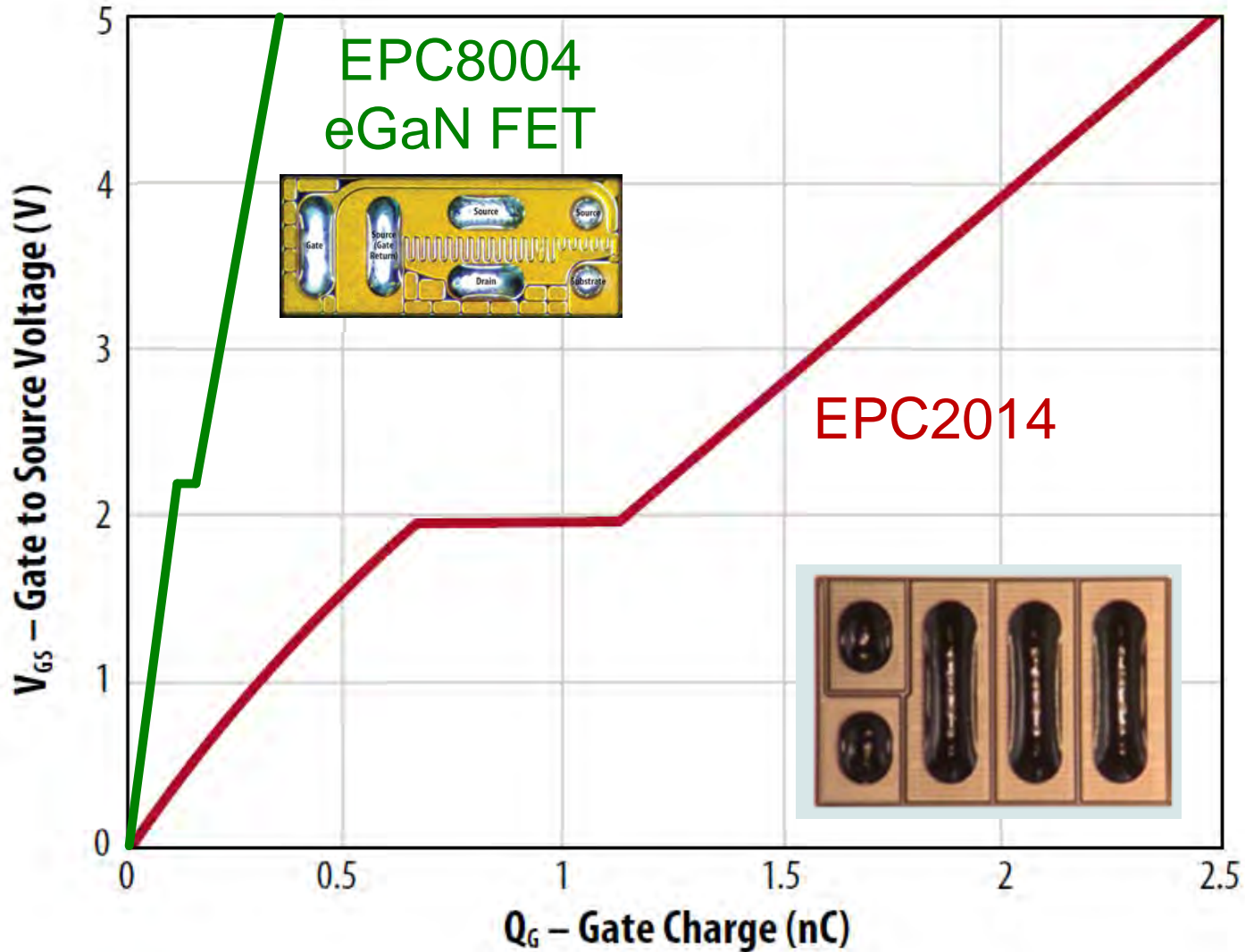

# Hard Switching FOM

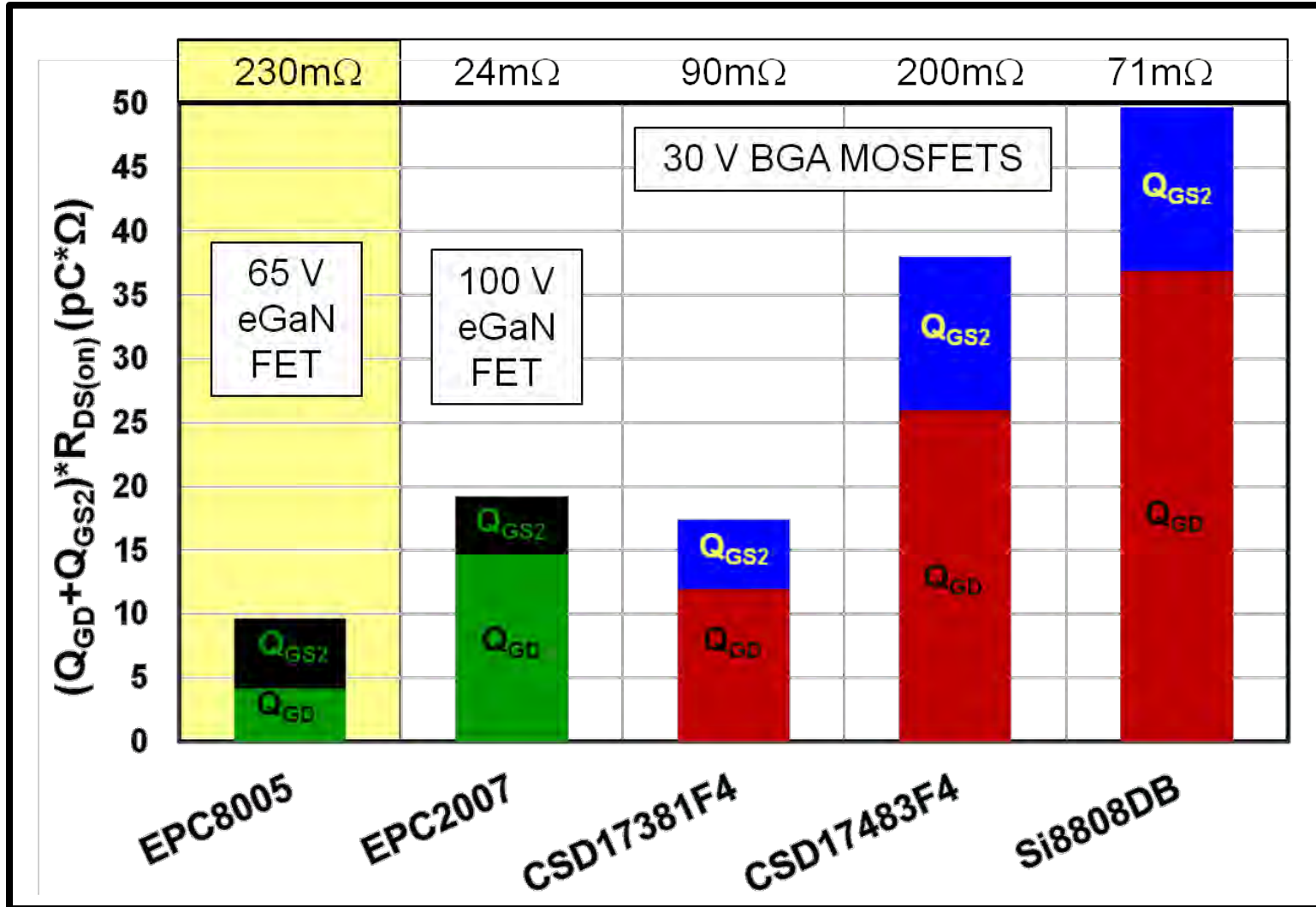


# dv/dt Immunity

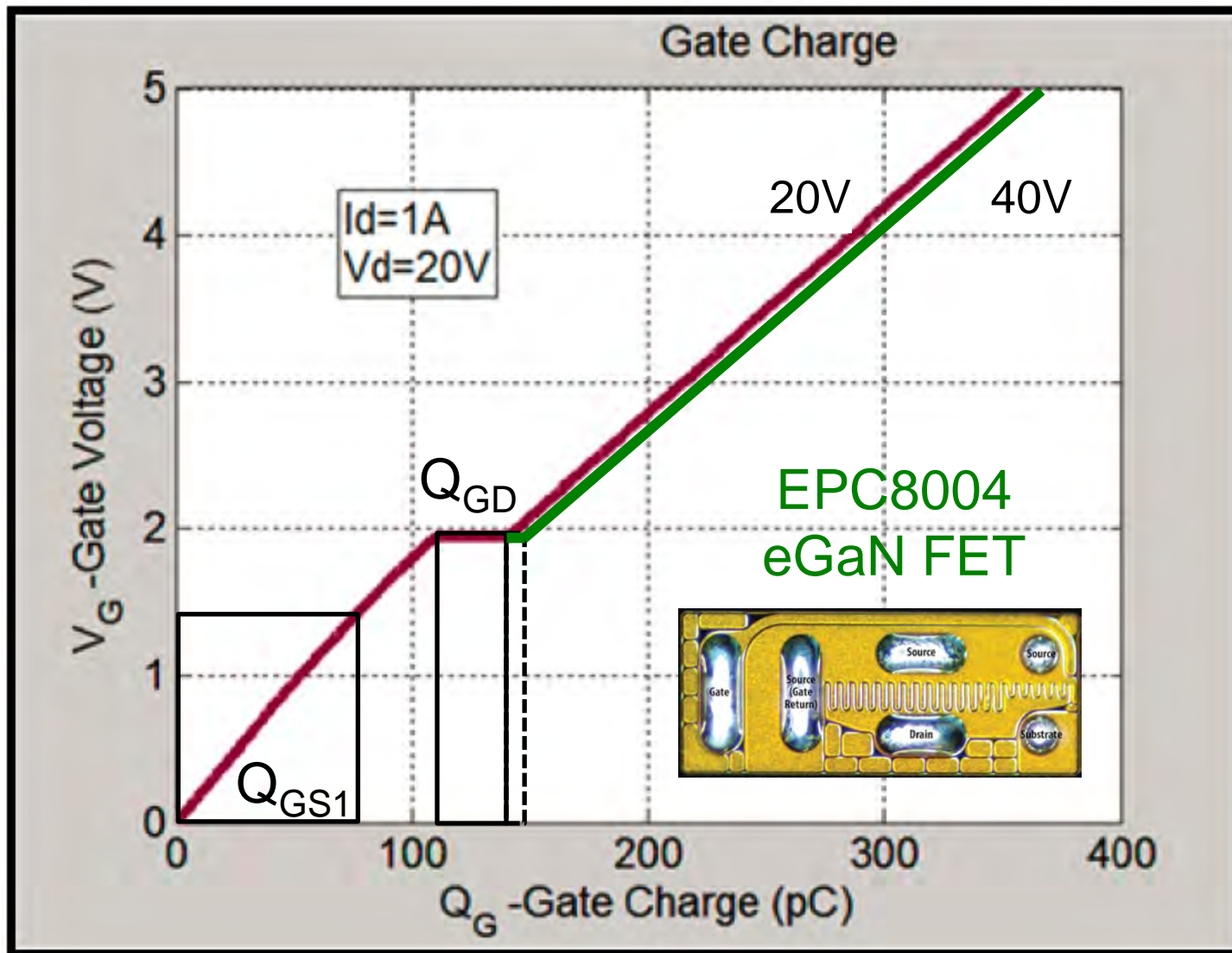

# Low Parasitic Layout


Top Layer

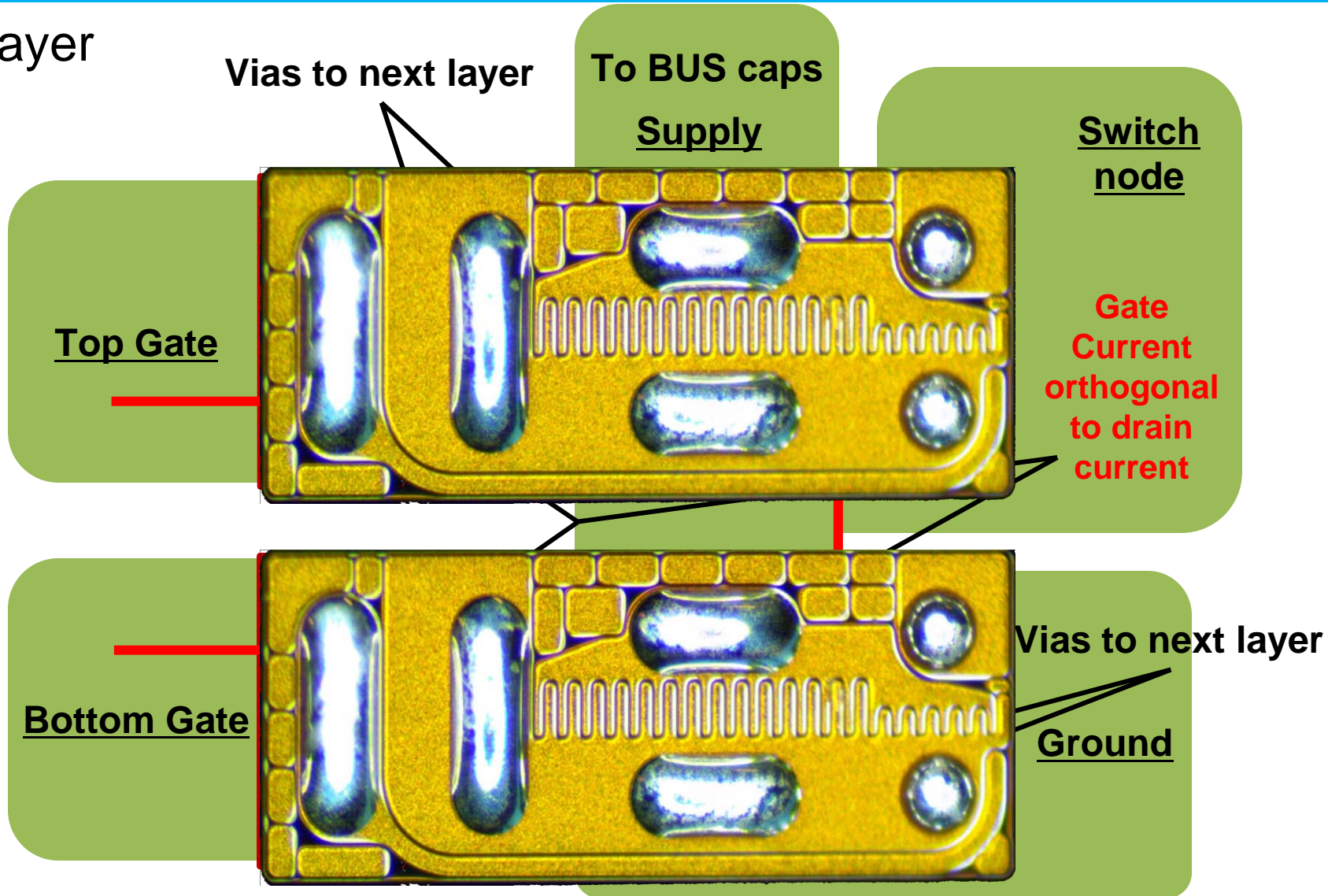





# Low Parasitic Layout

First InnerLayer

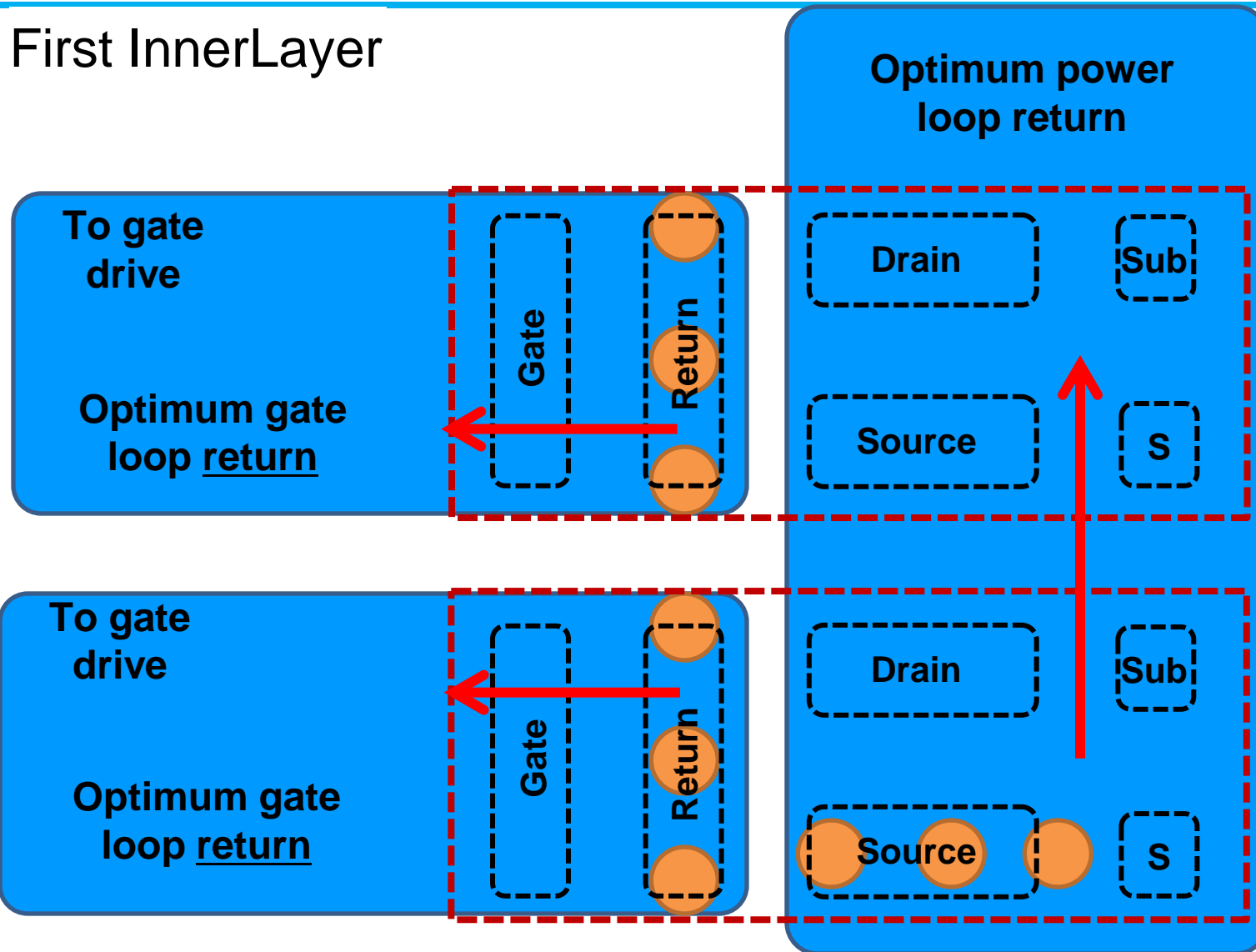

# ET Prototype Board

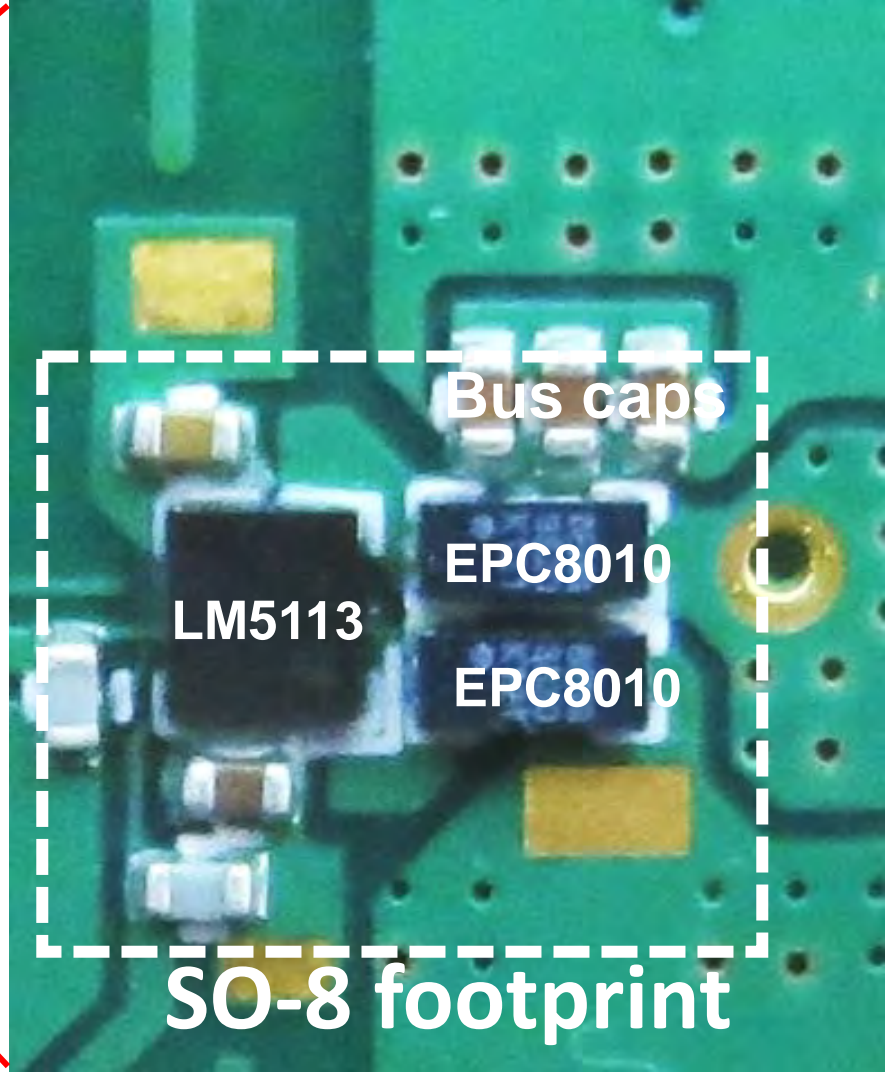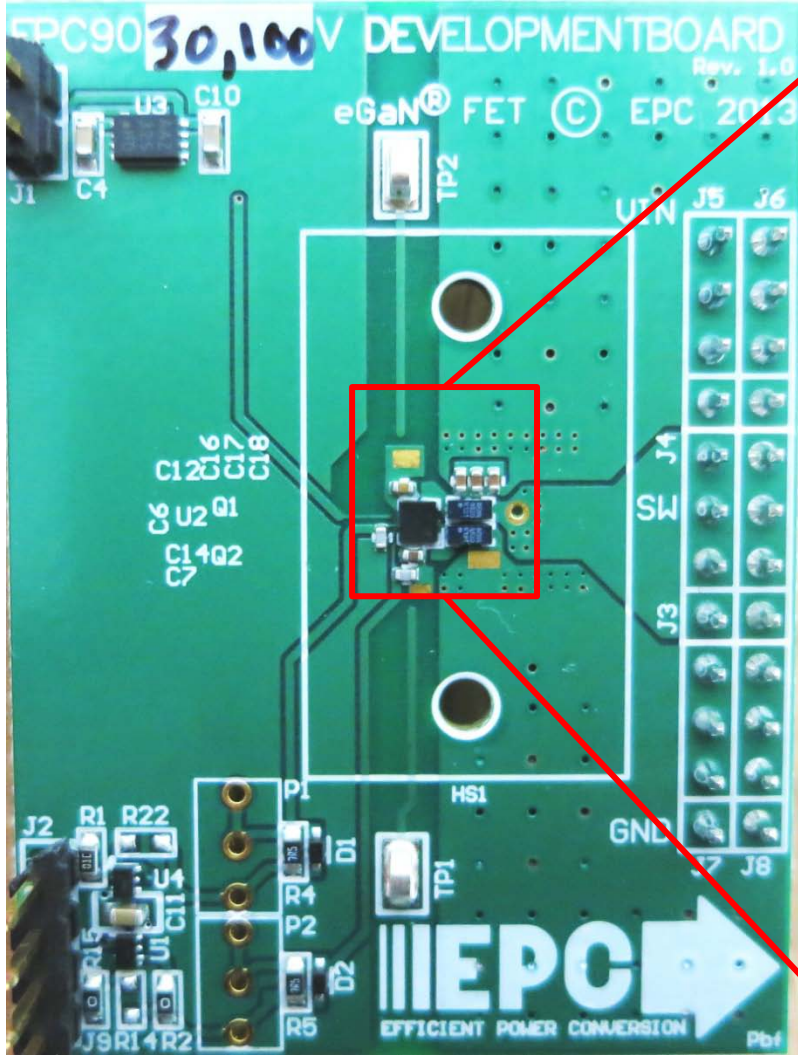




# 15 V<sub>IN</sub> to 3.3 V<sub>OUT</sub>, 10 MHz




RFIC 2014

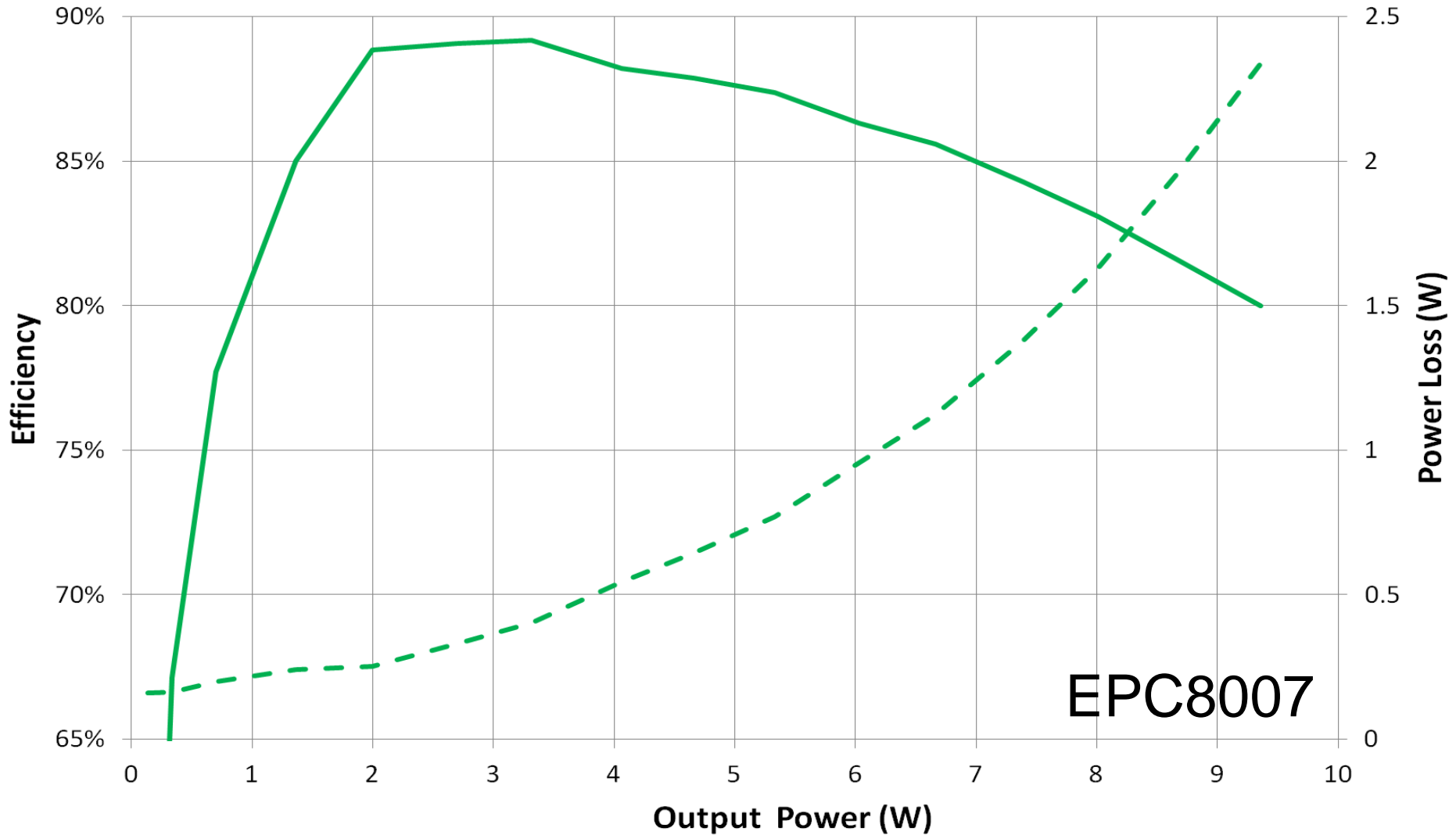


EPC8007
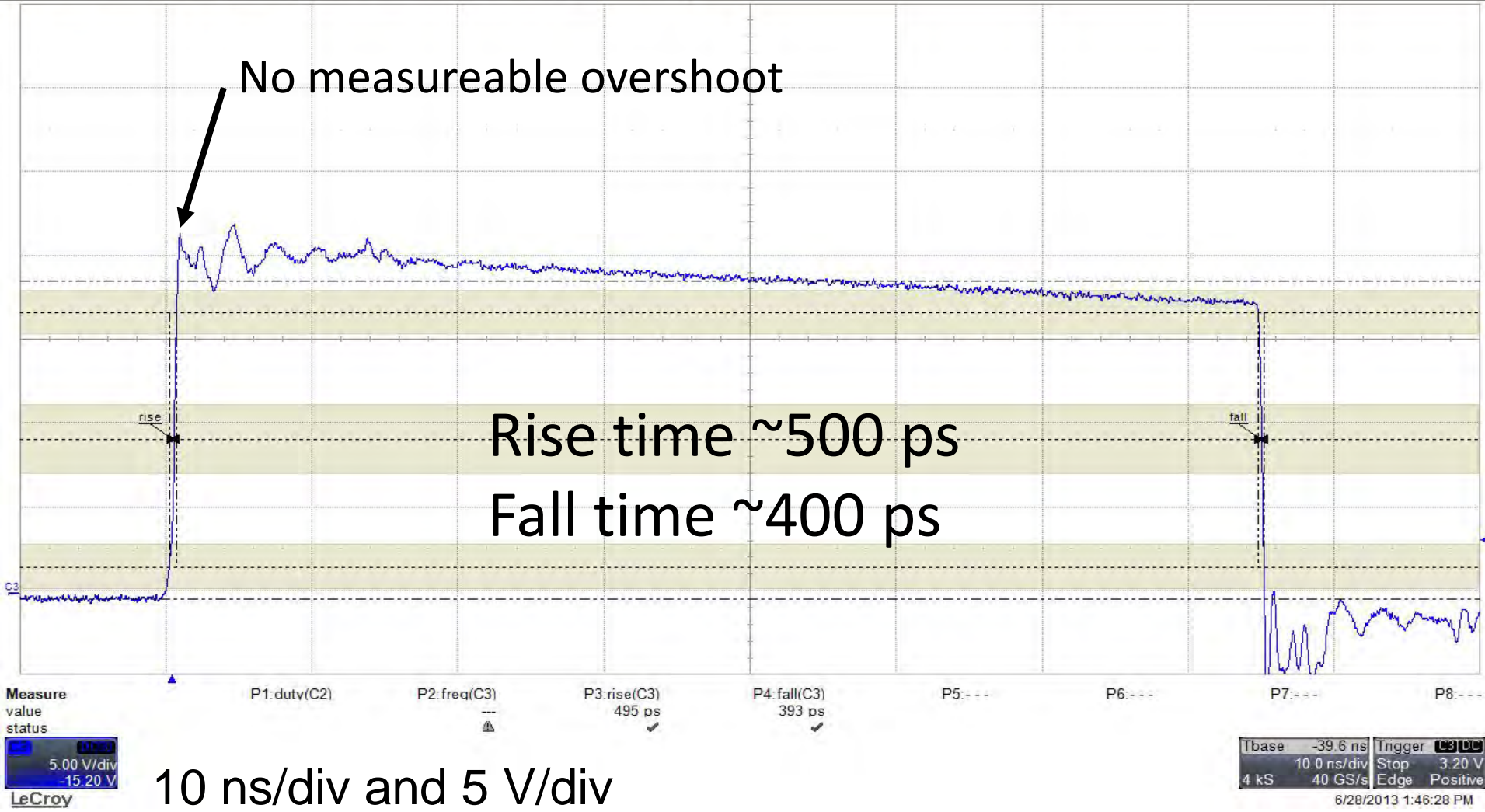
# 20 V<sub>IN</sub> at 4 A<sub>OUT</sub>

File Vertical Timebase Trigger Display Cursors Measure Math Analysis Utilities Help



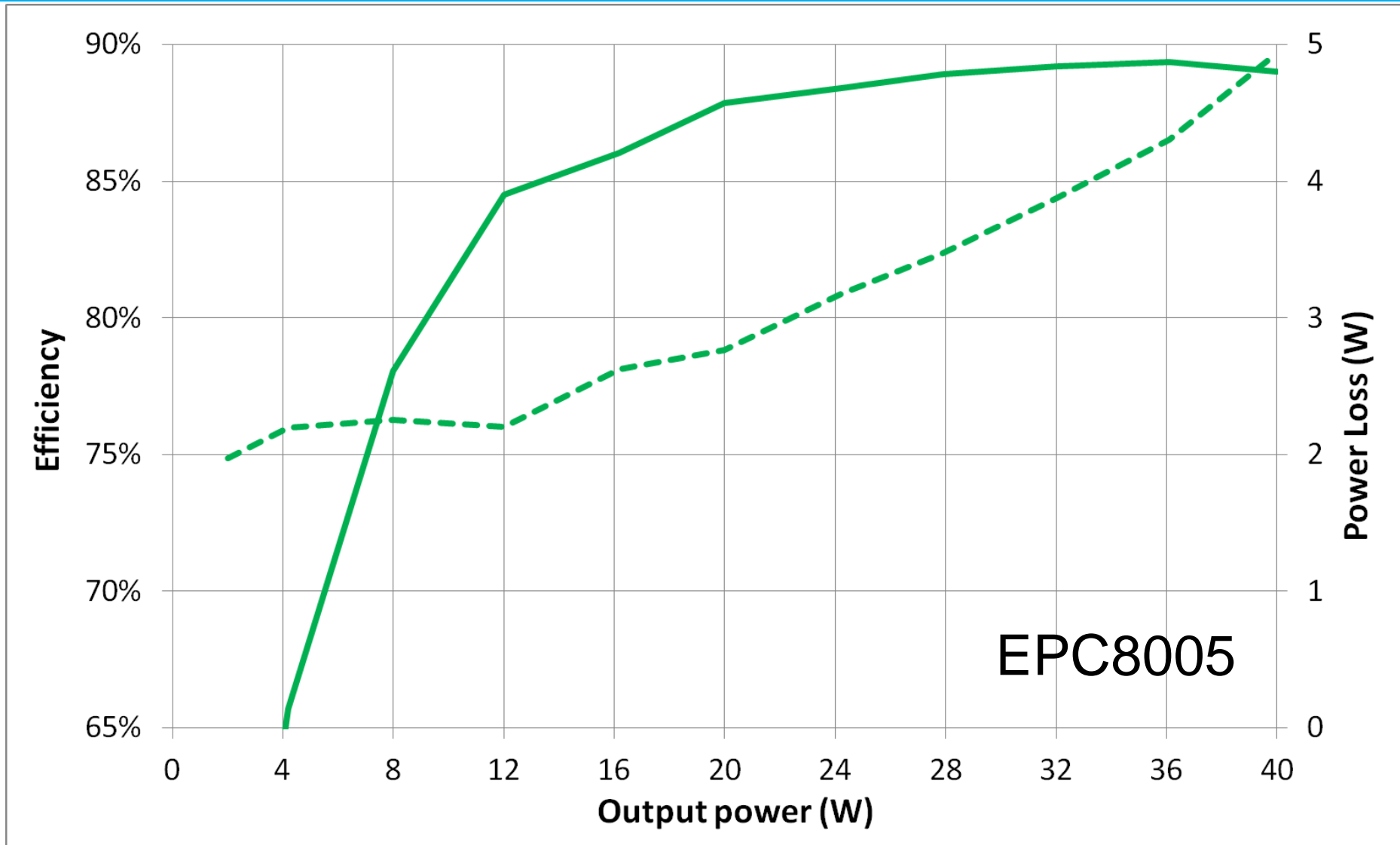
# 42 V<sub>IN</sub> to 20 V<sub>OUT</sub>, 10 MHz


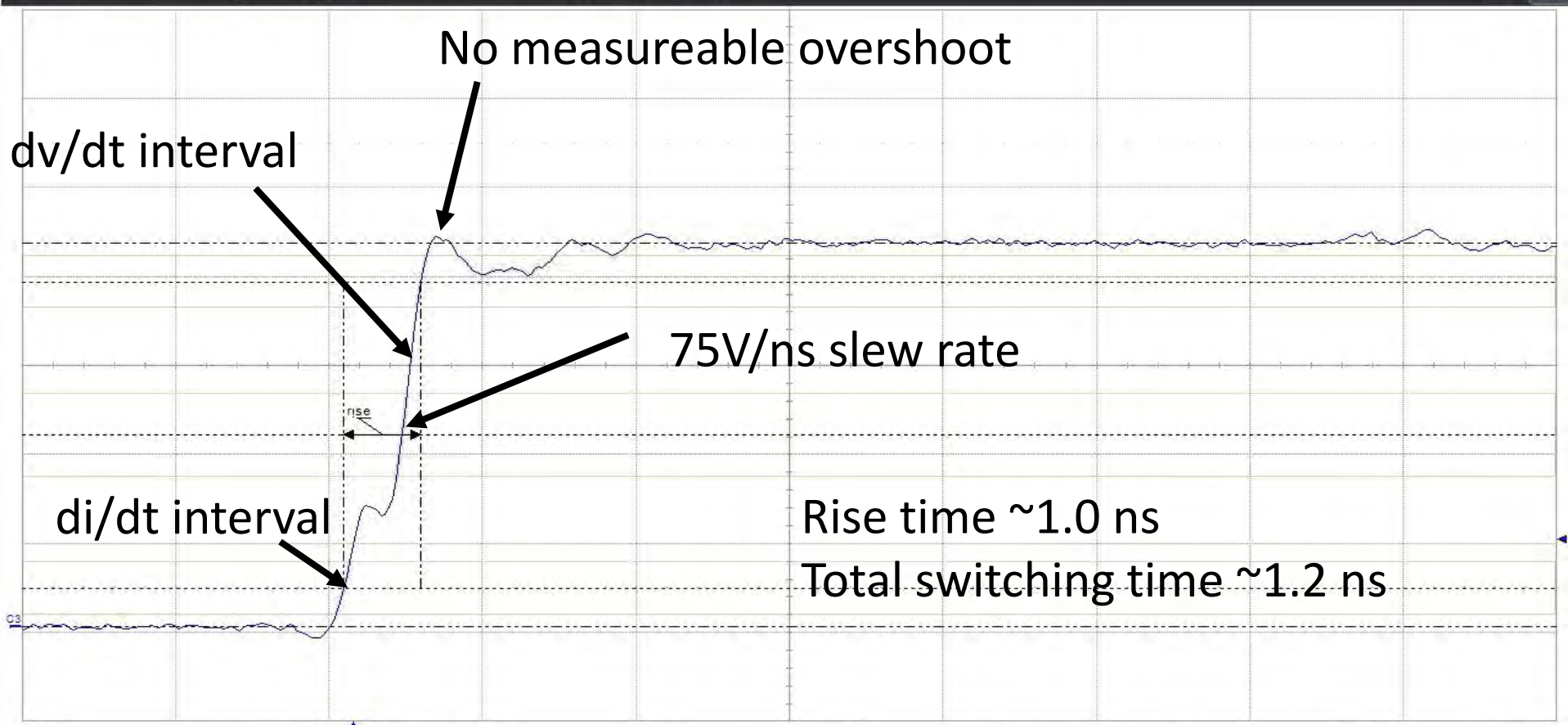
# 42 V<sub>IN</sub> at 1 A<sub>OUT</sub>

File Vertical Timebase Trigger Display Cursors Measure Math Analysis Utilities Help Zoom Undo



Measure value status

P1:duty(C2) P2:freq(C3) P3:rise(C3) 1.005 ns P4:fall(C3) P5:--- P6:--- P7:--- P8:---


10.0 V/div  
-29.30 V  
LeCroy

Tbase	-5.68 ns	Trigger	C3 [DC]
	2.00 ns/div	Stop	9.8 V
400 S	20 GS/s	Edge	Positive


7/2/2013 3:15:51 PM

2 ns/div and 10 V/div, 1 GHz 100:1 1 pF TM probe
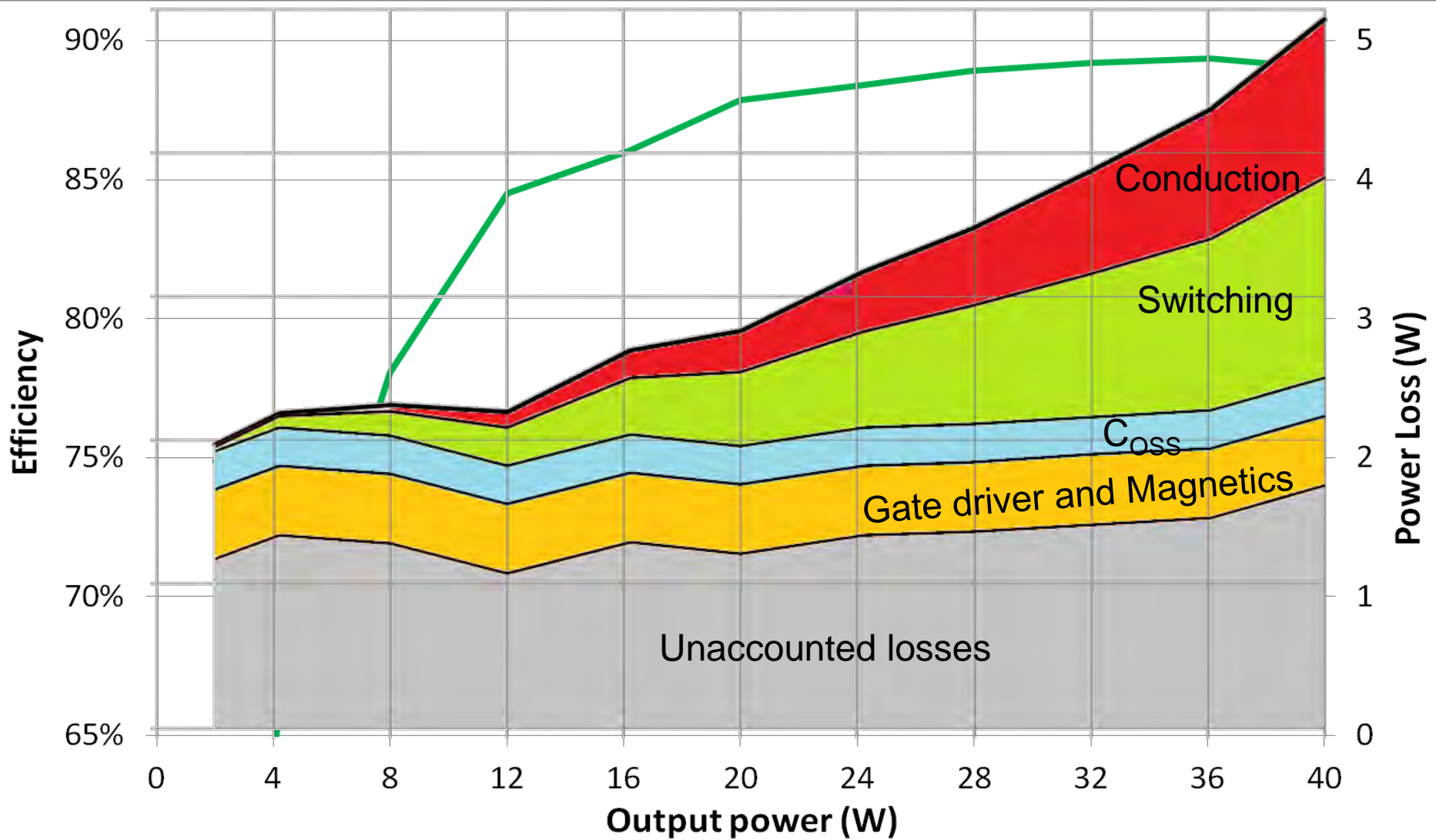
# 42 V<sub>IN</sub>, 20 V<sub>OUT</sub>, 10 MHz




# Loss Investigation

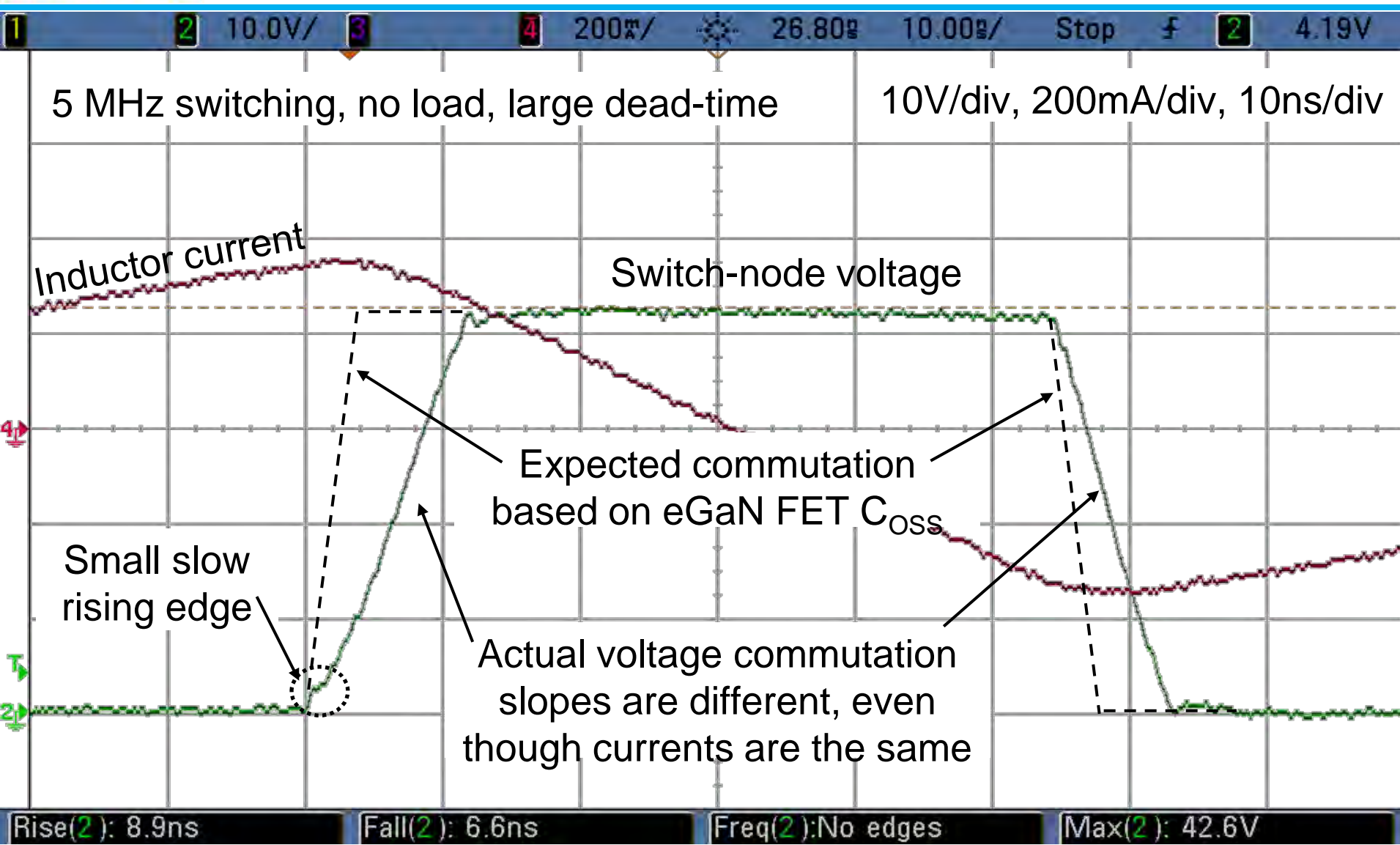





# No-load Switching

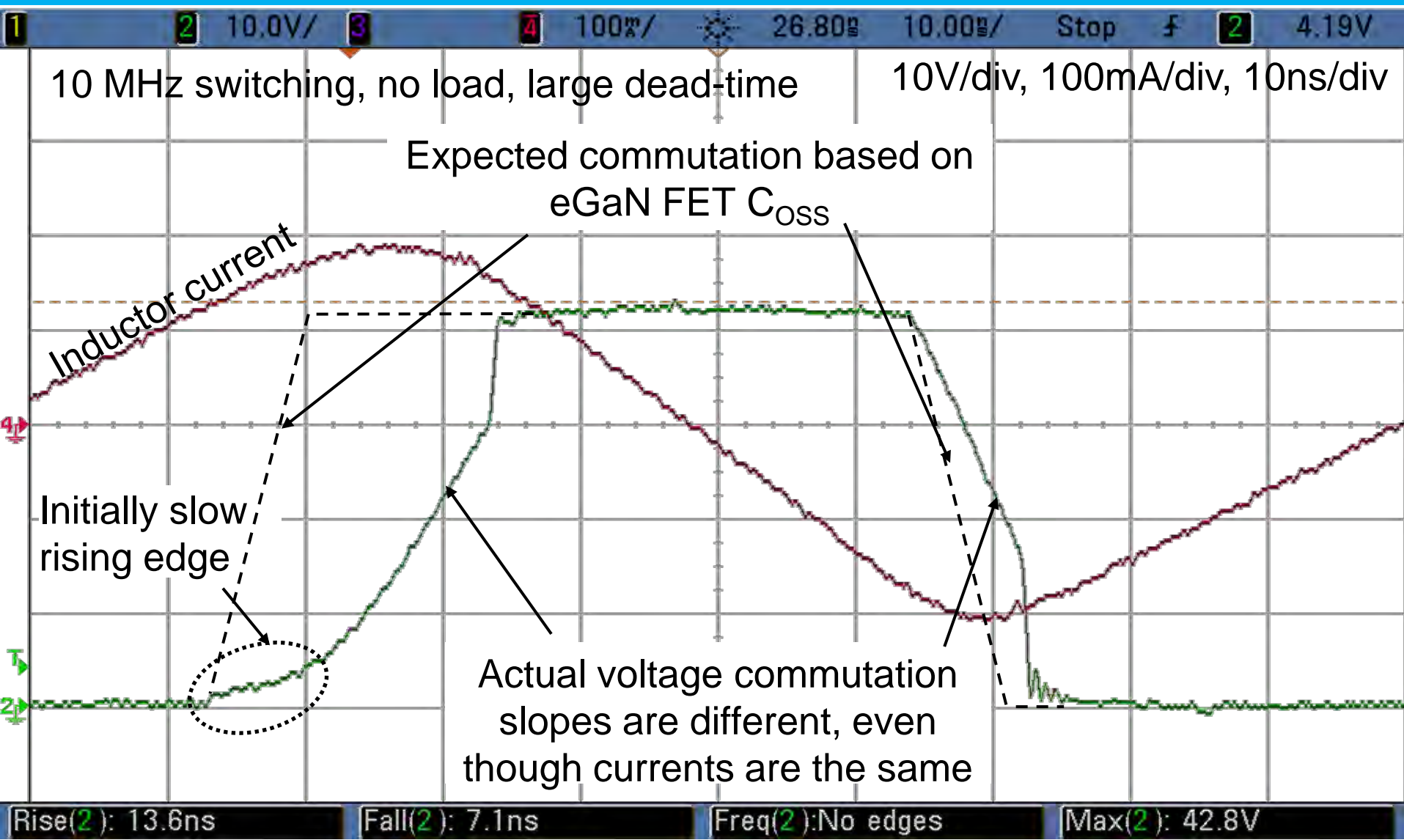


# Parasitic Losses

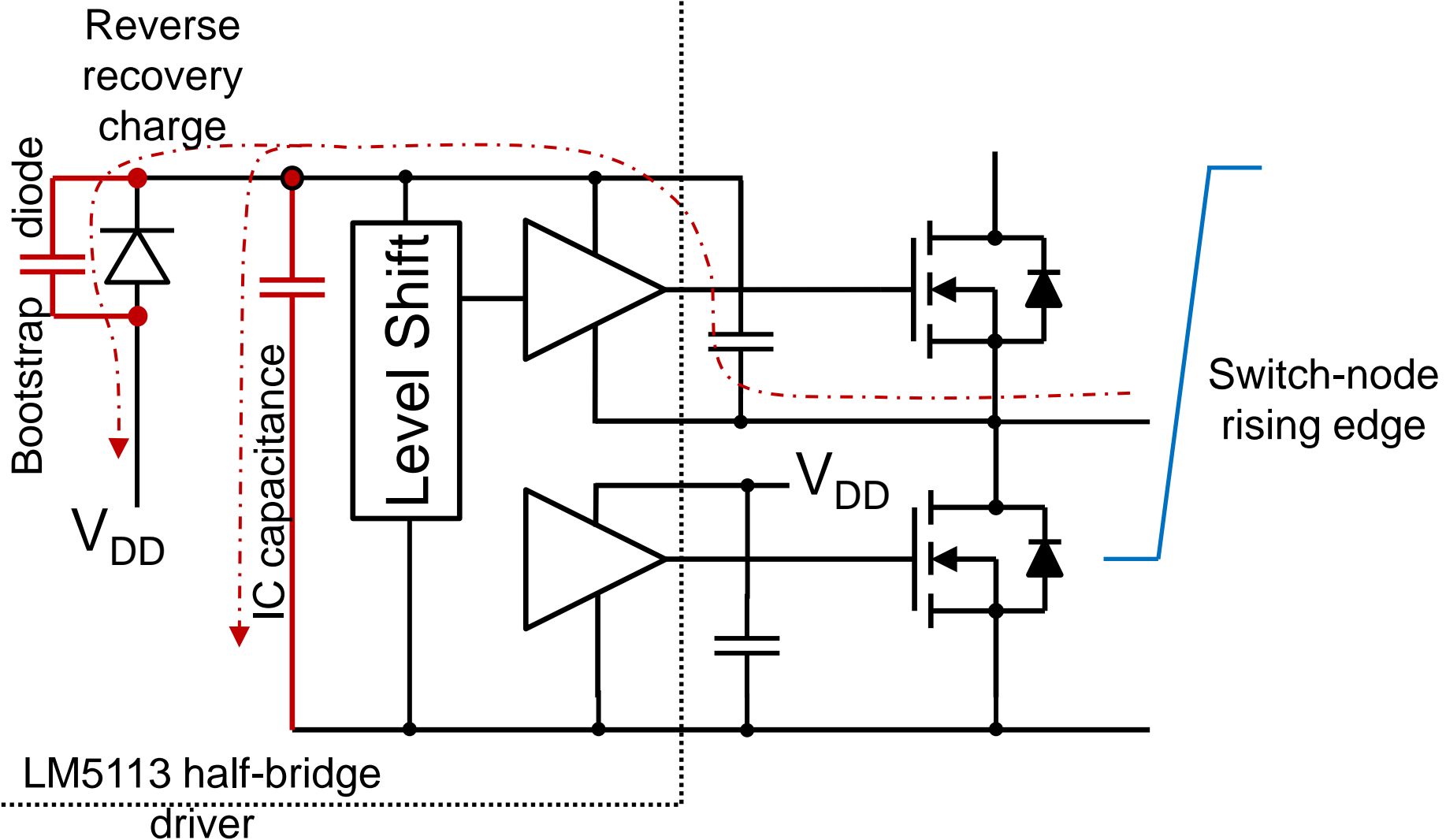


# Loss Breakdown

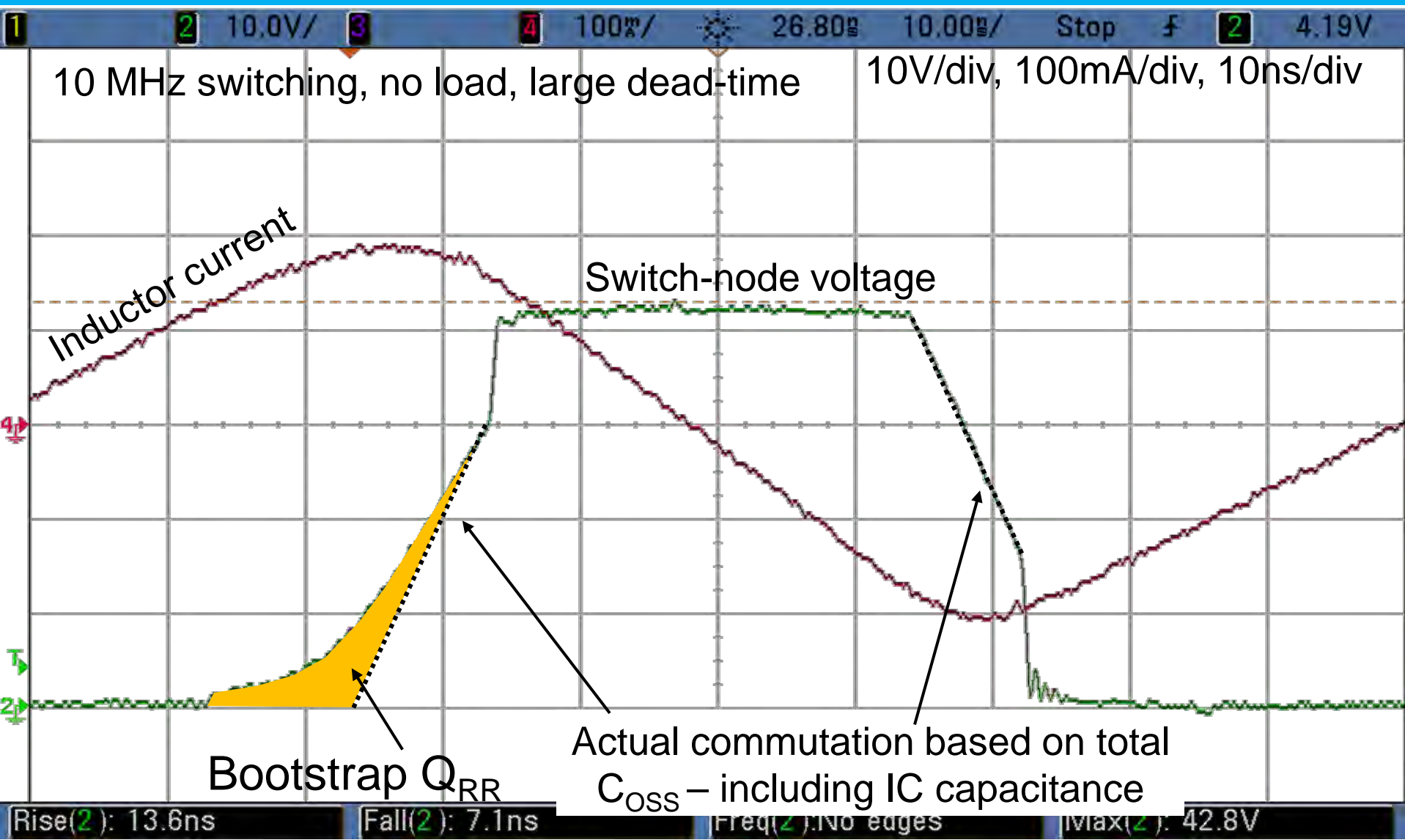


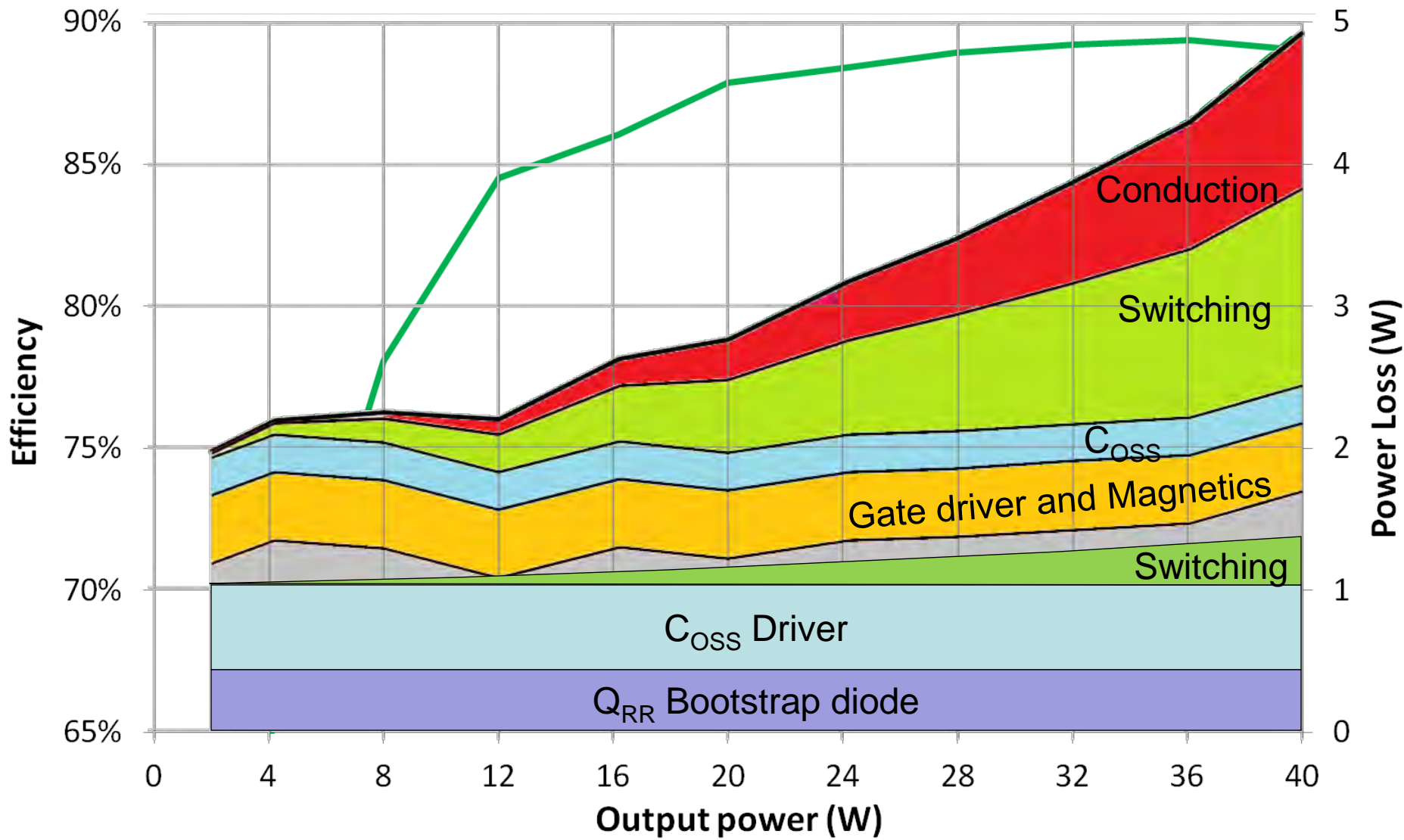
# 42 V<sub>IN</sub>, 20 V<sub>OUT</sub>, 10 MHz




# eGaN FET Limited Efficiency

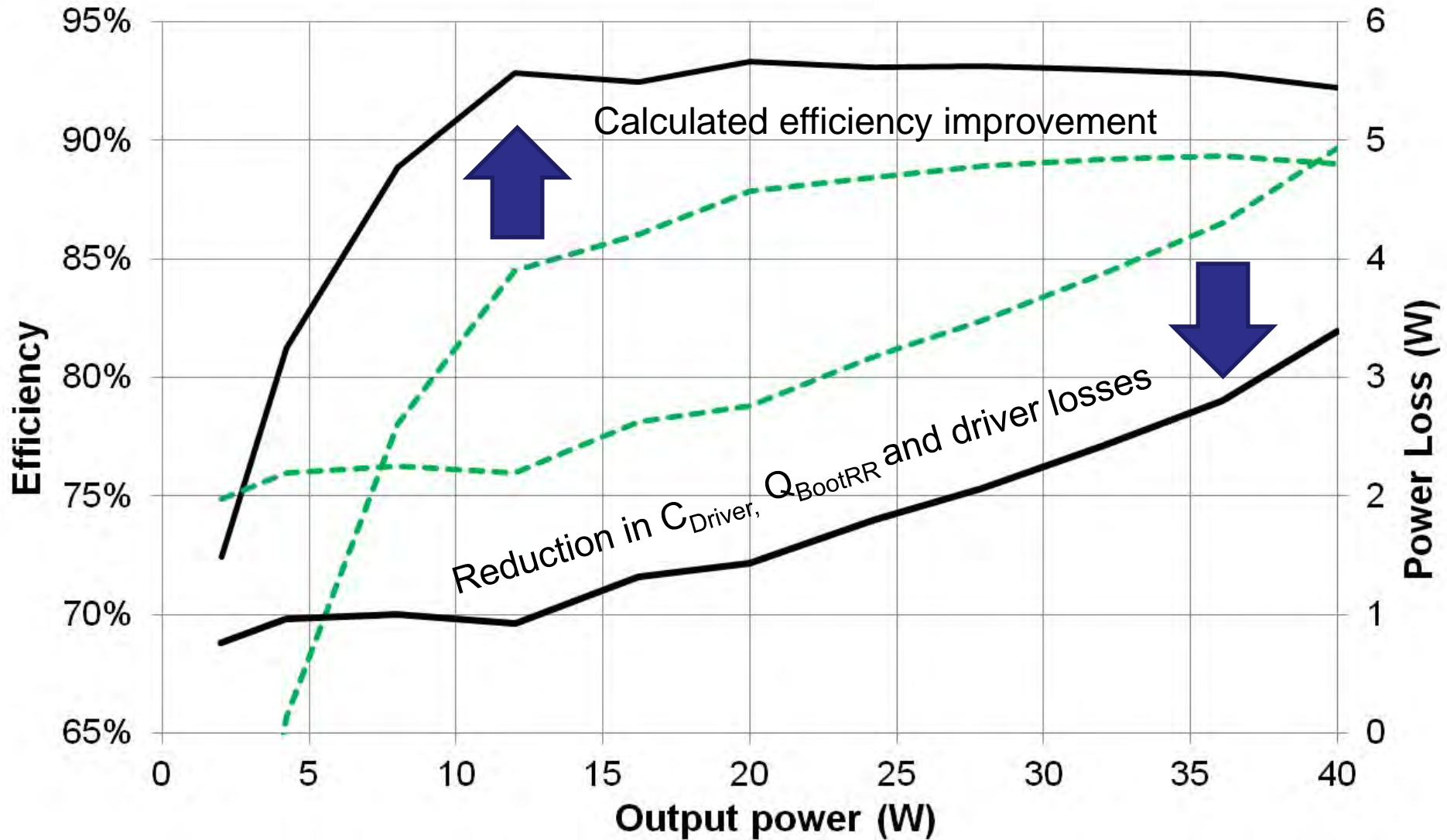

# Point of Load Buck Converter

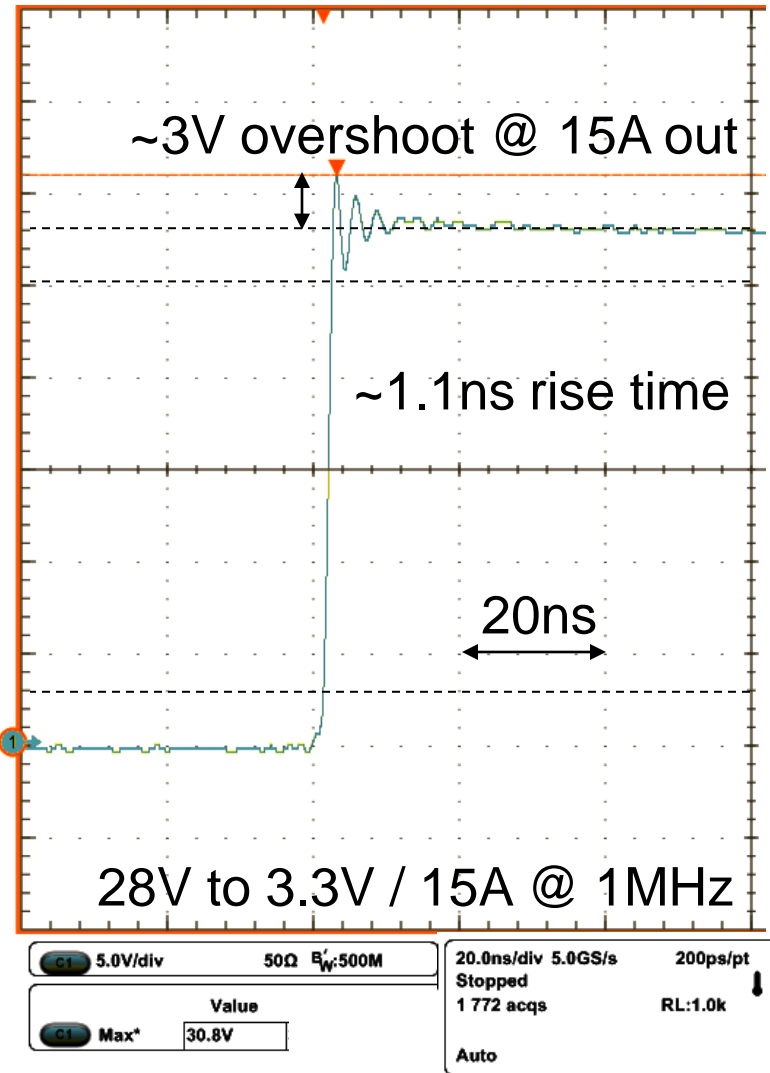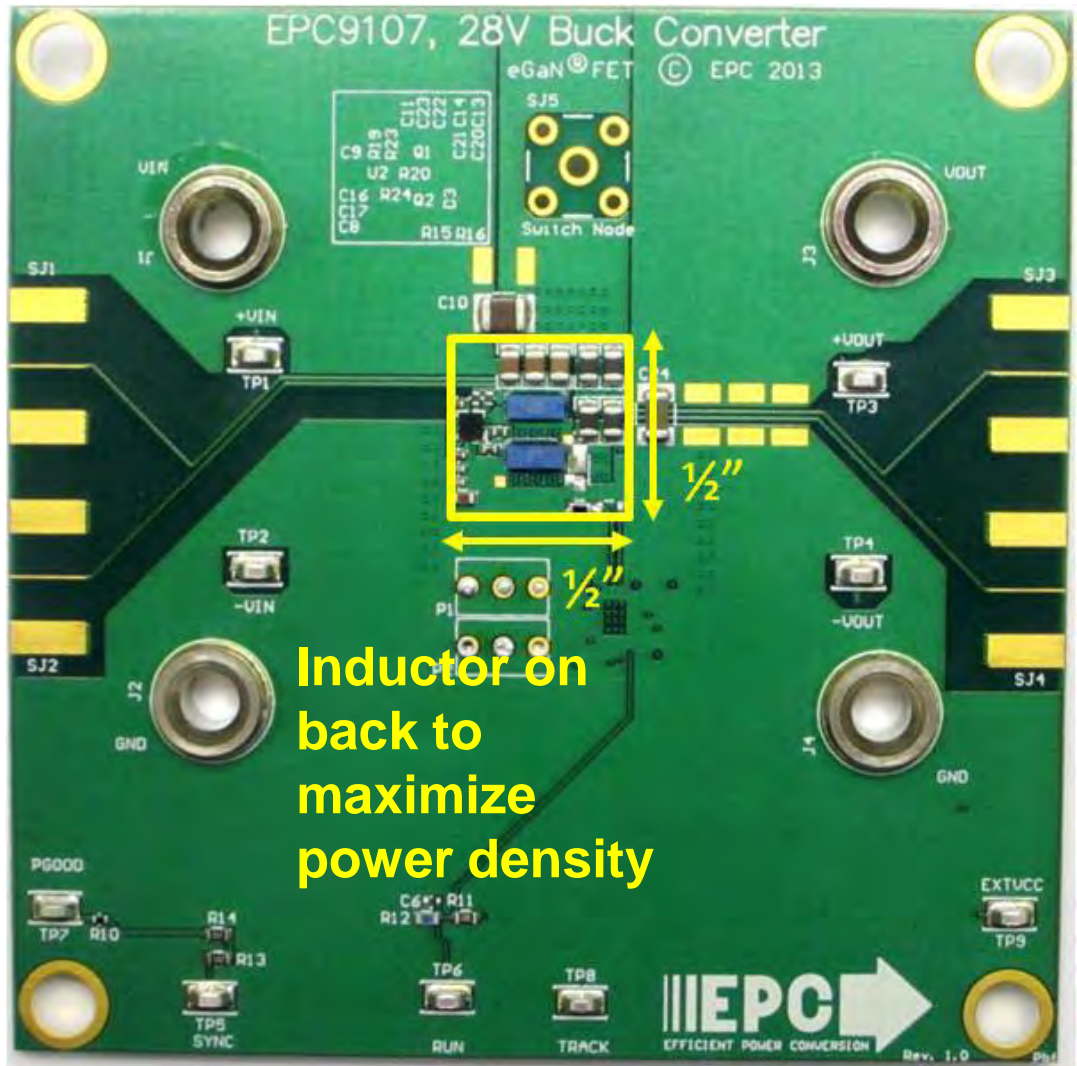

# EPC9107 Efficiency Results

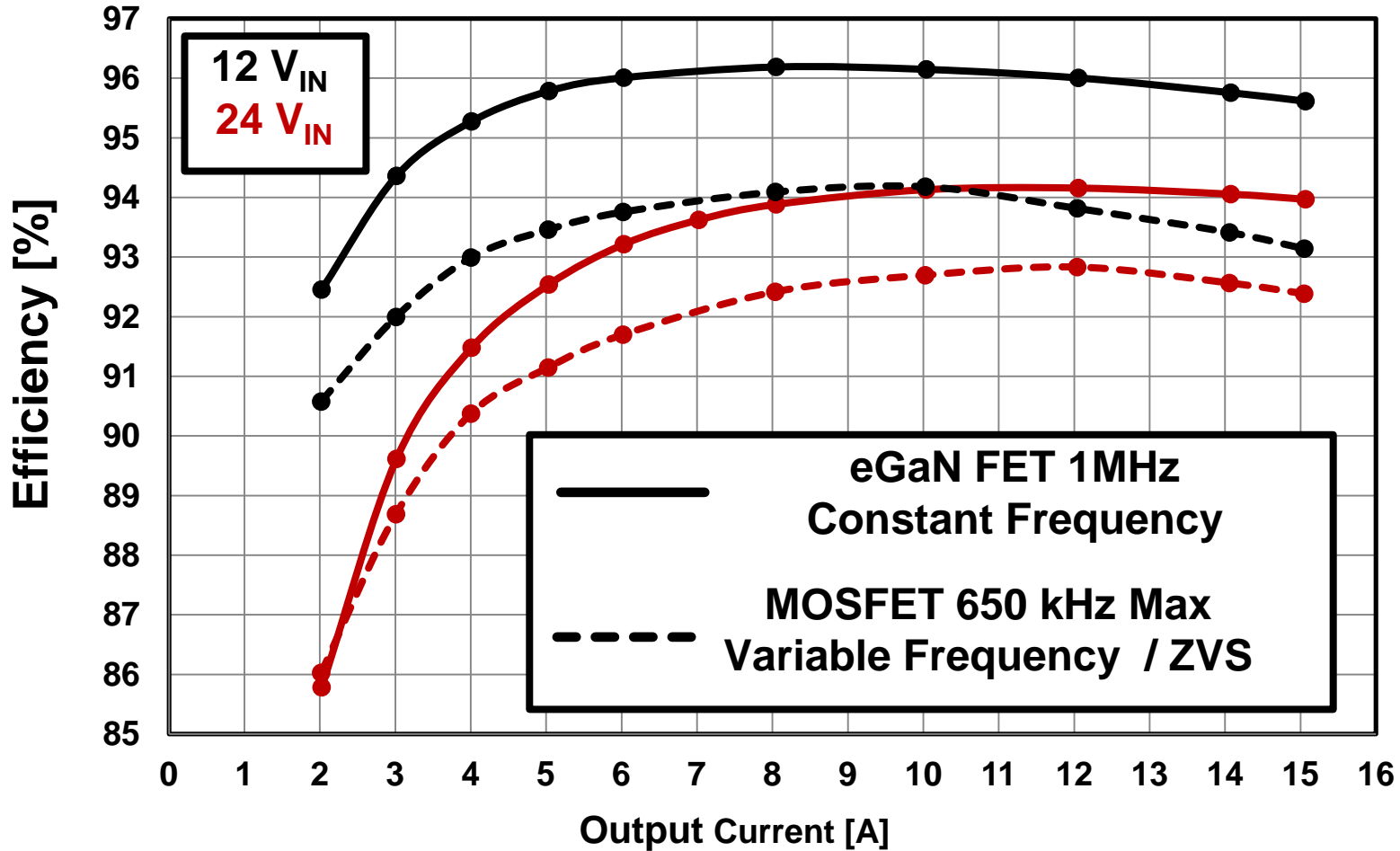

**$V_{OUT} = 3.3 V, f_{sw} = 1 MHz,$**

**GaN Switch/Synchronous Rect.: EPC2015, Driver LM5113**



# Device Summary



RFIC 2014

- **EPC8000 eGaN FETs proven up to 10 MHz**
- **New devices enable higher switching frequencies**
- **Switching 42V, 40W at 10MHz at 89% possible**
- **Driver parasitics limit performance**
  - **Doubles light load losses**
- **Gate driver improvements will allow further increase in switching frequency**





# Power Supply Summary



RFIC 2014

- **EPC8000 eGaN FETs enable High Frequency Power modulation.**
- **Superior FoM of eGaN FETs allow higher efficiency at higher frequencies.**
  - **Applicable to 42 V and 28 V DC to DC converters.**
  - **Enables very low duty cycle conversion**
- **eGaN FETs reduce energy cost.**



*The end of the road  
for silicon.....*

*is the beginning of  
the eGaN FET  
journey!*